
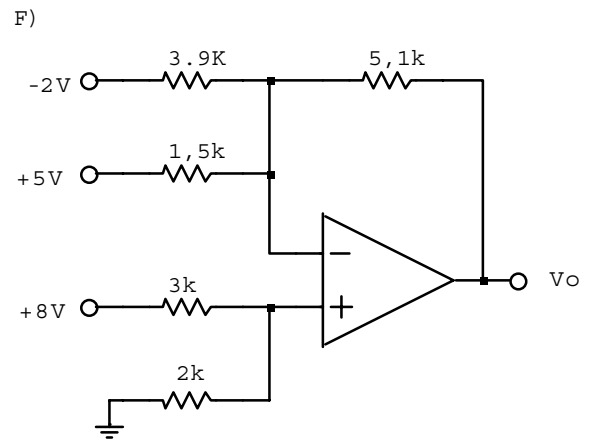
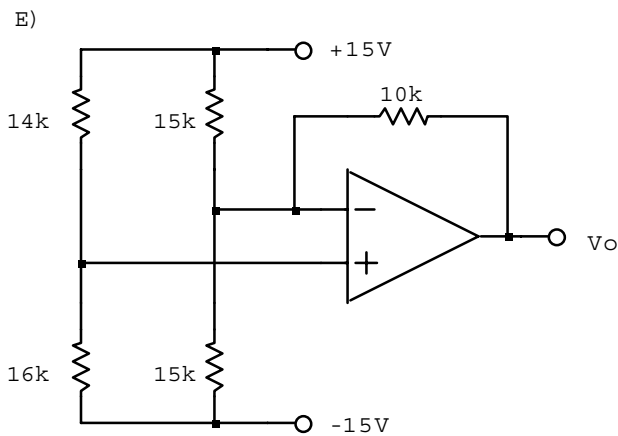
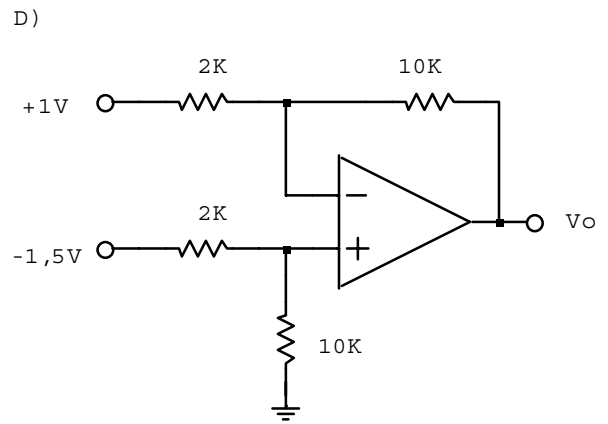
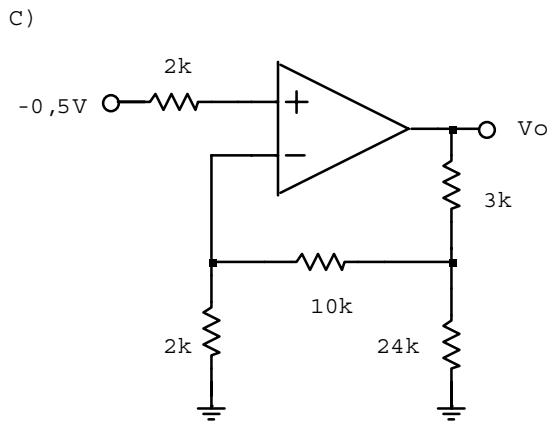
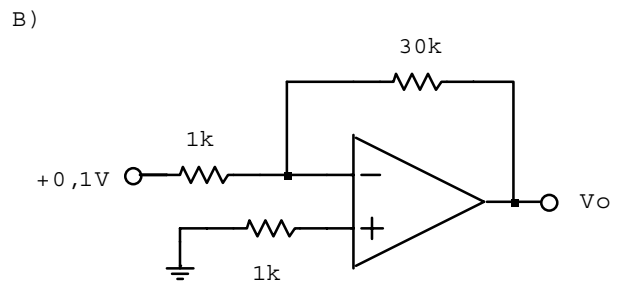


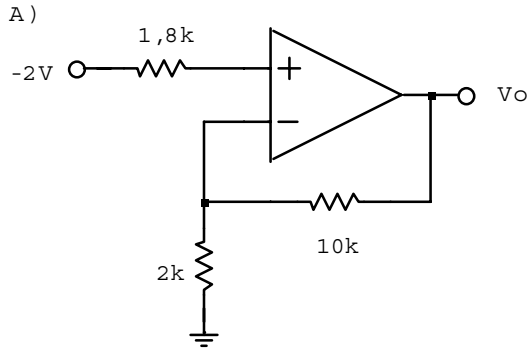EXERCISE IDEAL OP AMP ANALYSIS

No.1 Assuming ideal op amps, determine V_o for each and every circuit shown below.




EXERCISE

IDEAL OP AMP ANALYSIS


No.2 Assume typical op amp data for circuits A through E and worst case values for circuit F.

Op amp parameters for $V_{SUP}=\pm 15V$	minimum	typical	maximum
O/P voltage swing	$\pm 12V$	$\pm 13,5V$	-
I/P voltage range	$\pm 11V$	$\pm 12,5V$	-
Short circuit current	$\pm 12\text{ mA}$	$\pm 20\text{ mA}$	-


A) Determine V_x .

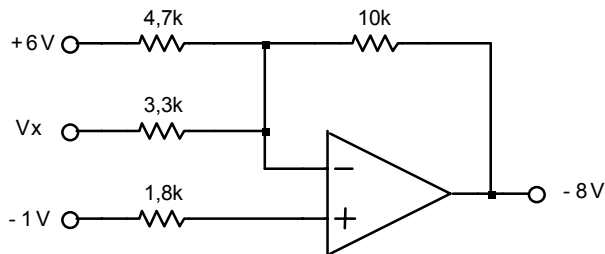


D) Determine V_o .

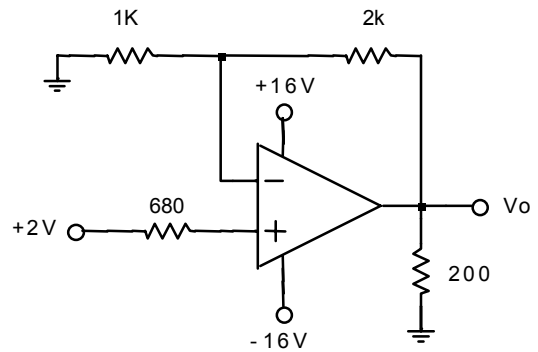

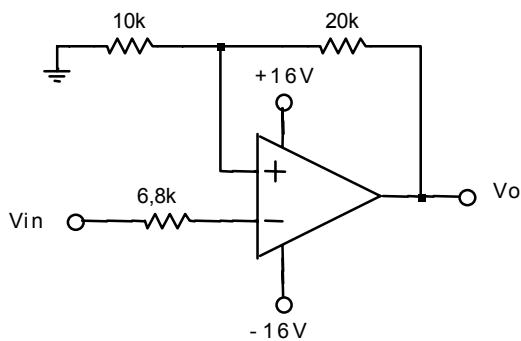
B) Determine V_o for $V_{in} = +6V$ and $V_{in} = -6V$.




E) Determine V_o .

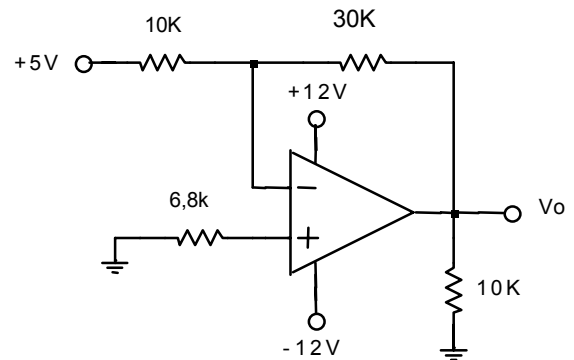

C) Determine V_o .

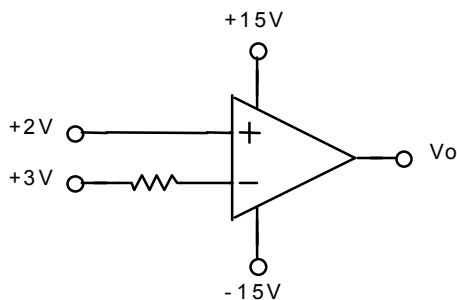

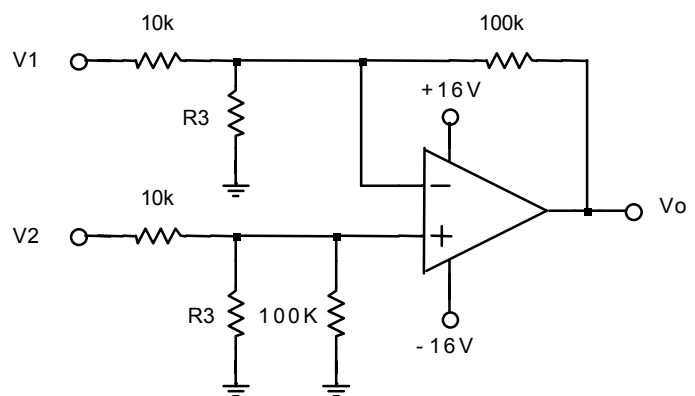F) Determine the maximum value of R_3 if we do not want to saturate the inputs of the op amp given that V_1 and V_2 range from 80V to 100V.




EXERCISE

No.3


$$\Delta V_o(PP) = V_o(t_2) - V_o(t_1) = -\left(\frac{1}{R_F C_F}\right) \int_{t_1}^{t_2} V_{in(AC)} dt \quad \text{if } \omega > \frac{10}{R_F C_F}$$

$$V_{in(ave)} = V_{in}^+ \left(\frac{PW}{T}\right) + V_{in}^- \left(\frac{SW}{T}\right) \quad \text{for a squarewave}$$

IDEAL OP AMP ANALYSIS

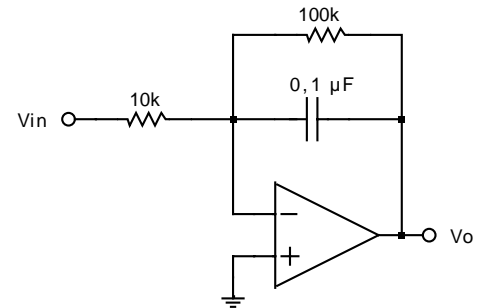

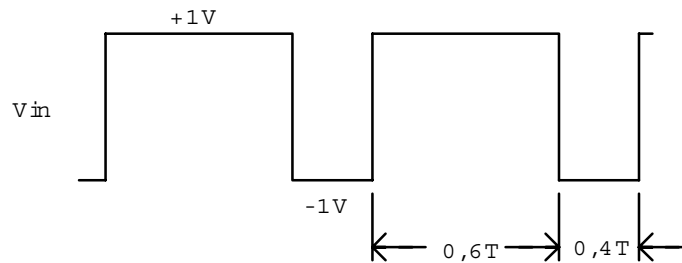A) Draw the output waveform with respect to V_{in} shown for frequencies of 50 Hz, 100 Hz, 1 kHz and 10 kHz - label waveforms with AC and DC values as well as PW and SW.



B) If V_{in} is a 2 V_{pp} squarewave with a 50% duty cycle, calculate the frequency of V_{in} that will produce $V_o = 1 V_{pp}$


C) Repeat step B for 75% duty cycle.

D) If V_{in} is a 10 V_{pp} triangular wave with a frequency of 5 kHz, draw the expected O/P waveform with respect to V_{in} .

No.4 A) Determine the output waveform relative to an input triangular wave with a 10 V_{pp} amplitude and a frequency of 250 Hz.

B) Determine the output waveform relative to an input square wave with a 2 V_{pp} amplitude and a frequency of 250 Hz.

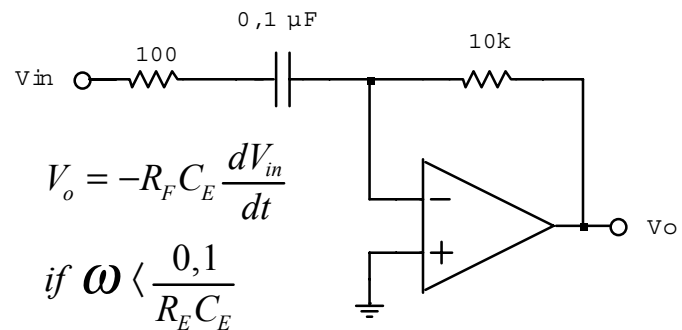C) What is the function of the 100Ω resistor?




No.5 PHASE SHIFTER

$$A_{VF} = \frac{P1 + jX_C}{P1 - jX_C} \quad |A_{VF}| = 1$$

$$\angle A_{VF} = 2 \arctan \frac{X_C}{P1}$$






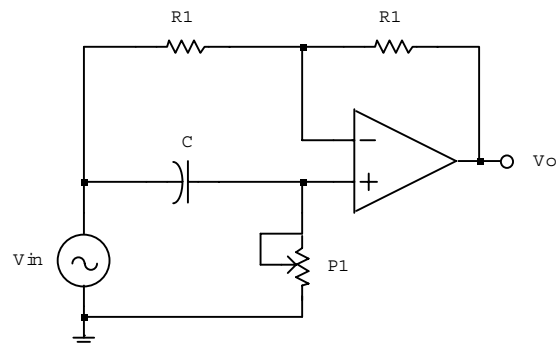
Design the circuit in order to obtain a phaseshift of 20° to 180° with a 100K pot (P1) at a frequency of 1 kHz.



EXERCISE

IDEAL OP AMP ANALYSIS


SOLUTIONS

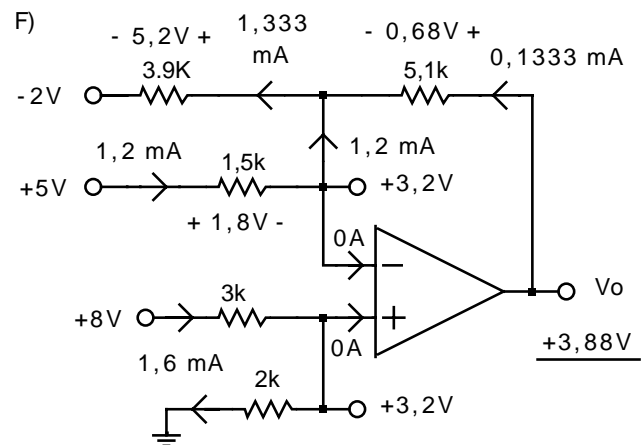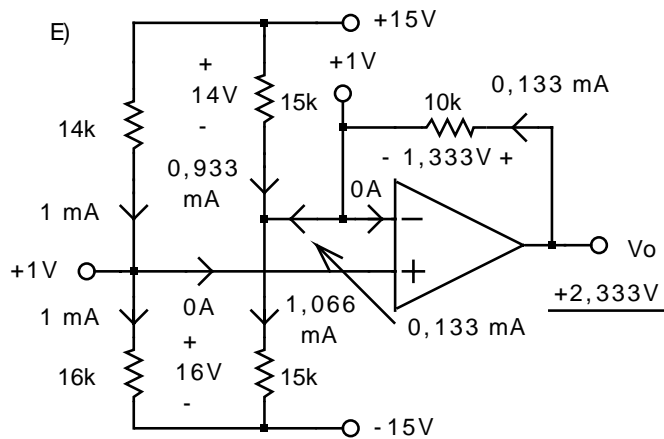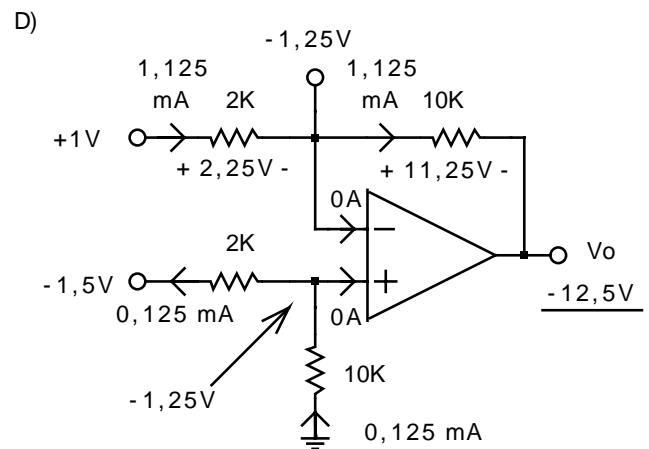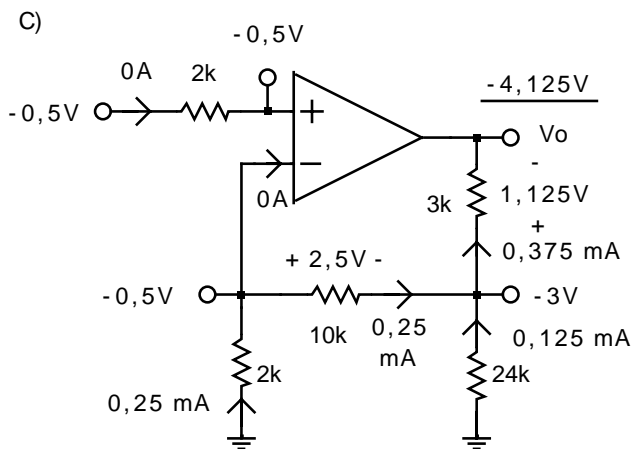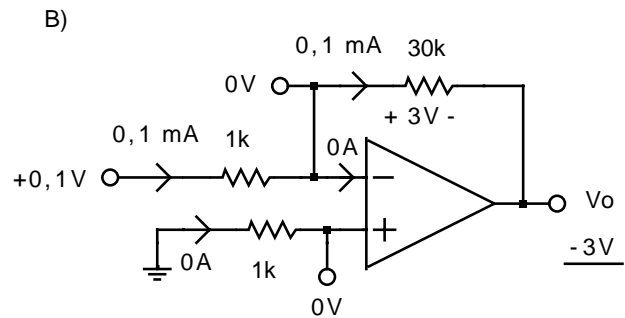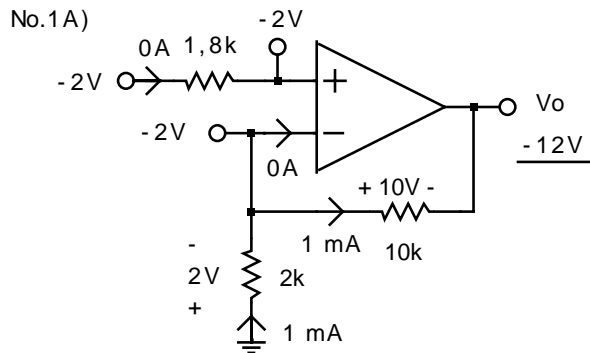


EXERCISE

IDEAL OP AMP ANALYSIS

No.2 A)

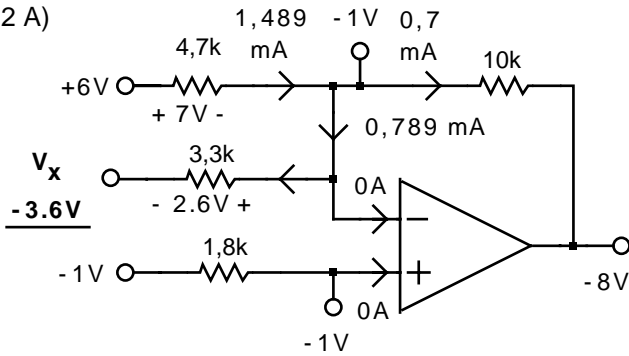

C)

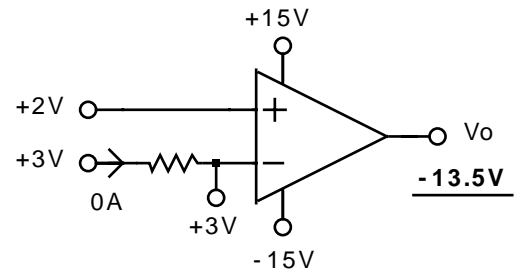


No feedback, the output saturates with a polarity determined by the sign of the differential I/P voltage:

$$V_o = A_d (V^+ - V^-) = (2-3) = -$$

$$V_o = -V_{sat} = \underline{-13.5V}$$

B)

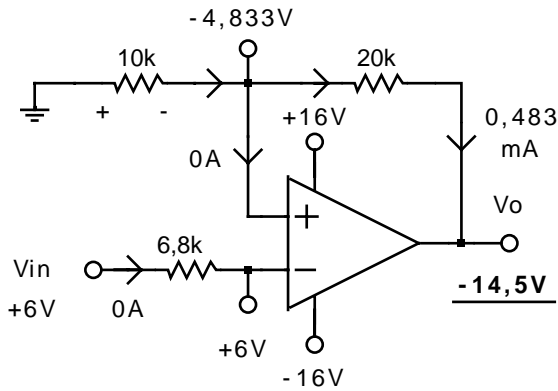


Positive feedback will make the output saturate with a polarity determined by the sign of the differential I/P voltage. With +6V applied to the -ve I/P of the op amp, the O/P should be of the opposite polarity, therefore assume

$$V_o = -V_{sat} = \underline{-14.5V}$$

and determine the V^+ and verify the sign of the differential I/P voltage in order to validate your assumption of $V_o = -V_{sat}$, that is:

$$V_o = A_d (V^+ - V^-) = (-4.83-6) = -$$

therefore the assumption was valid.

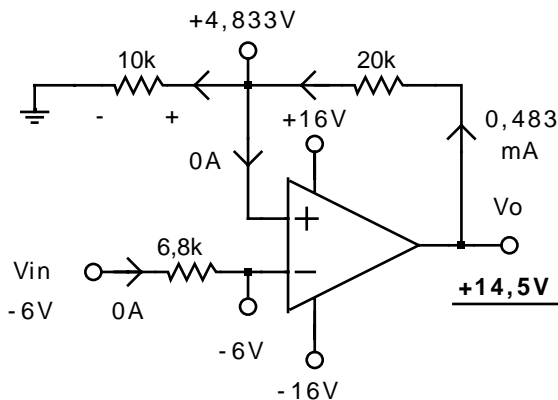

Same procedure here, except now V^- is negative, therefore the O/P polarity is expected to be positive:

$$V_o = +V_{sat} = \underline{+14.5V}$$



Verify assumption with sign of $V_d = (V^+ - V^-)$

$$V_o = A_d (V^+ - V^-) = (+4.83-(-6)) = +$$

EXERCISE


IDEAL OP AMP ANALYSIS

2 D)

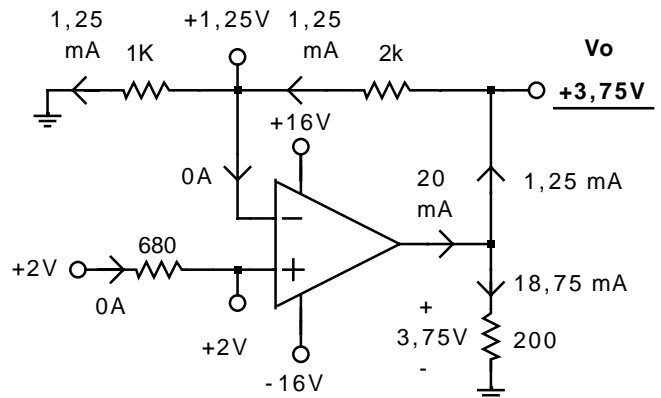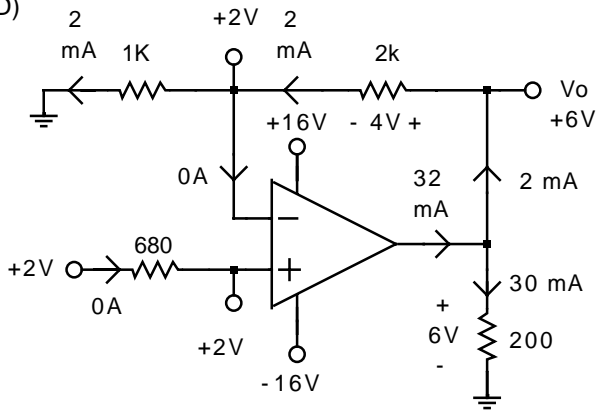


Output of op amp has reached current limit, notice that $V^- = V^+$ and -ve feedback is rendered ineffective not forcing $V^- = V^+$

E)

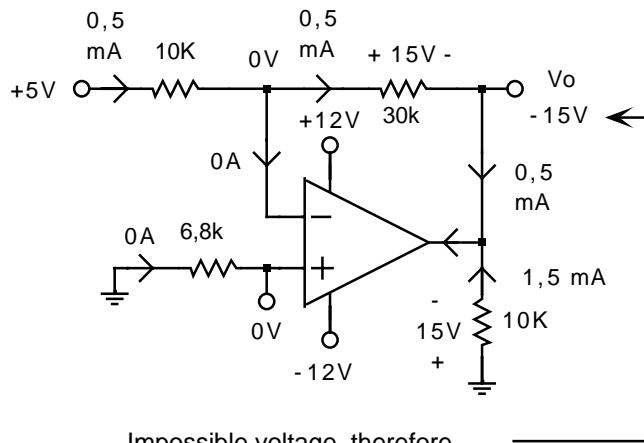


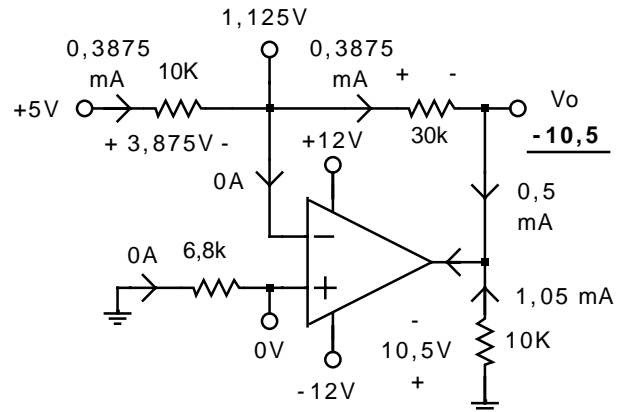Impossible voltage, therefore $V_o = -V_{sat} = -10.5V$ typical.



Output of op amp has reached saturation, notice that $V^- = V^+$ and -ve feedback is rendered ineffective not forcing $V^- = V^+$

F)

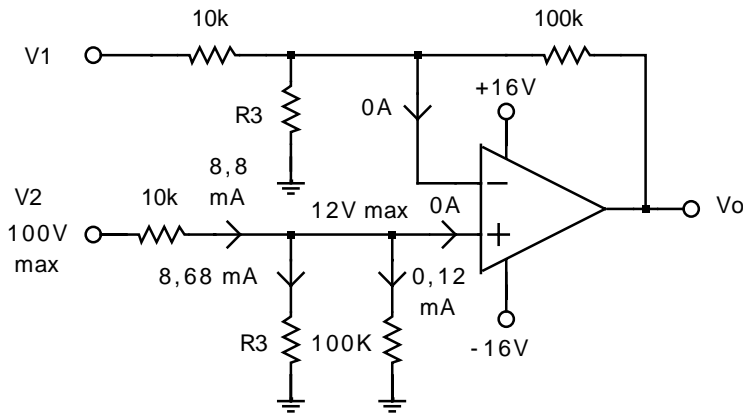

$$V^- \text{ or } V^+ \text{ max} = 16 - 4 = 12V$$

$$R_3 < 12V / 8.68 \text{ mA} = \underline{1382}$$

R_3 should be less than 1382

in order to keep V^- and V^+ inside a safe range of $\pm 12V$.

EXERCISE

IDEAL OP AMP ANALYSIS

No.3

$$\text{If } F \gg \frac{10}{2\pi R_F C_F} = \frac{10}{2\pi 100k \times 0,1\mu} = 159 \text{ Hz then } \Delta V_{o(PP)} = -\left(\frac{1}{R_E C_F}\right) \int_{t_1}^{t_2} V_{in(AC)} dt$$

A)

$$V_{(ave)} = V^+ \left(\frac{PW}{T}\right) + V^- \left(\frac{SW}{T}\right)$$


$$V_{in(DC)} = +0,2V$$

$$\Delta V_{o(PP)} = -1000 \int_{t_1}^{t_2} V_{in(AC)} dt$$

$$\Delta V_{o(PP)} = -1000 \times \text{area}$$

$$\Delta V_{o(PP)} = -1000 \times 0,8 \times 0,6T$$

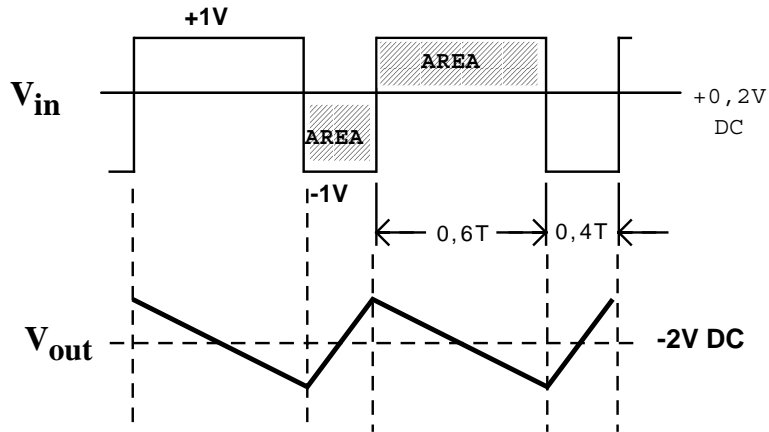Integral does not apply for 50 Hz and 100 Hz.



$\Delta V_{out} = 0,48V_{pp}$ at 1 kHz
and 48 mV_{pp} at 10 kHz

B)


$$\Delta V_{o(PP)} = -1000 \int_{t_1}^{t_2} V_{in(AC)} dt$$

$$\Delta V_{o(PP)} = -1000 \times \text{area}$$

$$= 1000 \times \frac{T}{2} \times 1V_p = \frac{1000}{2F} = 1V_{PP}$$

$$F = \frac{500 \text{ Hz}}{2}$$

F > 159 Hz integral OK.

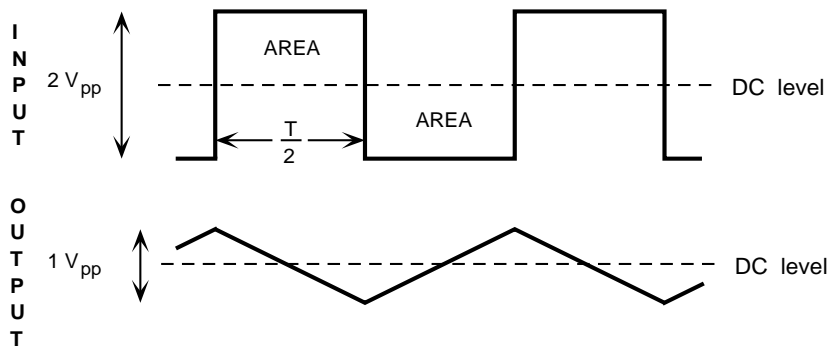

C)


$$\Delta V_{o(PP)} = -1000 \int_{t_1}^{t_2} V_{in(AC)} dt$$

$$\Delta V_{o(PP)} = -1000 \times \text{area} =$$

$$1000 \times \left(0,5 \times \frac{3T}{4}\right) = \frac{375}{F} = 1V_{PP}$$

$$F = 375 \text{ Hz}$$

F > 159 Hz integral OK.

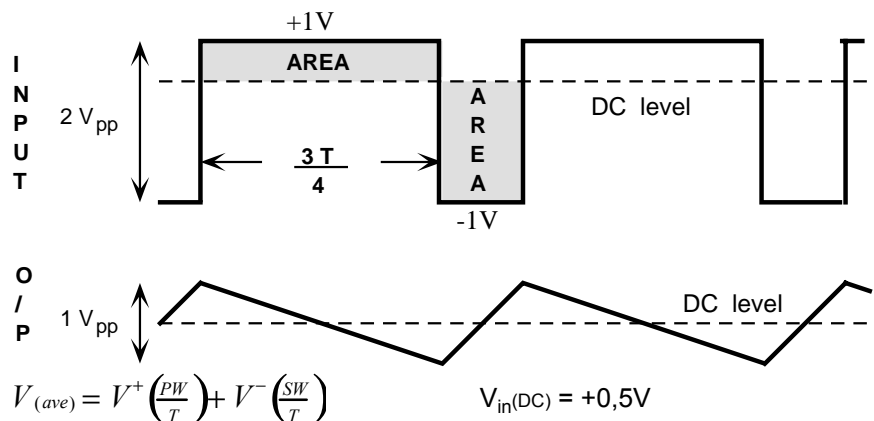

EXERCISE

IDEAL OP AMP ANALYSIS

No.3 D)


$$\Delta V_{o(PP)} = -1000 \int_{t_1}^{t_2} V_{in(AC)} dt$$

$$\Delta V_{o(PP)} = -1000 \times area$$

$$= 1000 \times \left(\frac{100\mu \times 5}{2} \right)$$

$$\Delta V_{o(PP)} = 0,25V_{PP}$$

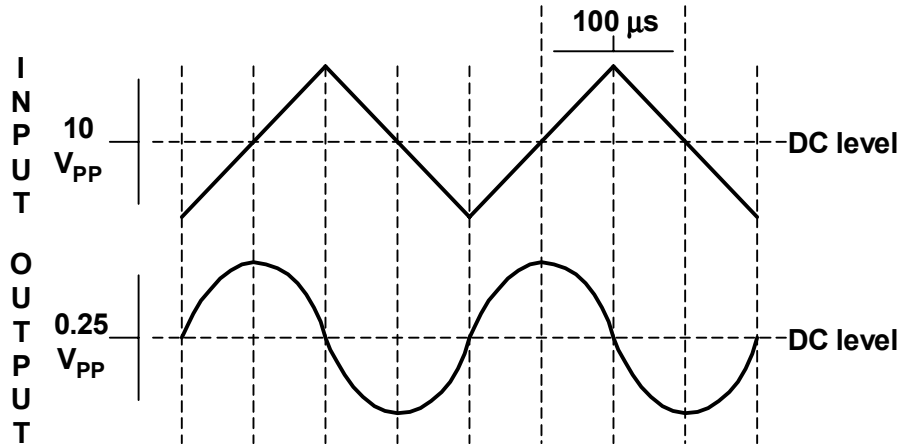O/P is a parabolic wave, not a sine wave.




No.4 A)

$$V_o = -R_F C_E \frac{dV_{in}}{dt}$$

$$V_o = -10K \times 0,1\mu \left(\pm \frac{10V}{2ms} \right)$$

$$V_o = \mp 5V_P$$

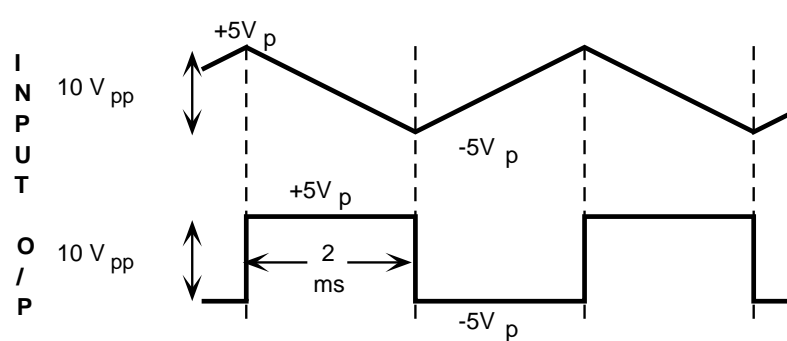

B) On edges we have:


$$V_o = -10K \times 0,1\mu (\pm \infty)$$

$$V_o = \mp \infty \Rightarrow \mp V_{sat}$$

On flat portions we have:

$$V_o = -10K \times 0,1\mu (\pm 0)$$

$$V_o = 0$$

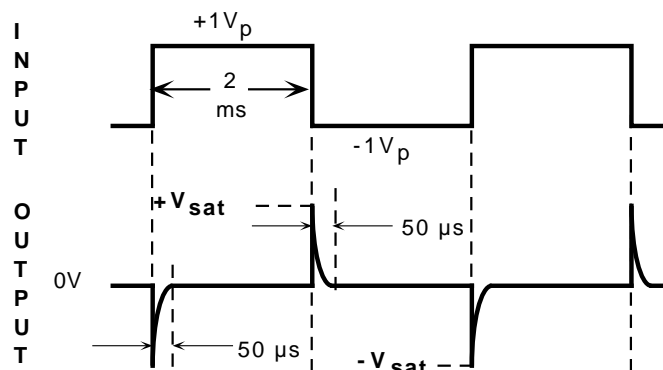

The O/P spikes settle down in $5\tau = 5R_E C_E = 50 \mu s$

C) To stabilise negative feedback in order to avoid self oscillations from the circuit.

No. 5 Phase shifter $P_1 = 0 \quad \Phi = 2 \times ATAN \left(\frac{X_C}{0} \right) = 180^\circ$

$$\Phi = 20^\circ = 2 \times ATAN \left(\frac{X_C}{P_1} \right) \Rightarrow 10^\circ = ATAN \left(\frac{X_C}{P_1} \right) \Rightarrow TAN(10^\circ) = \frac{X_C}{P_1} = \frac{1}{2\pi F C P_1}$$

$$P_1 = \frac{1}{2\pi F C \times TAN(10^\circ)} = \frac{1}{2\pi 1000 \times 100k \times TAN(10^\circ)} = 9.026 nF \Rightarrow 9.1 nF \text{ std}$$

The +ve input sees 0 to 100k DC wise, average of 50k, and the -ve input sees $R_1 || R_1 = R_1/2 = 50k$
 $R_1 = 100K$. This means that O/P DC offset will not be minimized for all P_1 settings.