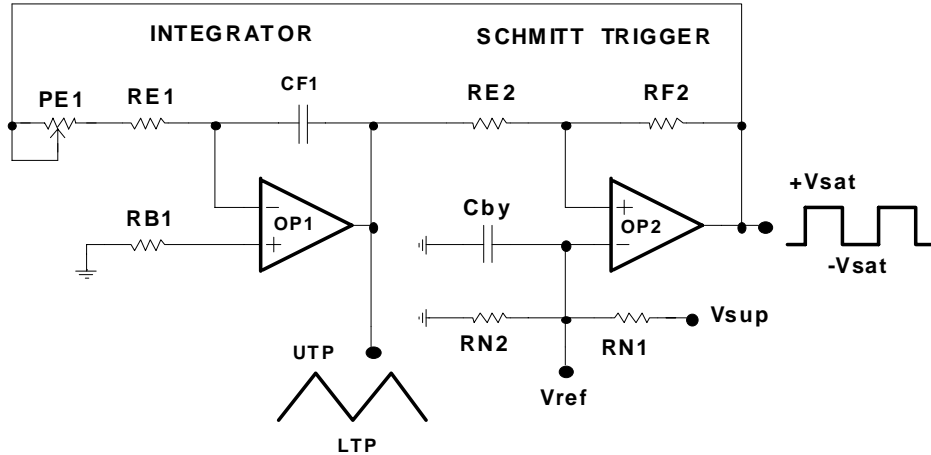



BASIC SQUARE WAVE-TRIANGULAR WAVE OSCILLATOR

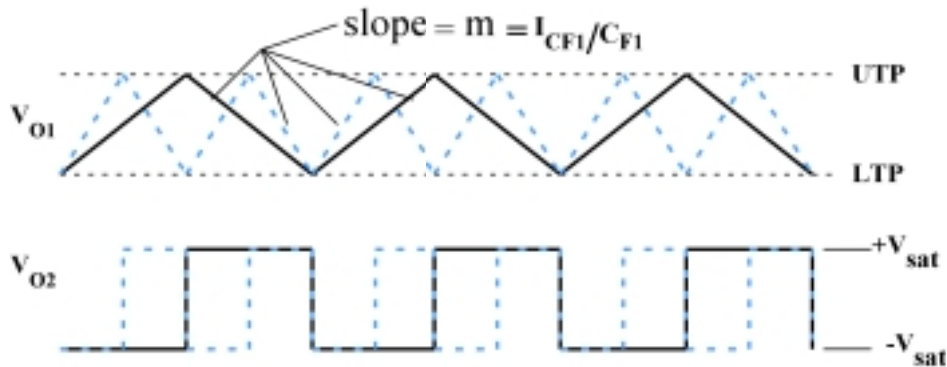1. Circuit description



The above oscillator is basically a switched integrator that outputs a triangular wave whose slopes are controlled by the charging current of C_{F1} , more specifically:


$$\frac{\Delta V_{o1}}{\Delta t} = \frac{I_{CF1}}{C_{F1}} \Rightarrow \frac{UTP - LTP}{0.5 \times T} = \frac{V_{SAT}}{(P_{E1} + R_{E1}) C_{F1}} \Rightarrow F = \frac{1}{T} = \frac{V_{SAT}}{2(UTP - LTP)(P_{E1} + R_{E1}) C_{F1}}$$




We can see on the above waveforms that if the capacitor charging current is doubled, the frequency of oscillation also doubles because the capacitor is charged twice as fast which results in a slope dV_{o1}/dt twice as large. Note here that the capacitor is charged linearly and not exponentially because the charging current is constant.

If the +ve and -ve saturation voltages are the same, only then are the +ve and -ve charging currents the same which results in a 50% duty cycle square wave.

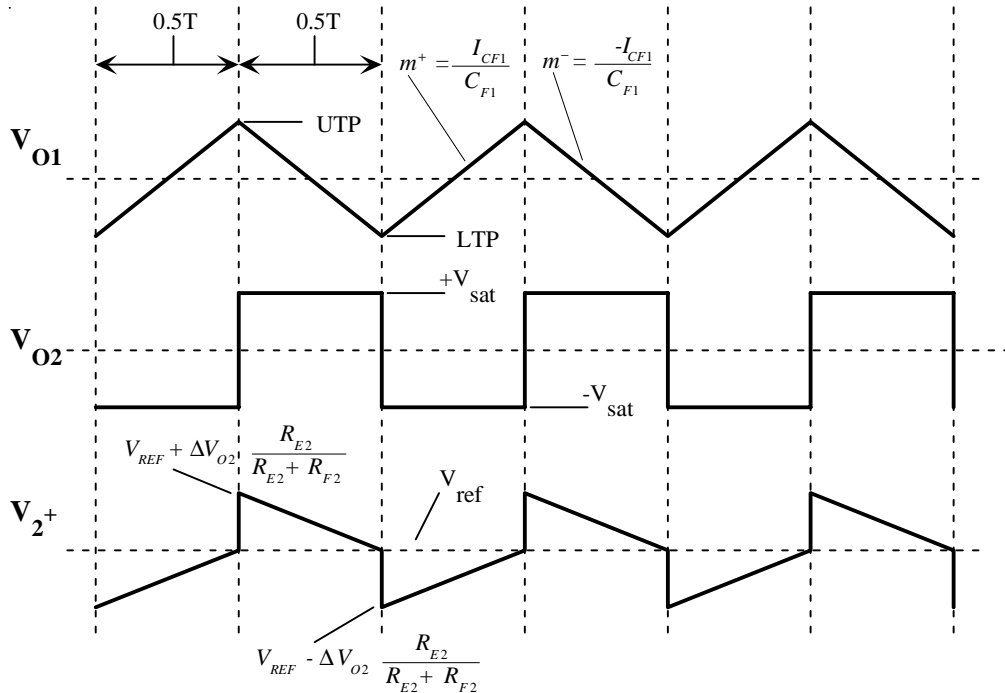UTP and LTP are the trigger voltages of the Schmitt trigger.



2. Analysis example

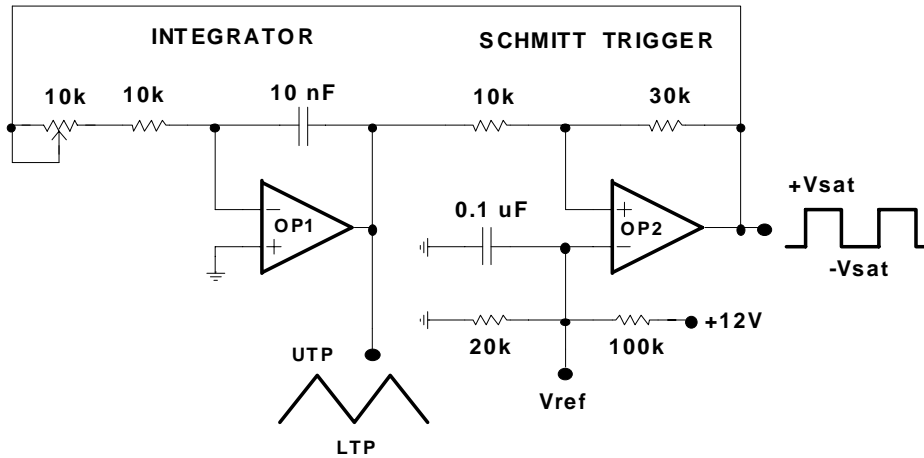



Assuming the op amps are LF347 with the following specs:

Specs for $V_{sup} = \pm 15V$	minimum	typical	maximum
O/P Voltage swing, $R_L = 10K$	$\pm 12V$	$\pm 15V$	---
I/P voltage range	$\pm 11V$	$+15V, -12V$	---

Determine the two O/P waveforms showing voltages and range of PW and SW of square wave. Assume $\pm 12V$ supply voltages and typical op amp parameters.

Analysis of trigger points of OP2:

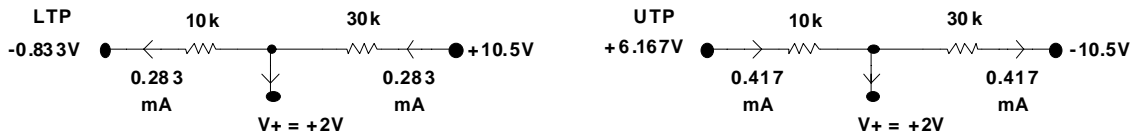

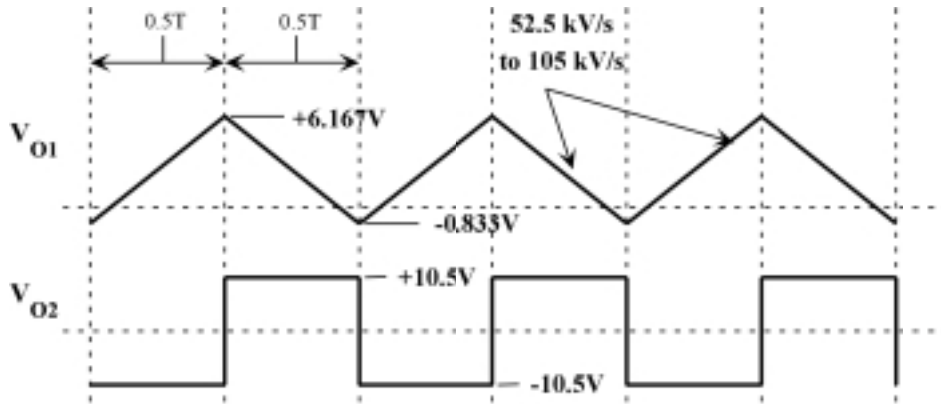

$$\frac{I_C}{C_F} = \frac{\Delta V_{O1}}{\Delta t} \Rightarrow \Delta t = \frac{T}{2} = C_F \times \frac{\Delta V_{O1}}{I_C} = 10n \times \frac{6.166 - (-0.833)}{10.5} = 66.66 \mu s \rightarrow 133.3 \mu s$$

$10k \rightarrow 20k$


$$T = 133.3 \mu s \rightarrow 266.6 \mu s \quad F = 3.75 \text{ kHz} \rightarrow 7.5 \text{ kHz}$$

NOTE: If the +ve and -ve saturation voltages are not exactly equal, then the integrator capacitor charge and discharge currents will be different and the duty cycle will not be exactly 50%. To remedy this, one should use rail-to-rail op amps with matching +ve and -ve supply voltages provided by a dual tracking regulator.

3. Design example

Design an oscillator that meets the following specifications:

- | | |
|---------------------------------|--|
| Supply Voltages: $\pm 5V$ | Op amps: OP291 DUAL rail-to-rail I/P and O/P |
| Frequency range: 1 kHz to 5 kHz | |
| Triangular wave: $\pm 2V_P$ | Square wave: $\pm 5V_P$ with fixed 50% duty cycle and 0V-5V _P with 0% to 100% adjustable duty cycle |

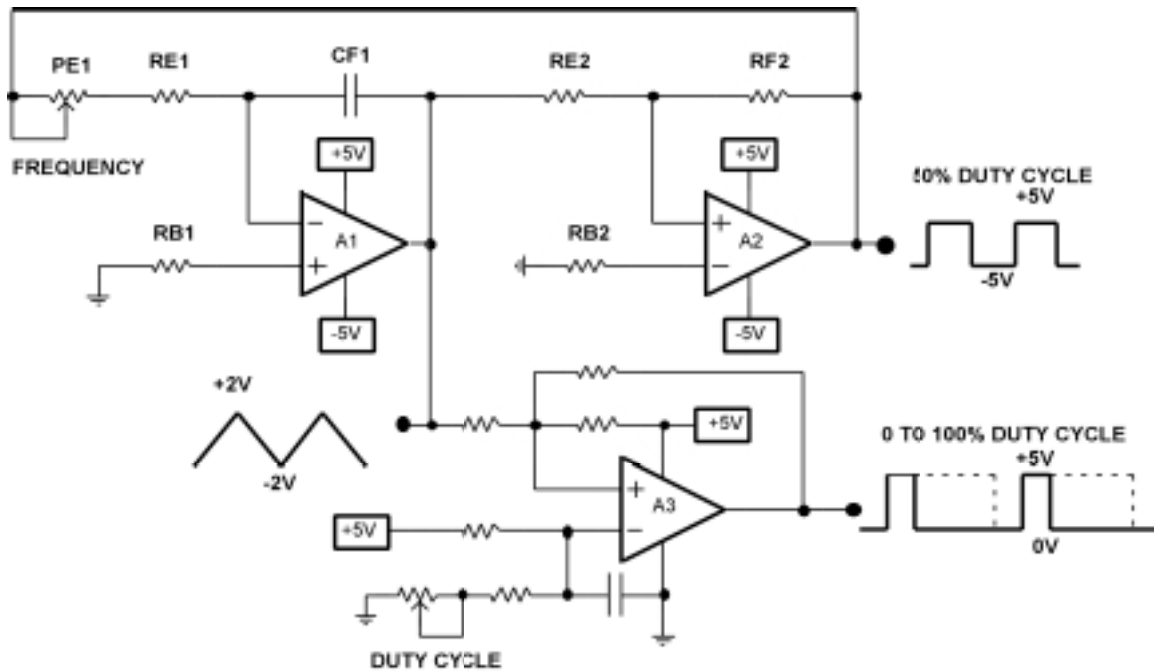

Schmitt Trigger Design


1. No pull-up resistor required

$$2. \frac{R_F}{R_E} = \frac{V_o^+ - V_o^-}{UTP - LTP} = \frac{5 - (-5)}{2 - (-2)} = 2.5 \Rightarrow R_E = 12K \text{ std and } R_F = 30K \text{ std}$$

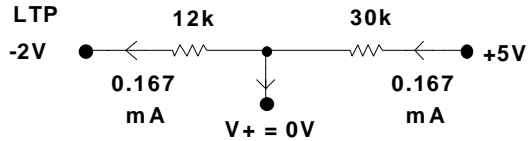3. Calculation of V_{REF}


$$V_{REF} = V^+ = 0V \text{ at triggering}$$

Therefore the -ve I/P of A2 has to be grounded.



$$4. R_{B2} = 12k \parallel 30k = 8.57k \rightarrow 8.2k \text{ std}$$

Integrator Design

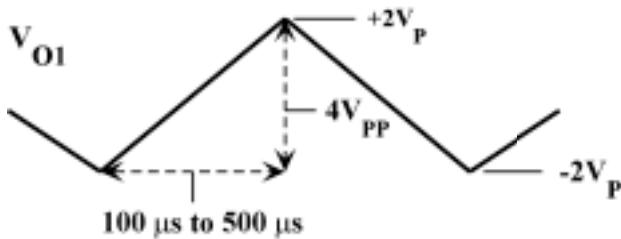

$$\frac{I_C}{C_F} = \frac{\Delta V_{O1}}{\Delta t} = \frac{2 - (-2)}{100\mu \rightarrow 500\mu}$$

$$\frac{I_C}{C_F} = 40 \text{ kV/s} \rightarrow 8 \text{ kV/s}$$

Let I_C max = 1 mA, therefore

$$C_F = \frac{1mA \rightarrow 0.2mA}{40 \text{ kV/s} \rightarrow 8 \text{ kV/s}} = 25 \text{ nF}$$

$$\text{Let } C_F = 22 \text{ nF} \Rightarrow I_C = C_F \times \frac{\Delta V_{O1}}{\Delta t} = 22n \times (40k \rightarrow 8k) = 0.88 \text{ mA} \rightarrow 0.176 \text{ mA}$$

$$P_{E1} + R_{E1} = \frac{5V}{0.88 \text{ mA} \rightarrow 0.176 \text{ mA}} = 5682 \rightarrow 28409 \quad \text{Let } R_{E1} = 5.6K \text{ std}$$

$$P_{E1} = 28409 - 5600 = 22.81k \quad \text{closest std pot value above is } 50K, \text{ therefore}$$


$$\frac{1}{50k} + \frac{1}{R_{par}} = \frac{1}{22.81k} \rightarrow R_{par} = 41.94k \rightarrow 43k \text{ std}$$

$$P_{E1} + R_{E1} = 5.6k \rightarrow 28.72k \quad (P_{E1} + R_{E1})_{ave} = R_{B1} = 17.16k \rightarrow 18k \text{ std}$$


Standard pots available: 1k, 2k, 5k, 10k, 20k, 50k, 100k, 200k, 500k

Level Detector Design

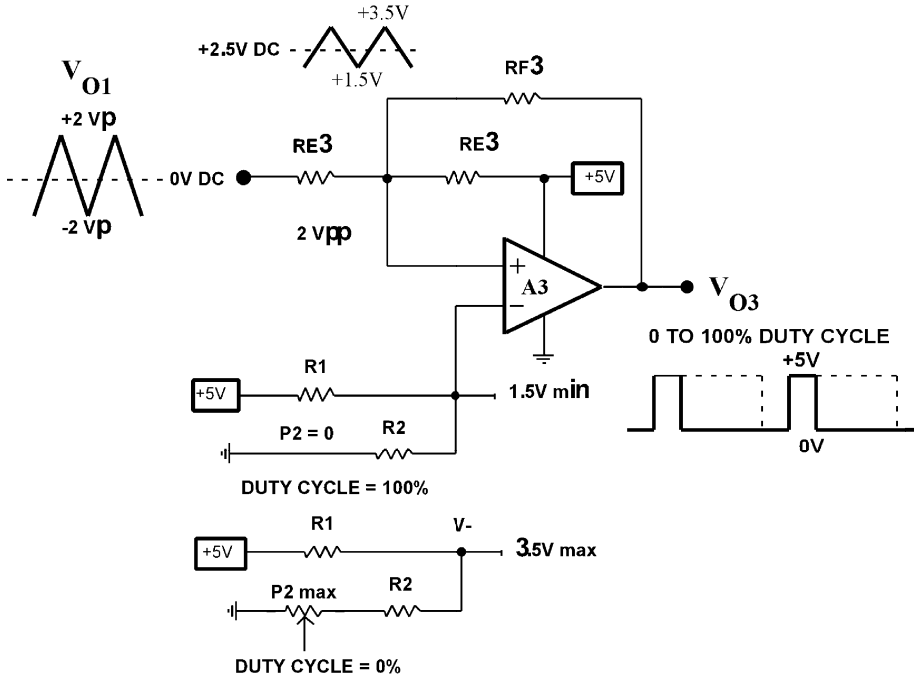A3 is powered with +5V only to obtain 0V and +5V levels at the O/P, therefore we cannot apply the triangular wave directly to the I/P of A3. The two R_{E3} resistors will attenuate the triang. wave by 50% and will also pull it up to +2.5V average. R_{F3} provides a little DC hysteresis to prevent O/P chattering of A3. Let the hysteresis be 20 mV.



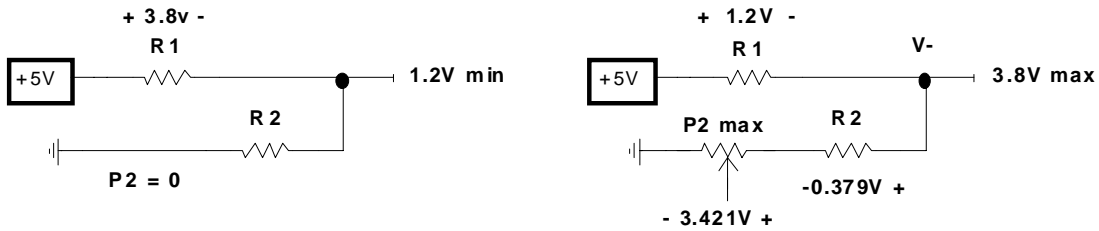To be safe and ensure that 0% to 100% range is covered, let V_3^- range from 1.2V to 3.8V.



$$\frac{P_2}{R_1} = \frac{3.8}{1.2} = 3.16\bar{6}$$

$$\frac{P_2}{R_1} = \frac{3.421}{1.2} = 2.85$$

P_2	$R_1=P_2/2.85$	R_1 std	$R_2=R_1/3.166$	R_2 std	V_{min}	V_{max}
10000	3509	3600	1137	1100	1.170	3.776
10000	3509	3600	1137	1200	1.250	3.784
10000	3509	3300	1042	1000	1.163	3.846
10000	3509	3300	1042	1100	1.250	3.854


Assuming mid-range setting of pot for balancing I/P resistance of A3 (for min O/P offset voltage), we have

$$R_N = 3.3K \parallel (1000 + 0 \rightarrow 10K) = 767 \rightarrow 2538 \quad R_{N\text{ave}} = 1653$$

$$R_P = R_{E3} \parallel R_{E3} \parallel R_{F3} \approx R_{E3} \parallel R_{E3} = 0.5 R_{E3} = 1653 \rightarrow R_{E3} = 3306 \text{ (3.3K std)}$$

$$\frac{R_{F3}}{R_{E3} \parallel R_{E3}} = \frac{V_{O3}^+ - V_{O3}^-}{UTP - LTP} = \frac{5 - 0}{20m} = 250 \Rightarrow R_{F3} = 250 \times \frac{3.3k}{2} = 412.5k \text{ (430k std)}$$

Final Circuit

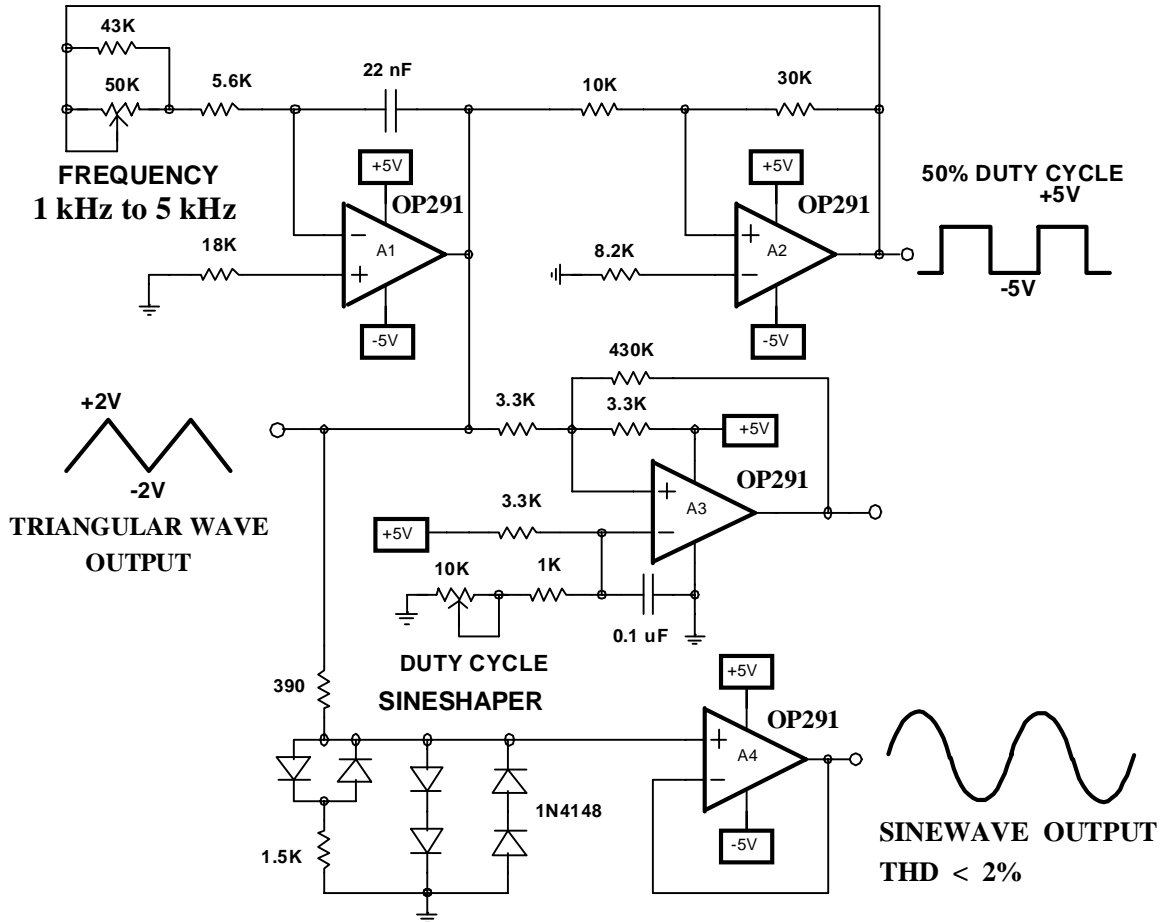

The sineshaper uses the diodes' non-linearity to distort the triangular wave into a crude sinewave that usually has less than 2% THD (total harmonic distortion) which is typical for a general purpose lab function generator but not good enough for testing audio equipment where < 0.01% THD would be required for the sinewave test signal.

To adjust the amplitude of the output waveforms, we could have a SP4T (single pole, quadruple throw) switch that selects one of the four O/P waveforms and then use a potentiometer to control the final amplitude of the selected waveform.