

NAME: SOLUTIONS 10

Determine the output voltage using ideal op amp analysis. Mark up circuit with currents, polarities, etc to show your work – no formulas allowed.

