

PROGRAMMABLE POWER SUPPLY

PRE-LAB

Design a programmable power supply that meets the following specifications.

CASE #	Unregulated V_{in} (V)		V_o max (V)	I_{LIMIT} max (A)	5% std resistors X 10^N
	min	max	BIN1=255 _{dec}	BIN2=100 _{dec}	
1	18	22	15.3	1.5	1
2	18.5	22.5	15.81	1.45	1.1
3	19	23	16.32	1.4	1.2
4	19.5	23.5	16.83	1.35	1.3
5	20	24	17.34	1.3	1.5
6	20.5	24.5	17.85	1.25	1.6
7	21	25	18.36	1.2	1.8
8	21.5	25.5	18.87	1.15	2
9	22	26	19.38	1.1	2.2
10	22.5	26.5	19.89	1.05	2.4
11	23	27	20.4	1	2.7
12	23.5	27.5	20.91	0.95	3
13	24	28	21.42	0.9	3.3
14	24.5	28.5	21.93	0.85	3.6
15	25	29	22.44	0.8	3.9
16	25.5	29.5	22.95	0.75	4.3
17	26	30	23.46	0.7	4.7
18	26.5	30.5	23.97	0.65	5.1
19	27	31	24.48	0.6	5.6
20	27.5	31.5	24.99	0.55	6.2
21	28	32	25.5	0.5	6.8
22	28.5	32.5	26.01	0.45	7.5
23	29	33	26.52	0.4	8.2
24	29.5	33.5	27.03	0.35	9.1

Available Capacitors: 150 pF, 220 pF, 750 pF, 3.3 nF, 33 nF and 0.33 μF


CALCULATION OF CAPACITORS

Select C_1 on test for stable voltage loop - range 1nF to 0,1 μF. The smaller C_1 is, the faster the regulated output voltage will react to transient changes, but if it is too small the feedback loop risks being unstable for certain load currents.

Calculate C_8 such that $(2\pi R_8 C_8)^{-1} = BW_{SUB}$


Calculate $C_9 R_9$ such that $(2\pi R_9 C_9)^{-1} \approx 500$ Hz

 A small 0,01 to 0,1 μF cap across the load may have to be used for stability..



Use an LM317 to produce the +14V supply voltage.

T O C I R C U I T

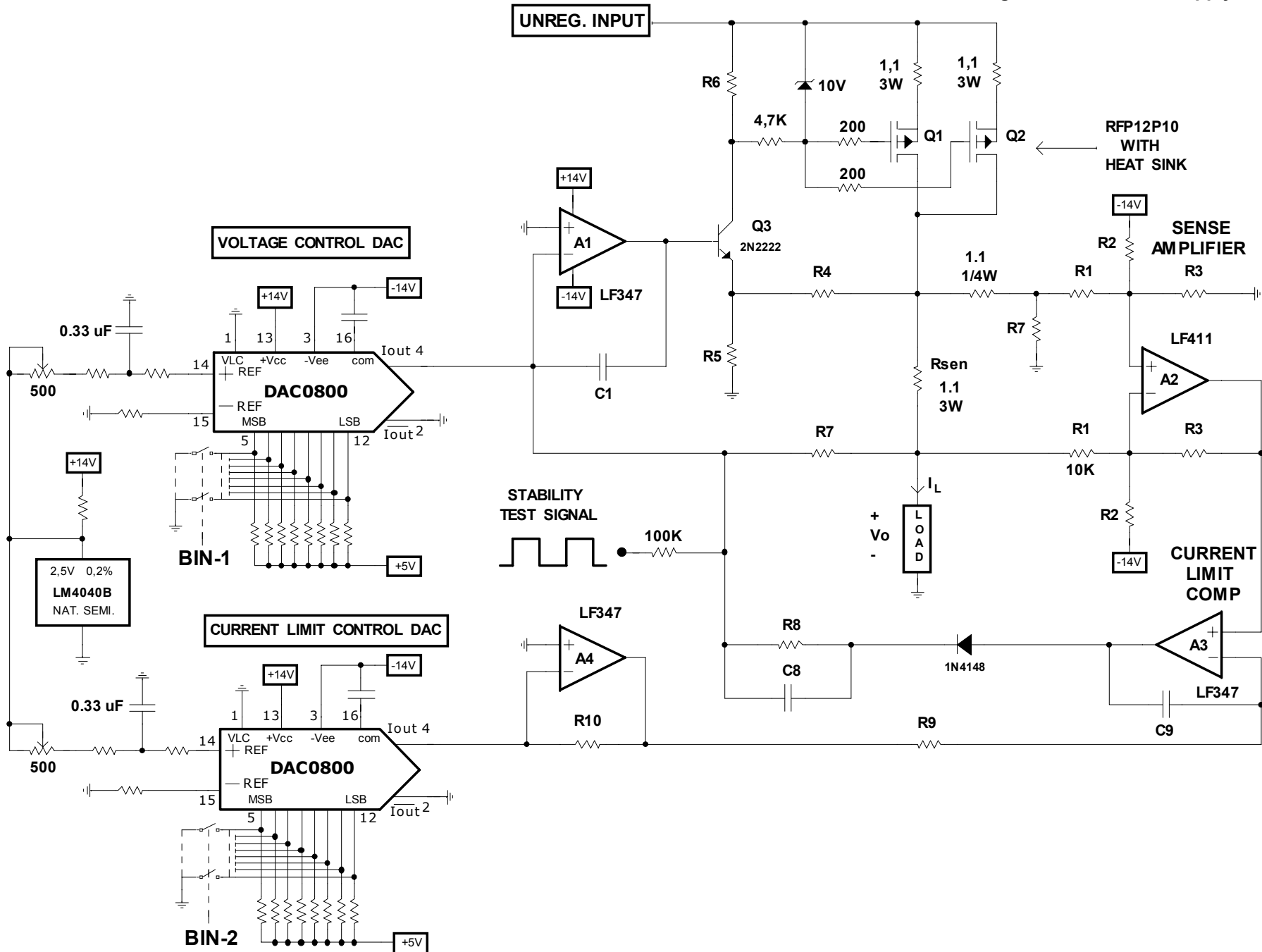

PROCEDURE

C A U T I O N

Monitor V_o all the time on the scope to ensure that there are no oscillations – an unstable feedback loop will oscillate, change the stabilising capacitor values to stop the oscillations.

Do not operate the load at I_{Lmax} for too long because the heat sinks are marginal for the amount of power being dissipated.

Part 1 VOLTAGE-CONTROL LOOP

1. Measure the precision reference voltage and the LM317 output voltage. Check for absence of HF oscillations at LM317 output – use scope.

V_{ref}		V_{out} of LM317	
Expected	Measured	Expected	Measured

2. Calibrate the voltage control DAC for an accurate full scale voltage without any load – you may have to change one of the fixed resistors in the DAC +ref branch if the pot does not provide enough range.

$V_{FS} =$ _____ State resistor change (if any): _____

3. Stability test

Set BIN1 to 128 and verify the voltage loop stability by observing the transient response of V_o resulting from the squarewave test signal shown on the circuit diagram – use $4 V_{PP}$ and a long enough period such that the output transient waveform has time to stabilise.

Verify that loop is stable (no ringing on V_o , only exponential edges) for $I_L = 0$ to 90% of I_{Lmax}
If ringing occurs, increase C_1 until it oscillations disappear.


Measure the (10%-90%) loop rise and fall times (V_o waveform) for $I_L = 0$, $I_L = 50\%$ of I_{Lmax} and $I_L = 90\%$ of I_{Lmax} using the same test squarewave.

$I_L = 0$		$I_L = 50\%$ of I_{Lmax}		$I_L = 90\%$ of I_{Lmax}	
Rise time	Fall time	Rise time	Fall time	Rise time	Fall time


Did the loop speed change with different load currents? Explain.

Teacher demo: Record the output waveform when the loop is unstable and compare to the stable loop response.

Stable O/P waveform

 

Unstable O/P waveform

 

4. Measure all bit weights and V_{FS} without a load.

BIT	BIT WEIGHT	
	Expected	Measured
B ₀ (LSB)		
B ₁		
B ₂		
B ₃		
B ₄		
B ₅		
B ₆		
B ₇ (MSB)		

V_{FS}	
Expected	Measured

5. Measure V_{FS} no load and full load then calculate the % load regulation. To do so, set decade box R value to obtain about $I_L = 95\%$ of I_{Lmax} and then toggle decade box last knob from 0 to 100K every 3 or 4 seconds so that you don't measure drift of V_o . If % regulation is not less than 0,05%, then clean up your grounds and measure at the proper sense point (right at the top of R₇) in the circuit.

$$LOAD\ REGULATION = \frac{V_{NL} - V_{FL}}{V_{NL}} \times 100 = \underline{\hspace{2cm}} \times 100 = \underline{\hspace{2cm}}$$

6. Measure line regulation by varying the unregulated input voltage from the minimum to the maximum values you have been assigned and record the changes in V_o . Again this must be done fast so that you don't measure drift.

$$LINE\ REGULATION = \frac{\Delta V_o}{\Delta V_{in}} \times 100 = \underline{\hspace{2cm}} \times 100 = \underline{\hspace{2cm}}$$

7. With $BIN_1 = 128$ and $BIN_2=100$, measure the minimum unregulated input voltage (V_{in}) at $I_L = 0$ and at $I_L = 90\%$ of I_{Lmax} , without going into current limiting, where V_o just starts dropping. Calculate the differential dropout voltage for each load condition and explain the results.

Load condition	$I_L = 0$		$I_L = 90\%$ of I_{Lmax}	
	V_{in} min	$V_{in}-V_o$ min	V_{in} min	$V_{in}-V_o$ min
Measured value				

8. Measure V_{O1} max and V_{GS} max under a worst case scenario? Also measure V_{GS} min at no load condition – this should be close to the threshold voltage of the MOSFET.

Explain worst case scenario: _____

V_{O1} max		V_{GS} max		V_{GS} min at $I_L = 0A$	
expected	measured	expected	measured	expected	measured

Are the above results safe? _____

Part II CURRENT LIMITING CONTROL LOOP

Throughout this experiment always monitor V_o on the scope to ensure that there are no oscillations.

1. **Without a load** – that is $I_L = 0A$ - set BIN1 to 255 and then switch the MSB of BIN1 back and forth and measure the subtractor output, it should not be more than $\frac{1}{2} LSB_2$ and should not change by more than $\frac{1}{2} LSB_2$.
 If the output changed by more than $\frac{1}{2} LSB_2$ your resistors are not well matched, therefore match them better and test again. If the output changed by less than $\frac{1}{2} LSB_2$ but was more than $\frac{1}{2} LSB_2$ by itself, resistors are well matched but the DC offset of the op amp is too high, you need to insert a balancing network and re-test.

NOTE: LSB_2 refers to the resolution of DAC_2 which corresponds to the weight of LSB_2 . Voltage wise, $LSB_2 = V_{o4}$ produced by $BIN_2 = 1$.

2. Set BIN1 to 255 and the current limit to 10% of I_{Lmax} and decrease the load resistor until the circuit goes into current limiting and the voltage drops to about 50% of $V_{o,reg}$ and verify the current loop stability by observing the transient response of V_o resulting from the squarewave test signal shown on the circuit diagram – use 4 V_{PP} and a long enough period such that the output transient waveform has time to stabilise. Modify C_8 or C_9 if the transient response is not stable. Repeat the procedure for $I_{LIM} = 90\%$ of I_{Lmax}


With C_8 and C_9 values that make loop stable for both current limits, measure the O/P waveform rise and fall times for $I_{LIM} = 10\%$ of I_{Lmax} , and for $I_L = 90\%$ of I_{Lmax} using the same test squarewave.

$I_L = 10\%$ of I_{Lmax}		$I_L = 90\%$ of I_{Lmax}	
Rise time	Fall time	Rise time	Fall time


Did the loop speed change with different load currents? Explain.

Teacher demo: Record the output waveform when the loop is unstable and compare to the stable loop response.


Stable O/P waveform

 

Unstable O/P waveform

 

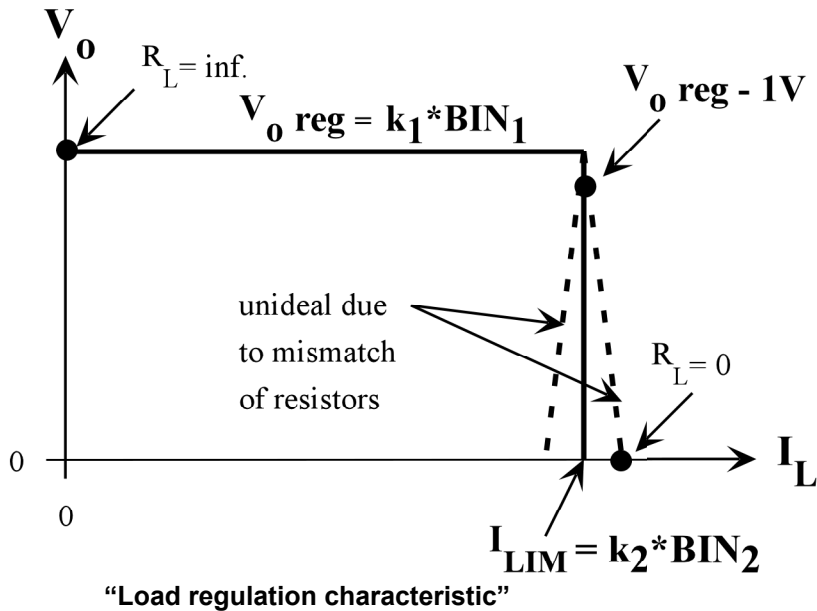4. With BIN_1 remaining at 255, measure weights of bits B_0 through B_6 of BIN_2 for $V_o = V_{o\text{ reg}} - 1V$ and $V_o=0V$ ($R_L=0$) **by decreasing R_L** until you go into current limiting. Insert a DC ammeter in series with the load to measure the actual bit weights of current limit.



BIT WEIGHTS OF BIN_2 (I_{LIMIT})			
BIT (BIN_2)	Expected (mA)	Measured at $V_{o\text{ reg}} - 1V$	Measured at $V_o = 0V$
B_0 (LSB)			
B_1			
B_2			
B_3			
B_4			
B_5			
B_6			
B_7 (MSB)	Do not measure, excessive current		

5. Measure I_{LIM} for $BIN_2 = 100_{\text{dec}}$ for $V_o = V_{o\text{ reg}} - 1V$ and $V_o=0V$ ($R_L=0$). Do not operate MOSFET's for too long at I_{Lmax} as they may overheat.

$BIN_2 = 100_{\text{dec}}$ $I_{LIM} = \underline{\hspace{2cm}}$ at $V_o = V_{o\text{ reg}} - 1V$
 $I_{LIM} = \underline{\hspace{2cm}}$ at $V_o = 0V$ or ($R_L=0$)