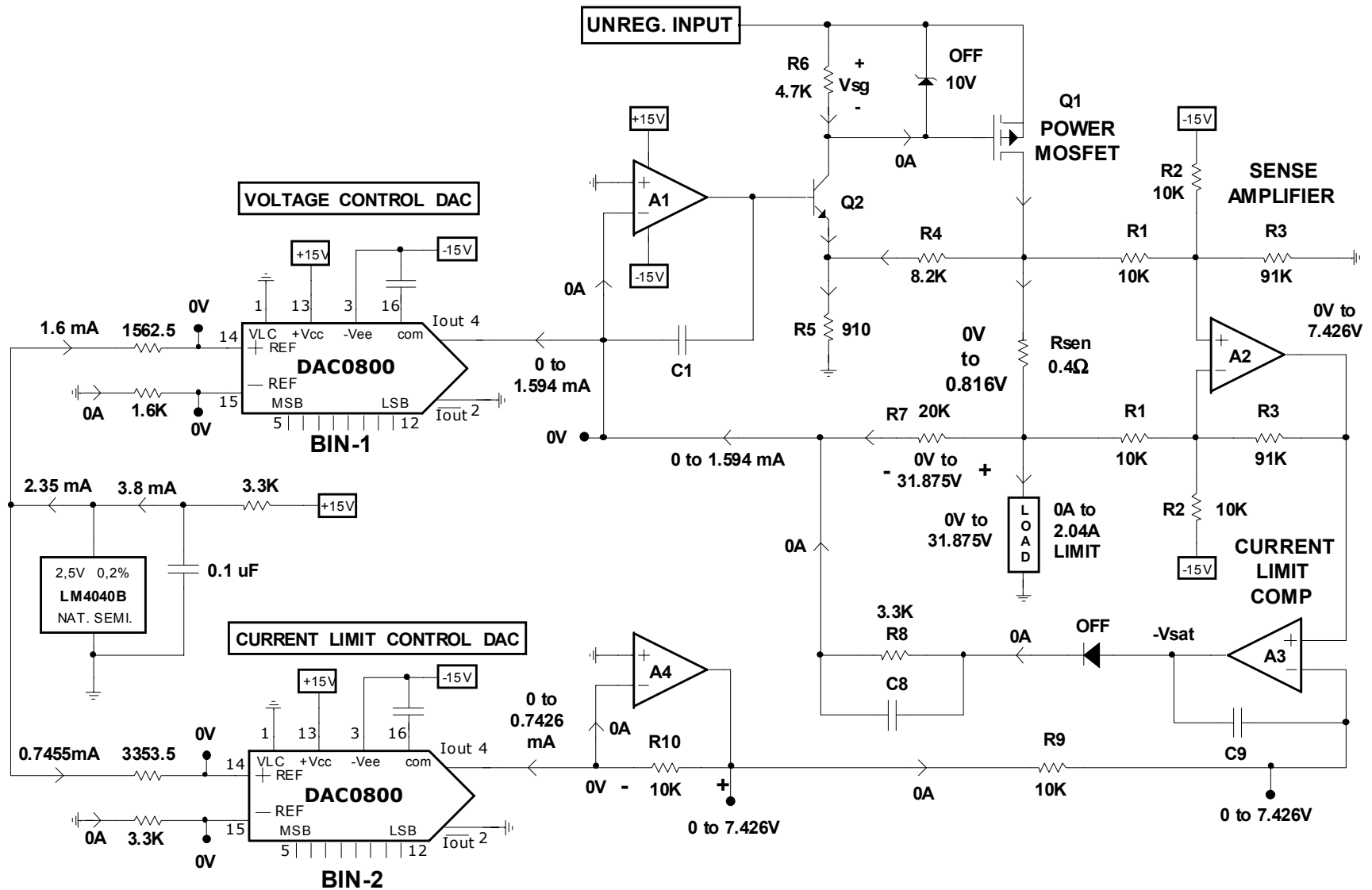


**EXAMPLE 7 PROGRAMMABLE POWER SUPPLY ANALYSIS**



**SENSE AMPLIFIER:** Amplifies sense voltage ( $I_L R_{\text{sen}}$ ) by gain  $R_3/R_1$  and produces  $V_{o2}$  that provides indication of load current.  $R_2$  does not affect gain but attenuates the high input voltages within the input voltage range of A2. Matching of  $R_1$ ,  $R_2$  and  $R_3$  resistor pairs is extremely critical to the accuracy of the current limit. Matching should be such that accuracy of  $I_{\text{limit}}$  is within  $1/2$  LSB.

**POWER MOSFET:** Provides heavy load current that op amps cannot supply. As load current increases, the small differential input of A1 increases – which means  $(V_1^+ - V_1^-)$  goes up –  $V_{o1}$  increases,  $V_{E2}$  of Q2 increases,  $I_{E3} \sim I_{C3}$  also increases, which ultimately increases  $V_{SG1} = I_{C3} R_6$  and tells the MOSFET to increase its drain and source currents thereby supplying the load current.

$R_4 - R_5$  : attenuates voltage  $V_{D1} = V_{\text{out}} + I_L R_{\text{sen}}$  to a low enough level such that  $V_{o1} = V_{E2} + 0.7$  does not saturate the output of A1 under worst case




conditions.  $V_{E2} = V_{D1} \frac{R_5}{R_4 + R_5} + I_{E2} (R_4 \parallel R_5)$  where  $I_{E2} = V_{SG1}/R_6$ .  $V_{E2}$  will be maximum when  $V_{D1}$  is maximum and  $I_{E2}$  is also maximum. This will occur at  $V_{\text{out max}}$  and  $I_L \text{ max}$ .  $V_{SG1 \text{ max}}$  can be obtained from the MOSFET characteristics ( $I_D$  versus  $V_{GS}$ ).

**CURRENT LIMIT:** Normally there is no current limiting if there is no overload. An overload condition can be detected by A3 which acts as a voltage comparator looking at  $V_3^+ = V_{o2} = I_L R_{\text{sen}} A_{\text{sen}}$  and  $V_3^- = V_{o4} = V_{\text{DAC2}}$ . As long as  $V_3^+ < V_3^-$ ,  $V_{o3}$  goes into –ve saturation and turns off the diode which keeps the current limit loop open and ineffective. As soon as  $V_3^+$  exceeds  $V_3^-$ ,  $V_{o3}$  goes +ve and turns the diode on which closes the current limit feedback loop and will now force  $V_3^-$  to equal  $V_3^+$  and will therefore force  $V_{o2} = I_L R_{\text{sen}} A_{\text{sen}}$  to equal  $V_{o4} = I_{\text{DAC2}} * R_{10}$ . Therefore  $I_L$  will be limited because of –ve feedback through A3 forcing  $V_{o2}$  to equal  $V_{\text{DAC2}} = V_{o4}$ .

**STABILITY OF FEEDBACK LOOPS:**  $C_1$ ,  $C_8$  and  $C_9$  are critical to the stability of the many feedback loops and will dictate the response time of the power supply to sudden changes in load current and voltage.

**EXAMPLE-8 DESIGN OF PROGRAMMABLE POWER SUPPLY**

**MOSFET CHARACTERISTICS**

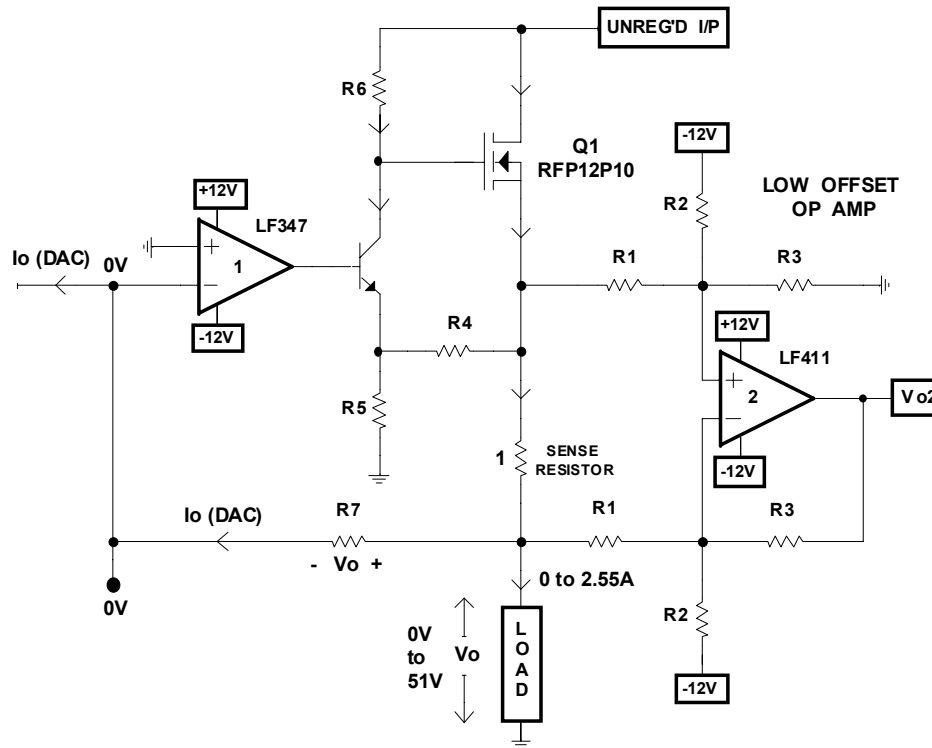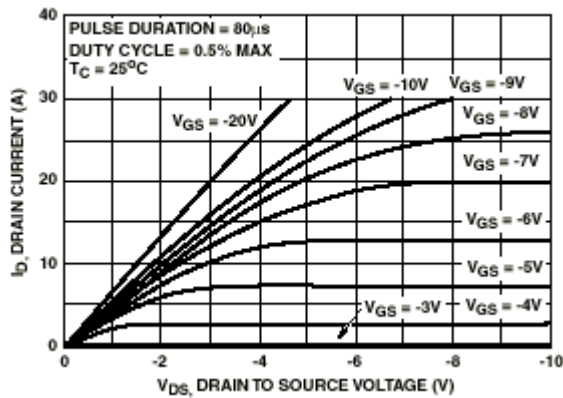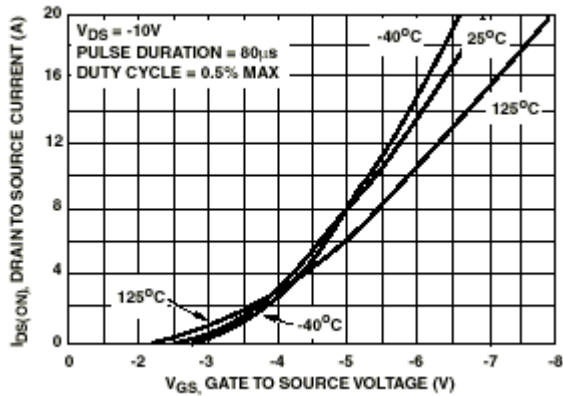

**GENERAL SPECIFICATIONS:**  $V_o = 0$  to 51V, BIN1 = 0 to 255,  $\Delta V_o = 0,2V$ ,  $I_{LIMIT} = 0$  to 2.55A, BIN2 = 0 to 255,  $\Delta I_L = 10$  mA

LF347 DATA ( $V_{SUP} = \pm 15V$ )				RFP10P12 DATA			
	MIN	TYP	MAX		MIN	TYP	MAX
$V_{out}$ swing	$\pm 12V$	$\pm 13,5V$		$V_{(TH)}$ at 1 mA	-2V		-4V
$V_{in}$ range	$\pm 11V$	+15V, -12V		$V_{GS}$ (MAX)			$\pm 20V$
$V_{io}$ @ 25°C		5 mV	10 mV	$V_{DS}$ (MAX)			-120V
LF411 DATA ( $V_{SUP} = \pm 15V$ )				$R_{ON}, V_{GS} = -10V$		0,5Ω	
$V_{out}$ swing	$\pm 12V$	$\pm 13,5V$		$C_{iss}, V_{DS} = -25V$		1,7 nF	
$V_{in}$ range	$\pm 11V$	+14.5V, -11.5V					
$V_{io}$ @ 25°C		0.8 mV	2 mV				

DESIGN EXAMPLE-9 DIGITAL CONTROL OF AC AND DC COMPONENTS

AC AMPLITUDE CONTROL DAC

