

16

Determine the range of V_o and the resolution in mV. Also determine the range of the current limit and the resolution in mA. Show all your work directly on the circuit diagram.

QUIZ #2 $V_o = 0 \rightarrow 28.73V$ $\Delta V_o = 112.6mV$
 $I_{Limit} = 0 \rightarrow 3.455A$ $\Delta I = 13.55mA$

QUIZ #3 $V_o = 0 \rightarrow 24.9V$ $\Delta V_o = 97.656mV$
 $I_{Limit} = 0 \rightarrow 4.207A$ $\Delta I = 16.489mA$

6

10

