


NAME: SOLUTIONS

QUIZ #2

$V_A = 0 \rightarrow 8.6955V$
 $\Delta V_A = 8.5mV$
 $I_x = 0.374mA$
 $m = 1700V/p$

QUIZ #3

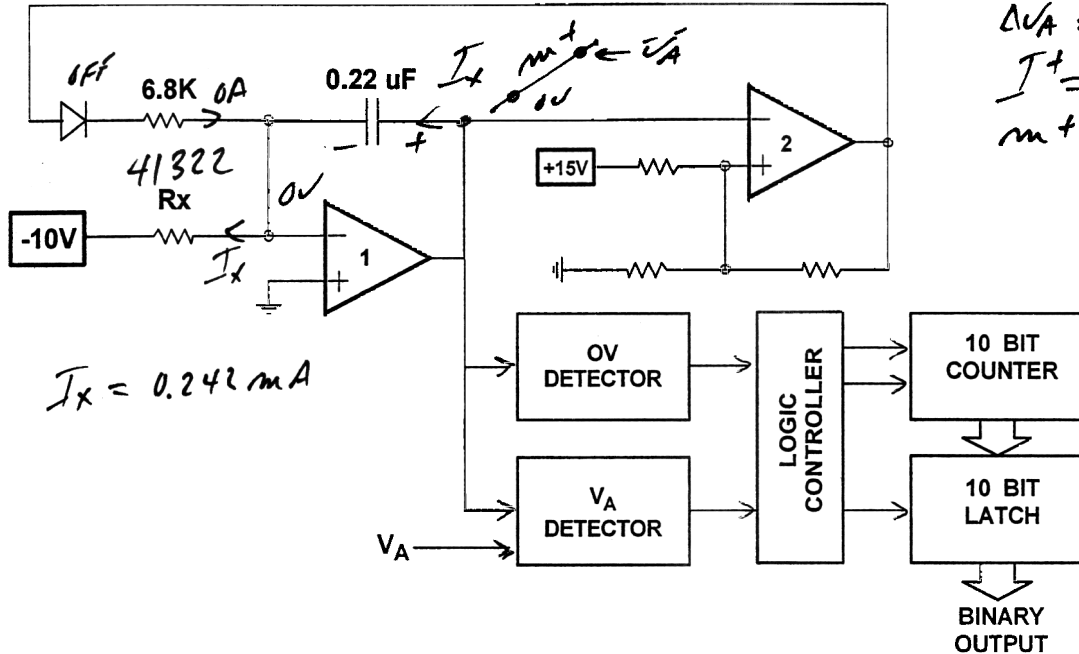
$I_x = 0.506mA$
 $m = 2300V/p$
 $V_A = 0 \rightarrow +11.765V$
 $\Delta V_A = 11.5mV$



$I_x = 0.242mA$

Assume $R_x = 41322$ and $V_{sat} = \pm 14V$ for op amps and $F_{CLK} = 200 kHz$ for counter.

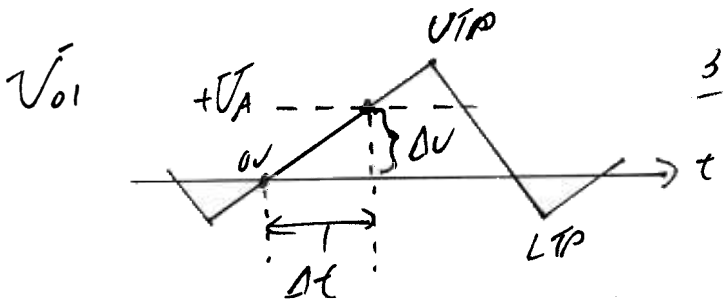- 9) A) Draw the waveform V_{o1} of op amp 1 and explain how this A to D converter works and derive the basic conversion equation $BIN = \frac{V_A \times F_{clk}}{m}$



V_A crossing counter starts.
 V_A crossing counter stops
 and count is binary
 conversion desired.

$\frac{\Delta V}{\Delta t} = \frac{V_A - 0}{BIN \times \frac{1}{F_{clk}}}$
 $BIN = \frac{V_A}{m} \times F_{clk}$

- 7) B) What is the analog conversion range of the ADC and its resolution in mV?

$V_A = \frac{BIN \times m}{F_{clk}} = \frac{BIN}{F_{clk}} \times \frac{I_x}{C_f} = \frac{0 \rightarrow 2^{10} - 1}{200k} \times \frac{0.242mA}{0.22\mu}$

- 4) C) Explain why this ADC is less accurate than the dual slope ADC.

$BIN = \frac{V_A}{m} \times F_{clk} = \frac{V_A}{\frac{|V_{REF}|}{R_x C_f}} \times F_{clk}$
 BIN depends on accuracy of V_{REF} , F_{clk} , R_x , C_f
 in DUAL SLOPE BIN conversion is independent of F_{clk} , R_x and C_f

$V_A = 0V \rightarrow +5.6265V$
 $\Delta V_A = 5.5mV = Neg.$