
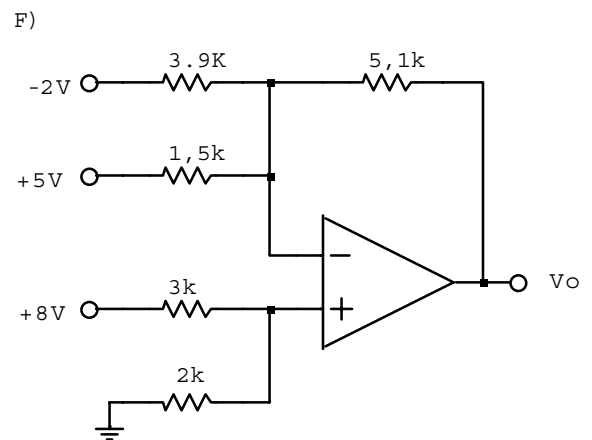
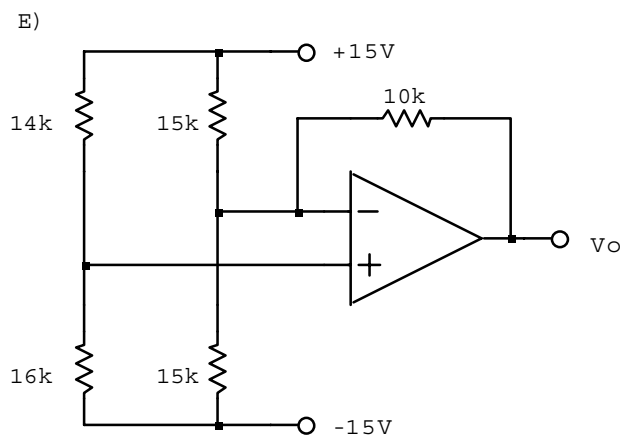
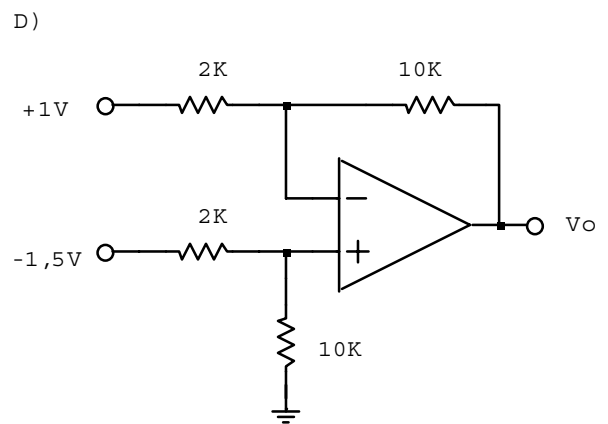
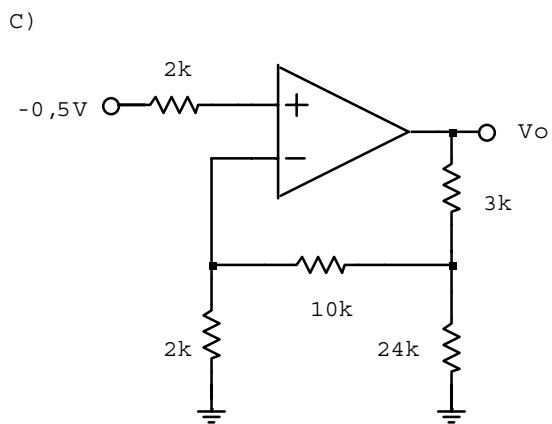
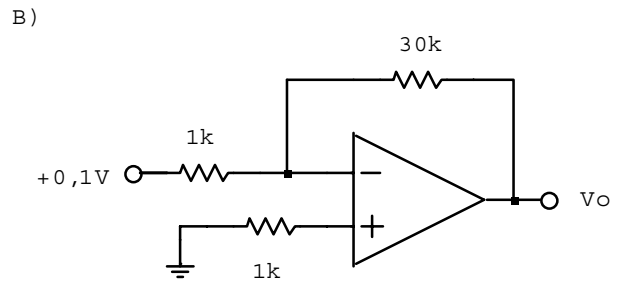


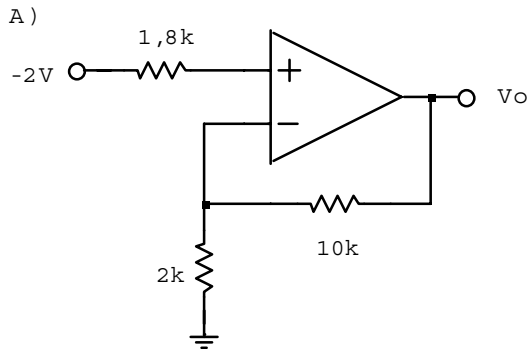**EXERCISE IDEAL OP AMP ANALYSIS**

No.1 Assuming ideal op amps, determine  $V_o$  for each and every circuit shown below.




**EXERCISE**

**IDEAL OP AMP ANALYSIS**


No.2 Assume typical op amp data for circuits A through E and worst case values for circuit F.

Op amp parameters for $V_{SUP}=\pm 15V$	minimum	typical	maximum
O/P voltage swing	$\pm 12V$	$\pm 13,5V$	-
I/P voltage range	$\pm 11V$	$\pm 12,5V$	-
Short circuit current	$\pm 12\text{ mA}$	$\pm 20\text{ mA}$	-


A) Determine  $\bar{y}$ .

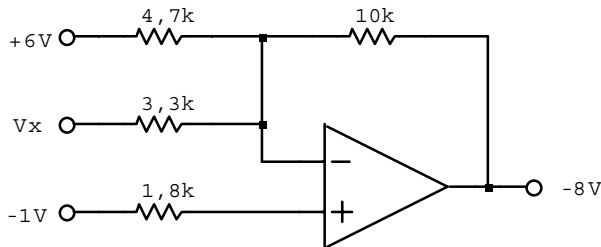


D) Determine  $\bar{y}$ .

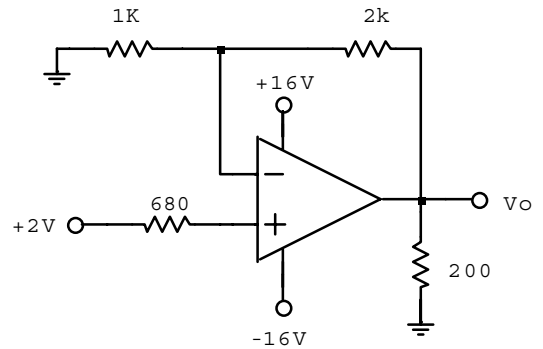

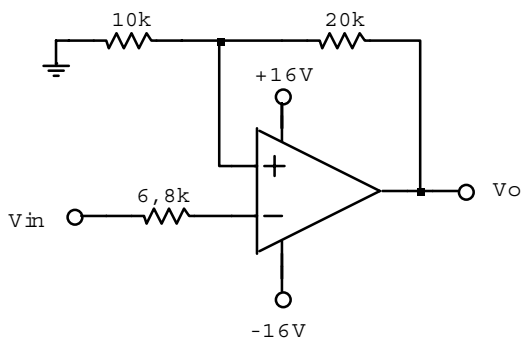
B) Determine  $\bar{y}$  for  $V_{in}=+6V$  and  $V_{in}=-6V$ .




E) Determine  $\bar{y}$ .

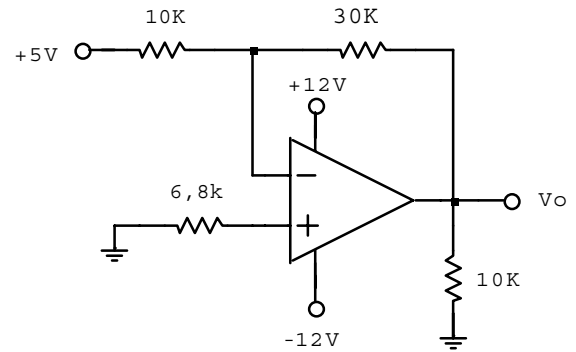

C) Determine  $\bar{y}$ .

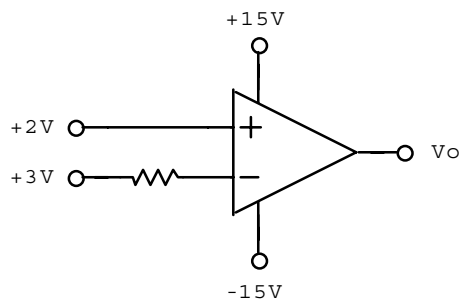

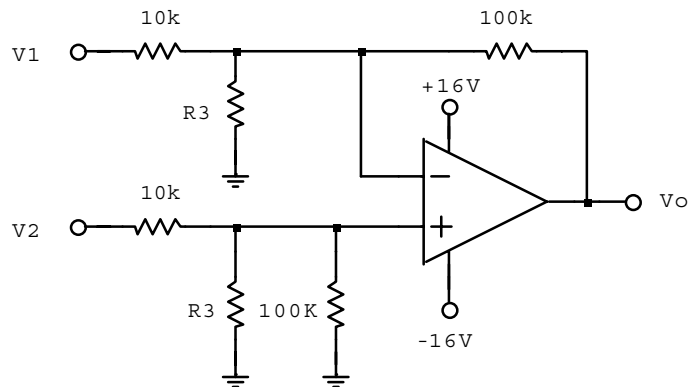F) Determine the maximum value of  $i_{IF}$  if we do not want to saturate the inputs of the op amp given and  $V_2$  range from 80V to 100V.




**EXERCISE**


**IDEAL OP AMP ANALYSIS**

No.3 Assume ideal op amps for each of the following circuits. Do not use any formulas, you must be able to derive them on your own. Mark up the circuit diagrams thoroughly for solutions.

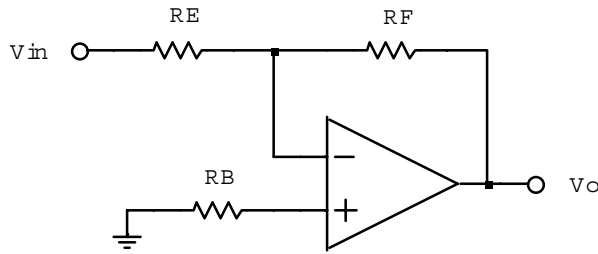
A) Determine  $B_f$ ,  $A_{v_f}$  and  $Z_{i_f}$



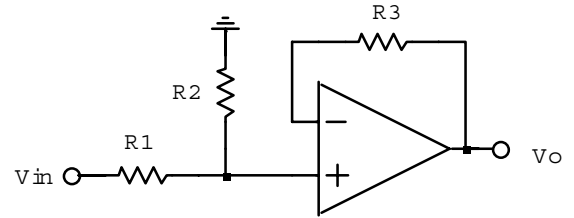
B) Determine  $B_f$ ,  $A_{v_f}$  and  $Z_{i_f}$




C) Determine  $A_{v_f}$  and  $Z_{i_f}$

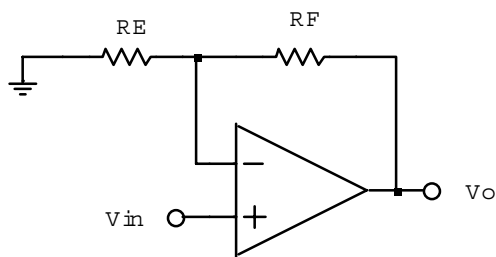

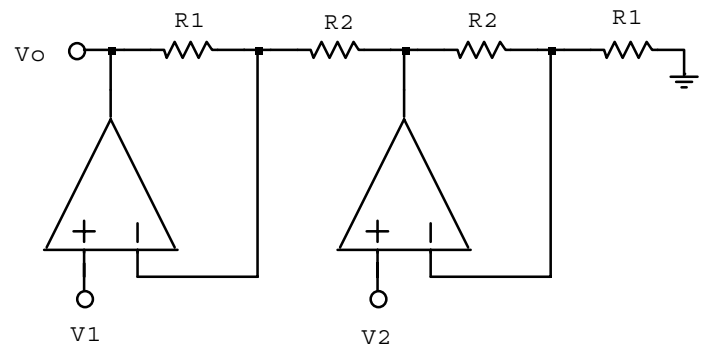
D) Determine  $\mathcal{Y}$  and  $Z_{i_f}$  seen by each I/P.



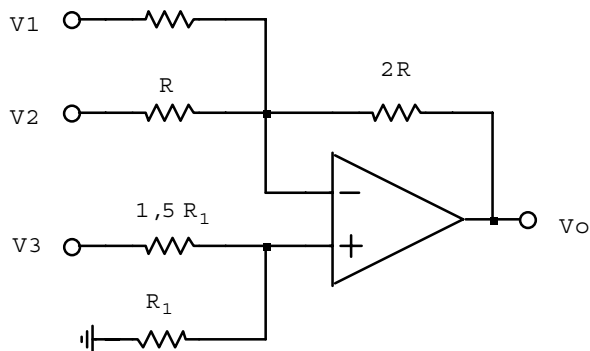E) Determine  $\mathcal{Y}$  and  $Z_{i_f}$  seen by each I/P.



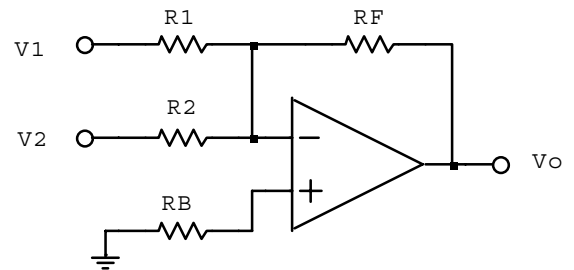F) Determine  $B_f$ ,  $\mathcal{Y}$  and  $Z_{i_f}$  seen by each I/P.



**EXERCISE**


**IDEAL OP AMP ANALYSIS**

No.4


$$\Delta V_o(PP) = V_o(t_2) - V_o(t_1) = -\left(\frac{1}{R_F C_F}\right) \int_{t_1}^{t_2} V_{in}(AC) dt$$

if  $\omega > \frac{10}{R_F C_F}$
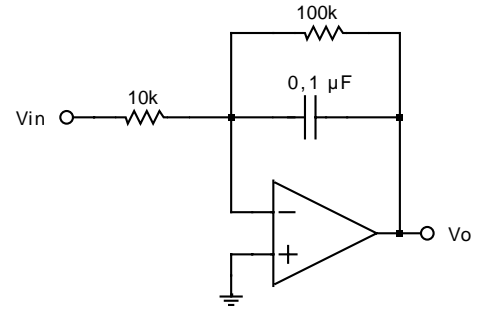
$$V_{in(ave)} = V_{in}^+ \left(\frac{PW}{T}\right) + V_{in}^- \left(\frac{SW}{T}\right) \quad \text{for a squarewave}$$



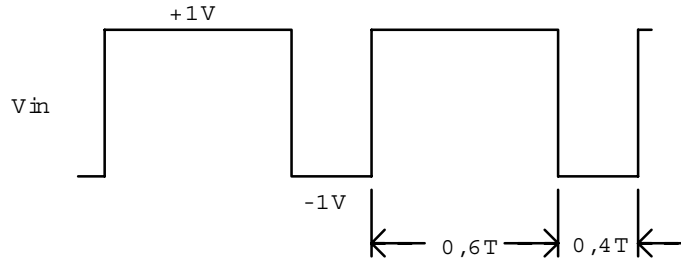A) Draw the output waveform with respect to  $V_{in}$  shown for frequencies of 50 Hz, 100 Hz, 1 kHz and 10 kHz - label waveforms with AC and DC values as well as PW and SW.



B) If  $V_{in}$  is a 2  $V_{pp}$  squarewave with a 50% duty cycle, calculate the frequency of  $V_{in}$  that will produce  $V_o = 1 V_{pp}$


C) Repeat step B for 75% duty cycle.

D) If  $V_{in}$  is a 10  $V_{pp}$  triangular wave with a frequency of 5 kHz, draw the expected O/P waveform with respect to  $V_{in}$ .



No.5 A) Determine the output waveform relative to an input triangular wave with a 10  $V_{pp}$  amplitude and a frequency of 250 Hz.

B) Determine the output waveform relative to an input square wave with a 2  $V_{pp}$  amplitude and a frequency of 250 Hz.

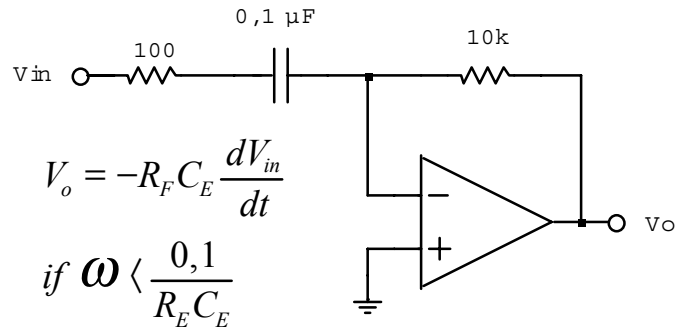C) What is the function of the 100Ω resistor?



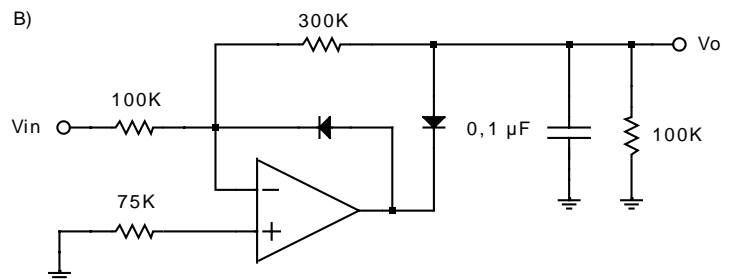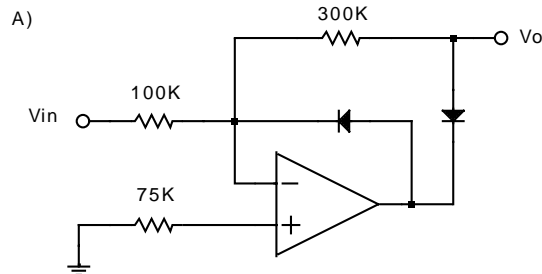No.6 Determine the O/P waveform relative to an input 2V (rms) 1 kHz sinewave for each circuit shown below.



**EXERCISE**

**IDEAL OP AMP ANALYSIS**


**No.7 PHASE SHIFTER**

Using ideal op amp analysis, prove that

$$A_{VF} = \frac{P1 + jX_C}{P1 - jX_C}$$

$$|A_{VF}| = 1$$
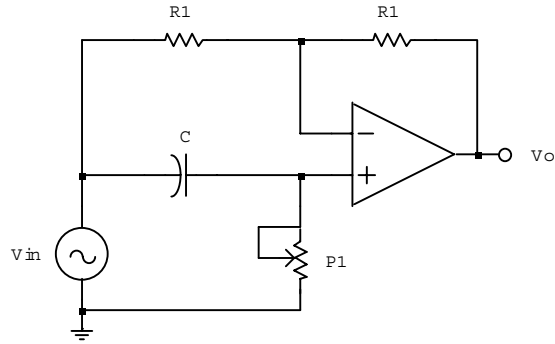
$$\angle A_{VF} = 2 \arctan \frac{X_C}{P1}$$




**No.8 PHASE SHIFTER**

Using ideal op amp analysis, prove that

$$A_{VF} = \frac{P1 + jX_C}{P1 - jX_C}$$

$$|A_{VF}| = 1$$
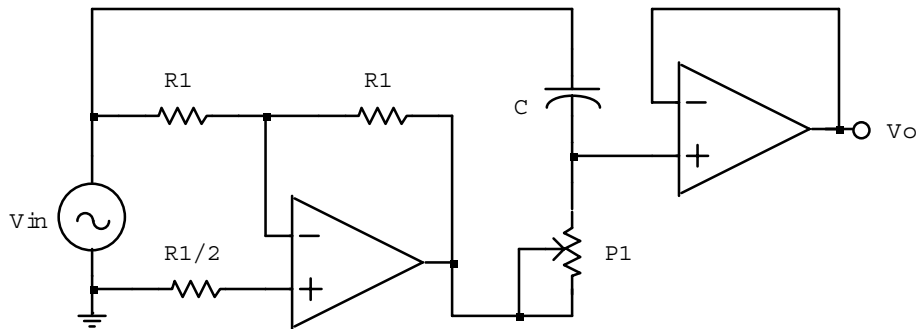
$$\angle A_{VF} = 2 \arctan \frac{X_C}{P1}$$




**No.9 Howland current source**

Prove that the load current is given by the following equation:

$$I_L = \frac{V_{in}}{R1}$$

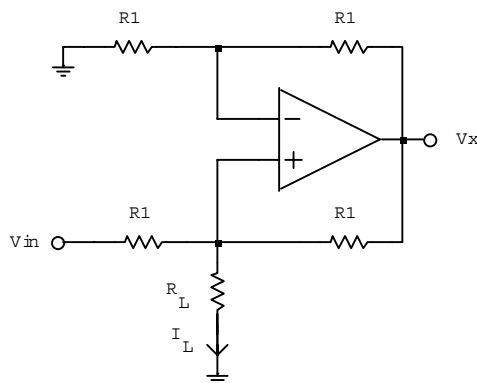
Hint: Work out currents in terms of  $V_{in}$  and unknown  $V_x$ .



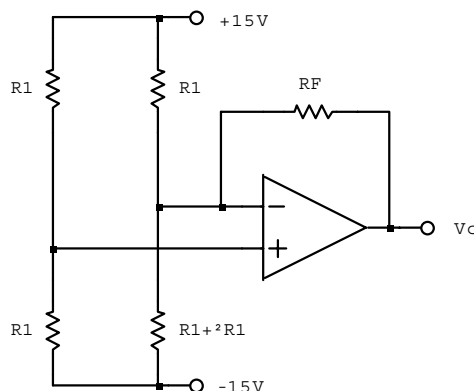**No.10 BRIDGE AMPLIFIER**

Prove that  $V_o$  is given by the following equation:

$$V_o = \frac{-15 * \Delta R_1}{R_1 (R_1 + \Delta R_1)} R_F$$




**EXERCISE**


**IDEAL OP AMP ANALYSIS**

**SOLUTIONS**


No.1A)

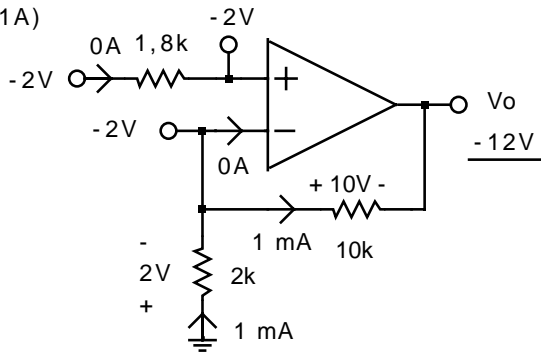


B)

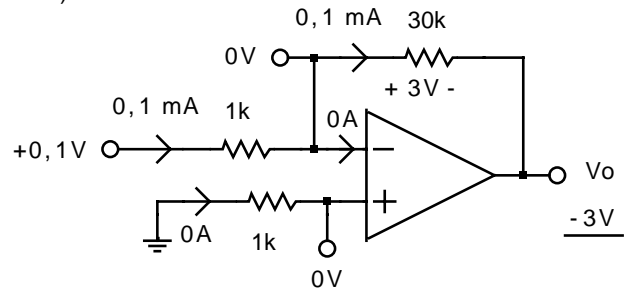


C)

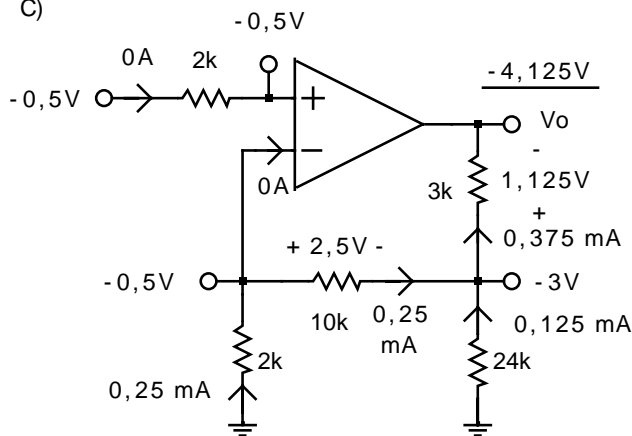


D)

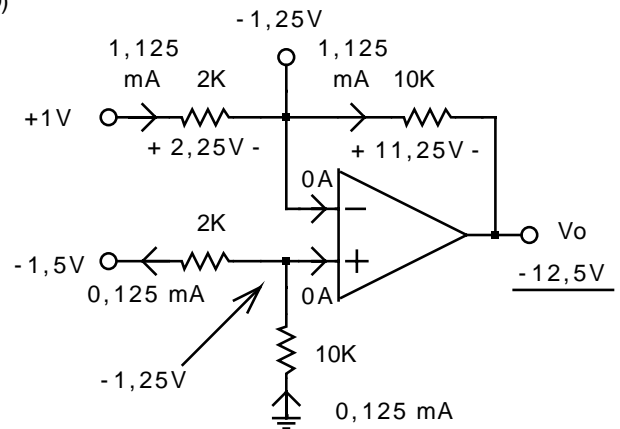

E)

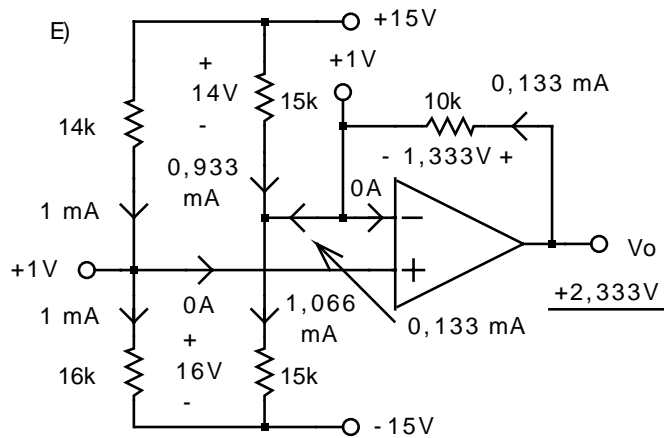


F)

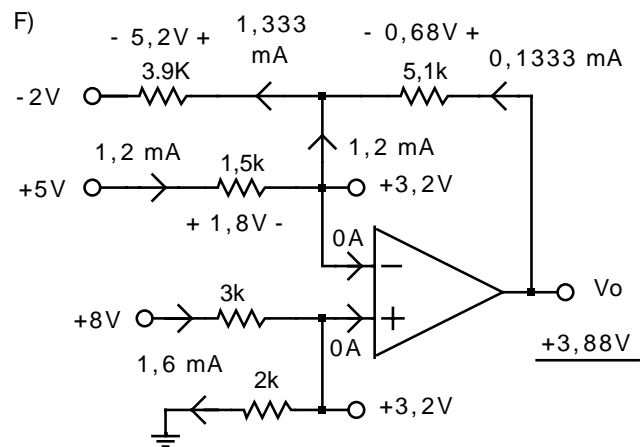


**EXERCISE**

**IDEAL OP AMP ANALYSIS**

No.2 A)

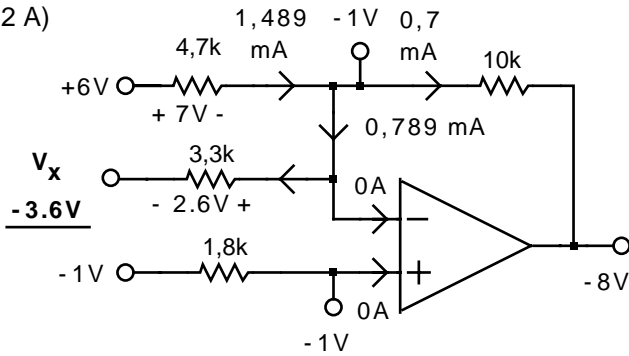

C)

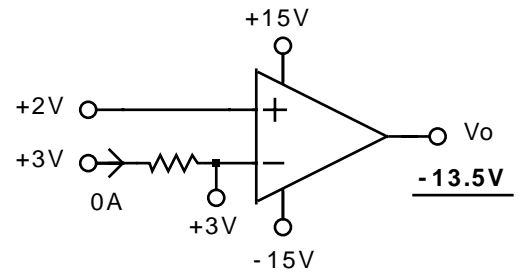


No feedback, the output saturates with a polarity determined by the sign of the differential I/P voltage:

$$V_o = A_d (V^+ - V^-) = (2-3) = -$$

$$V_o = -V_{sat} = \underline{-13.5V}$$

B)

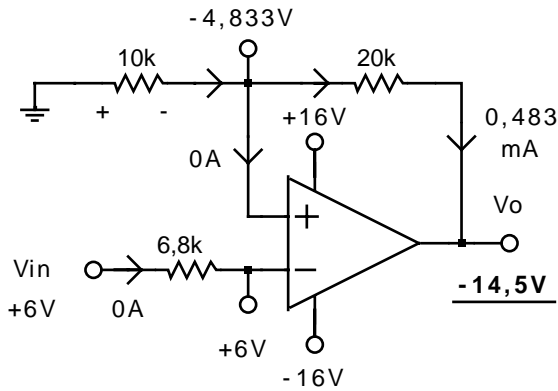


Positive feedback will make the output saturate with a polarity determined by the sign of the differential I/P voltage. With +6V applied to the -ve I/P of the op amp, the O/P should be of the opposite polarity, therefore assume

$$V_o = -V_{sat} = \underline{-14.5V}$$

and determine the  $V^+$  and verify the sign of the differential I/P voltage in order to validate your assumption of  $V_o = -V_{sat}$ , that is:

$$V_o = A_d (V^+ - V^-) = (-4.83-6) = -$$

therefore the assumption was valid.

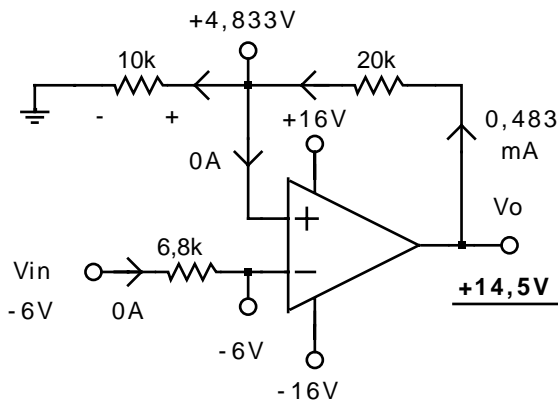

Same procedure here, except now  $V^-$  is negative, therefore the O/P polarity is expected to be positive:

$$V_o = +V_{sat} = \underline{+14.5V}$$



Verify assumption with sign of  $V_d = (V^+ - V^-)$

$$V_o = A_d (V^+ - V^-) = (+4.83-(-6)) = +$$

**EXERCISE**


**IDEAL OP AMP ANALYSIS**

2 D)

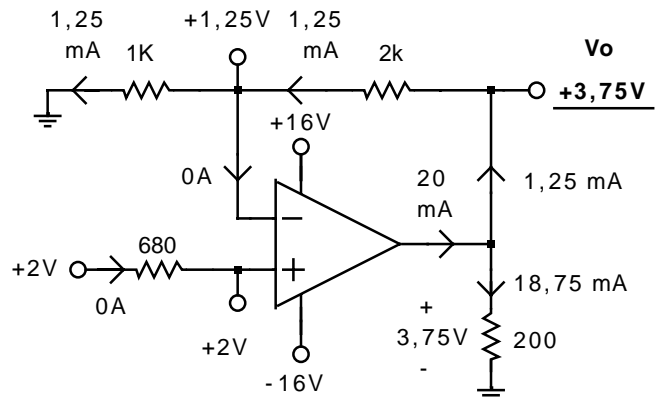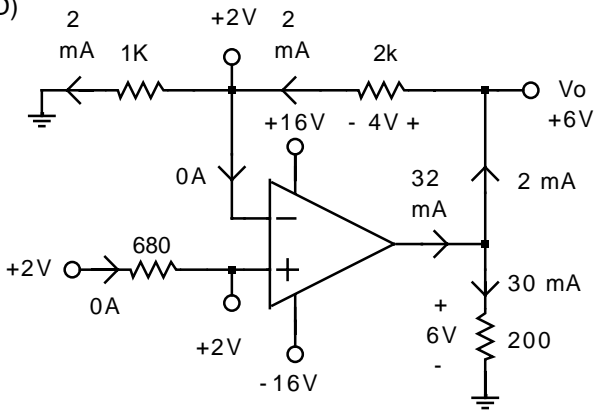


Output of op amp has reached current limit, notice that  $V^- = V^+$  and -ve feedback is rendered ineffective not forcing  $V^- = V^+$

E)

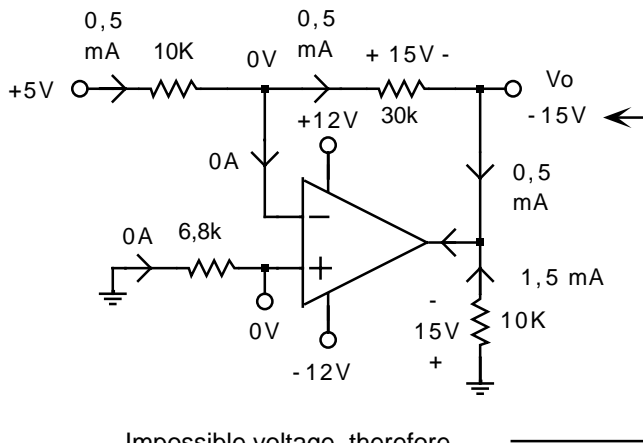


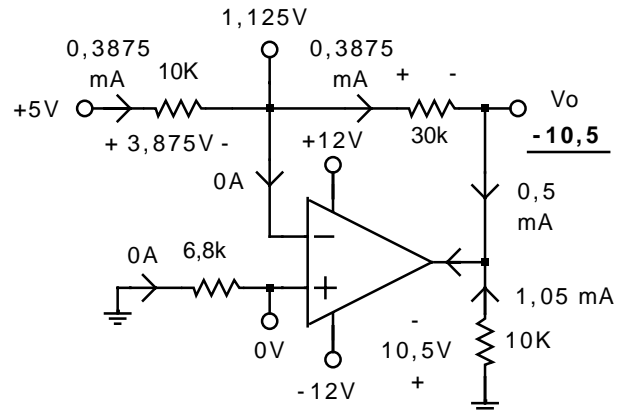Impossible voltage, therefore  $V_o = -V_{sat} = -10,5V$  typical.



Output of op amp has reached saturation, notice that  $V^- = V^+$  and -ve feedback is rendered ineffective not forcing  $V^- = V^+$

F)

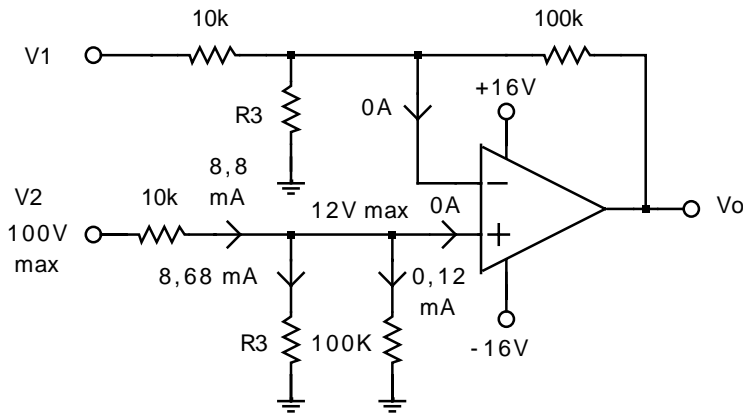

$$V^- \text{ or } V^+ \text{ max} = 16 - 4 = 12V$$


$$R_3 < 12V / 8,68 \text{ mA} = \underline{1382}$$

$R_3$  should be less than 1382

in order to keep  $V^-$  and  $V^+$  inside a safe range of  $\pm 12V$ .

EXERCISE


IDEAL OP AMP ANALYSIS

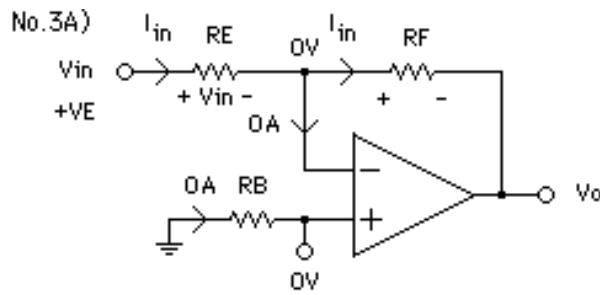

$$I_{in} = \frac{V_{in}}{R_x} \quad R_{in} = \frac{V_{in}}{I_{in}} = R_x \quad R_2 = R_x \parallel R_T$$

$$V_o = V^- - I_{in} R_T = 0 - \left( \frac{V_{in}}{R_x} \right) R_T$$

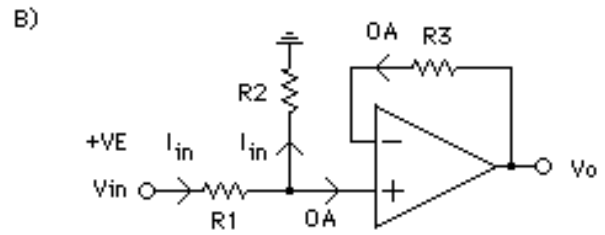
$$A_{VT} = \frac{V_o}{V_{in}} = -\frac{R_T}{R_x}$$



$$I_{in} = \frac{V_{in}}{R_1 + R_2} \quad R_{in} = \frac{V_{in}}{I_{in}} = R_1 + R_2$$

$$V_o = V^- = V^+ = I_{in} R_2 = \left( \frac{V_{in}}{R_1 + R_2} \right) R_2$$

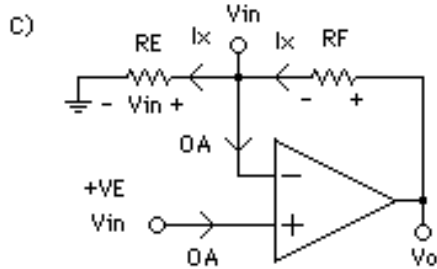
$$A_{VT} = \frac{V_o}{V_{in}} = \frac{R_2}{R_1 + R_2} \quad R_3 = R_1 \parallel R_2$$



$$I_{in} = 0 \quad R_{in} = \frac{V_{in}}{I_{in}} = \infty \quad I_x = \frac{V^-}{R_x} = \frac{V_{in}}{R_x}$$

$$V_o = V^- + I_x R_T = V_{in} + \left( \frac{V_{in}}{R_x} \right) R_T$$
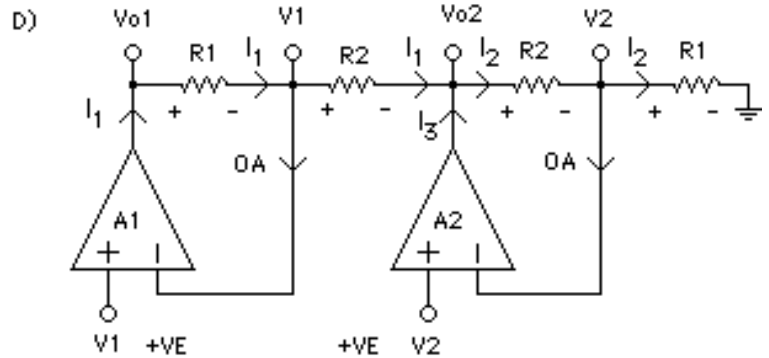
$$V_o = V_{in} \left( 1 + \frac{R_T}{R_x} \right) \Rightarrow A_{VT} = \frac{V_o}{V_{in}} = \left( 1 + \frac{R_T}{R_x} \right)$$



$$Z_{q1} = Z_{q2} = \frac{V_{in}}{0A} = \infty \quad I_2 = \frac{V_2}{R_1}$$

$$V_{o2} = V_2 + I_2 R_2 = V_2 + \left( \frac{V_2}{R_1} \right) R_2 = V_2 \left( 1 + \frac{R_2}{R_1} \right)$$

$$I_1 = \frac{V_1 - V_{o2}}{R_2} = \frac{V_1 - V_2 \left( 1 + \frac{R_2}{R_1} \right)}{R_2}$$


$$V_o = V_1 + I_1 R_1 = V_1 + \left[ V_1 - V_2 \left( 1 + \frac{R_2}{R_1} \right) \right] \left( \frac{R_1}{R_2} \right)$$

$$\text{After simplification } V_o = \left( 1 + \frac{R_1}{R_2} \right) \times (V_1 - V_2)$$

**EXERCISE**

**IDEAL OP AMP ANALYSIS**

No.3 E)

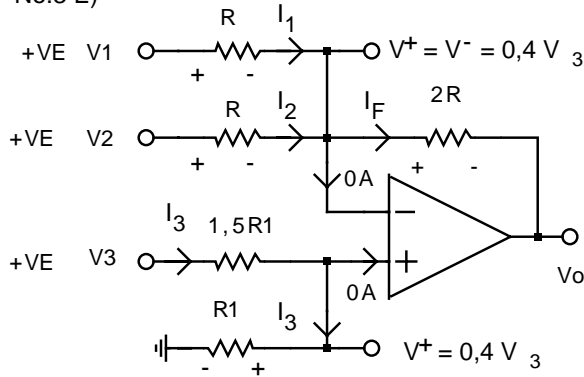

$$I_3 = \frac{V_3}{2,5R_1} \Rightarrow V^+ = V^- = I_3 R_1 = \frac{V_3}{2,5R_1} \times R_1 = 0,4V_3$$

$$Z_{if3} = \frac{V_3}{I_3} = 2,5R_1 \quad I_1 = \frac{V_1 - V^-}{R} = \frac{V_1 - 0,4V_3}{R}$$

$$I_2 = \frac{V_2 - V^-}{R} = \frac{V_2 - 0,4V_3}{R} \quad I_F = I_1 + I_2$$

$$I_F = \frac{V_1 - 0,4V_3}{R} + \frac{V_2 - 0,4V_3}{R} = \frac{V_1 + V_2 - 0,8V_3}{R}$$

$$V_o = V^- - I_F(2R) = 0,4V_3 - \left[ \frac{V_1 + V_2 - 0,8V_3}{R} \right] (2R)$$

$$V_o = 0,4V_3 - [2V_1 + 2V_2 - 1,6V_3]$$

$$V_o = 2[V_3 - V_2 - V_1]$$

$$Z_{if1} = \frac{V_1}{I_1} = \frac{V_1}{\frac{V_1 - 0,4V_3}{R}} = \frac{R}{\left(1 - \frac{0,4V_3}{V_1}\right)}$$


$$Z_{if2} = \frac{V_2}{I_2} = \frac{V_2}{\frac{V_2 - 0,4V_3}{R}} = \frac{R}{\left(1 - \frac{0,4V_3}{V_2}\right)}$$

to balance the inputs:

$$R \parallel R \parallel 2R = 0,4R = R_1 \parallel 1,5R_1 = 0,6R_1$$

$$R = 1,5R_1$$

F)

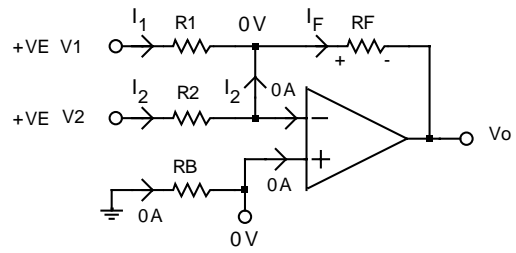

$$V_o = V^- - I_F R_F = 0 - (I_1 + I_2) R_F$$

$$V_o = -\left(\frac{V_1}{R_1} + \frac{V_2}{R_2}\right) R_F$$

$$V_o = -\left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2\right)$$

$$Z_{if1} = \frac{V_1}{I_1} = R_1 \quad Z_{if2} = \frac{V_2}{I_2} = R_2$$

$$R_B = R_1 \parallel R_2 \text{ to balance inputs}$$

N0.3 E)

$Z_{if1}$  and  $Z_{if2}$  are not constant, but will vary as  $V_3$  changes. On the other hand,  $Z_{if3}$  is fixed and does not affect either  $V_1$  or  $V_2$ .

**EXERCISE**

**IDEAL OP AMP ANALYSIS**

No.4

$$\text{If } F > \frac{10}{2\pi R_F C_F} = \frac{10}{2\pi 100k \times 0,1\mu} = 159 \text{ Hz then } \Delta V_{o(PP)} = -\left(\frac{1}{R_E C_F}\right) \int_{t_1}^{t_2} V_{in(AC)} dt$$

A)


$$V_{(ave)} = V^+ \left(\frac{PW}{T}\right) + V^- \left(\frac{SW}{T}\right)$$

$$V_{in(DC)} = +0,2V$$

$$\Delta V_{o(PP)} = -1000 \int_{t_1}^{t_2} V_{in(AC)} dt$$

$$\Delta V_{o(PP)} = -1000 \times \text{area}$$

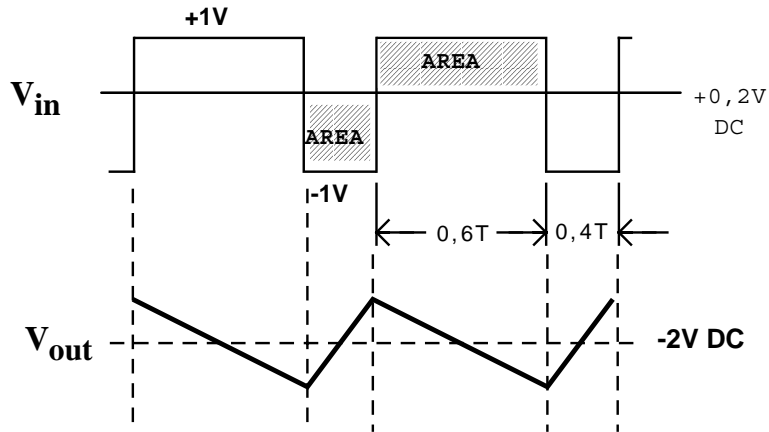Integral does not apply for 50 Hz and 100 Hz.



$\Delta V_{out} = 0,48V_{pp}$  at 1 kHz  
and  $48 \text{ mV}_{pp}$  at 10 kHz


B)

$$\Delta V_{o(PP)} = -1000 \int_{t_1}^{t_2} V_{in(AC)} dt$$

$$\Delta V_{o(PP)} = -1000 \times \text{area}$$

$$= 1000 \times \frac{T}{2} = \frac{1000}{2F} = 1V_{PP}$$

F = 500 Hz  
F > 159 Hz integral OK.

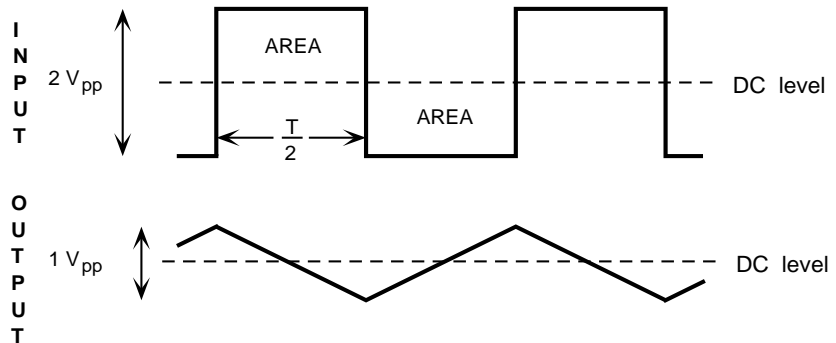

C)


$$\Delta V_{o(PP)} = -1000 \int_{t_1}^{t_2} V_{in(AC)} dt$$

$$\Delta V_{o(PP)} = -1000 \times \text{area}$$

$$= 1000 \times \left(0,5 \times \frac{T}{2}\right) = \frac{250}{F}$$

$$F = 250 \text{ Hz}$$

F > 159 Hz integral OK.

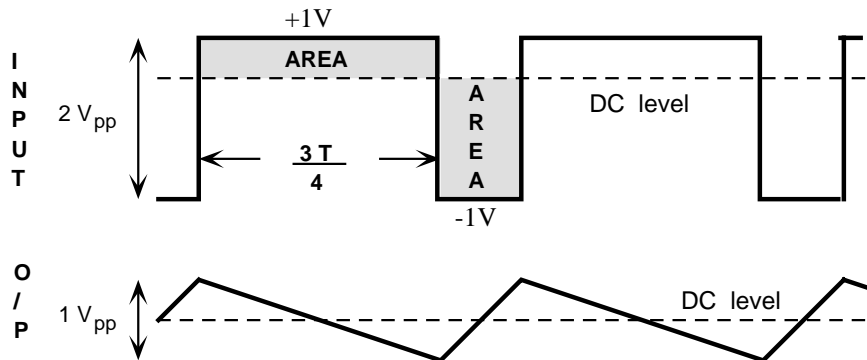

$$V_{(ave)} = V^+ \left(\frac{PW}{T}\right) + V^- \left(\frac{SW}{T}\right)$$

$$V_{in(DC)} = +0,5V$$

## EXERCISE

## IDEAL OP AMP ANALYSIS

No.4 D)

$$\Delta V_o(PP) = -1000 \int_{t_1}^{t_2} V_{in(AC)} dt$$

$$\Delta V_o(PP) = -1000 \times area$$

$$= 1000 \times \left( \frac{100\mu \times 5}{2} \right)$$

$$\Delta V_o(PP) = 0,25V_{PP}$$

O/P is a parabolic wave, not a sine wave.




No.5 A)

$$V_o = -R_F C_E \frac{dV_{in}}{dt}$$

$$V_o = -10K \times 0,1\mu \left( \pm \frac{10V}{2ms} \right)$$

$$V_o = m5V_P$$

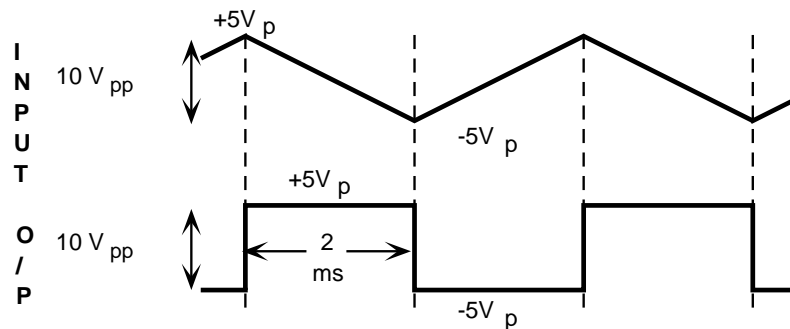

B) On edges we have:

$$V_o = -10K \times 0,1\mu (\pm \infty)$$


$$V_o = m\infty \Rightarrow m V_{sat}$$

On flat portions we have:

$$V_o = -10K \times 0,1\mu (\pm 0)$$

$$V_o = 0$$

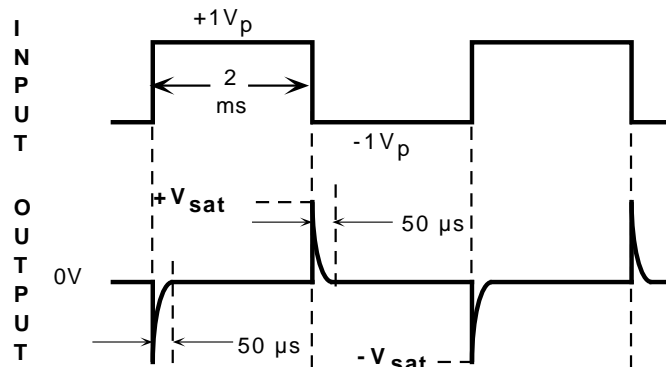The O/P spikes settle down  
in  $5\tau = 5R_E C_E = 50 \mu s$





C) To stabilise negative feedback in order to avoid self oscillations from the circuit.


EXERCISE

IDEAL OP AMP ANALYSIS

No.6 A)

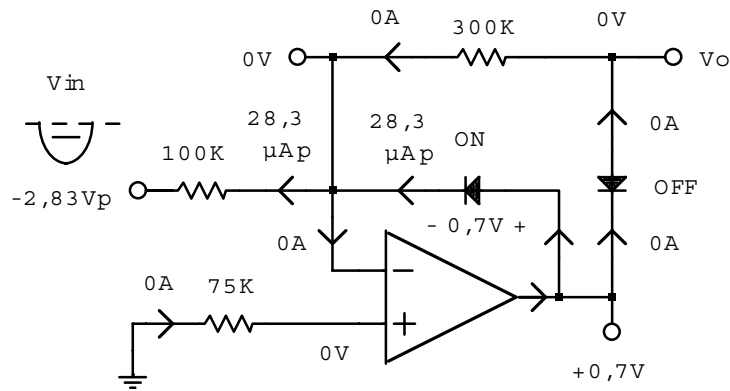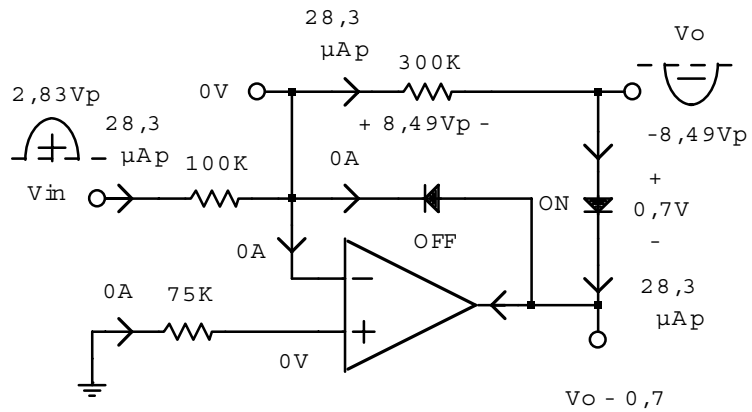


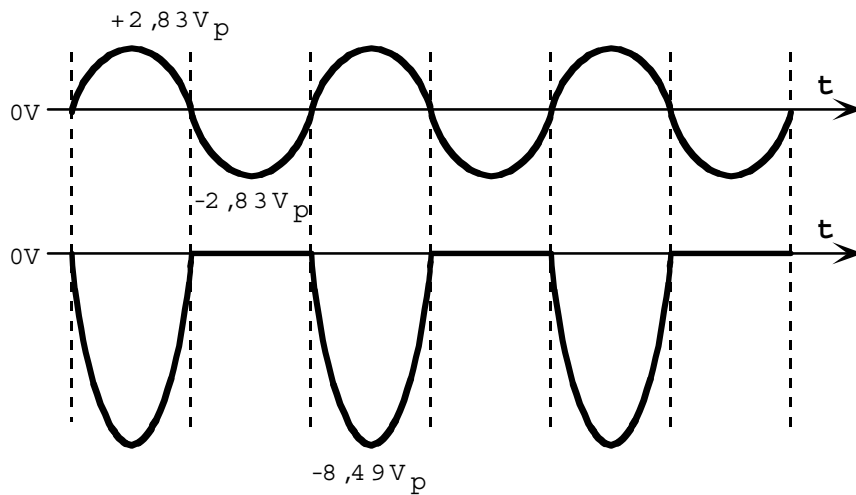
I  
N  
P  
U  
T  
  
O  
U  
T  
P  
U  
T



EXERCISE

IDEAL OP AMP ANALYSIS

N0.6 B)

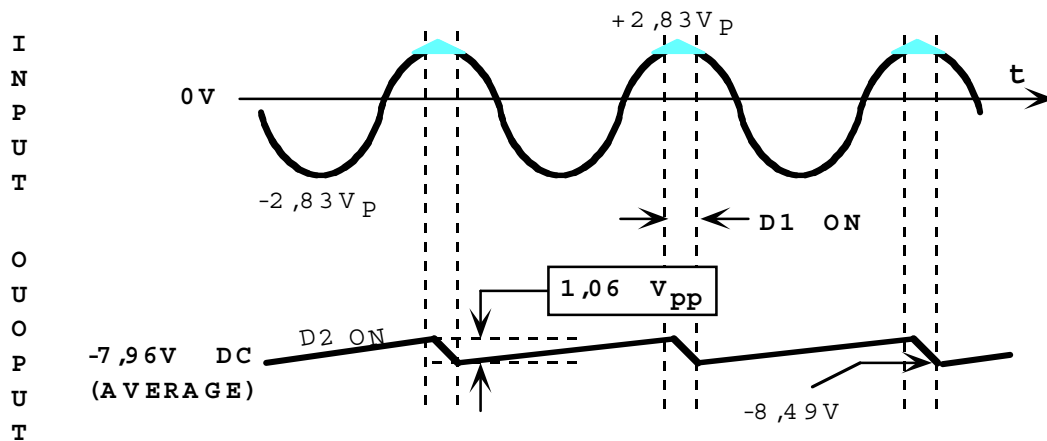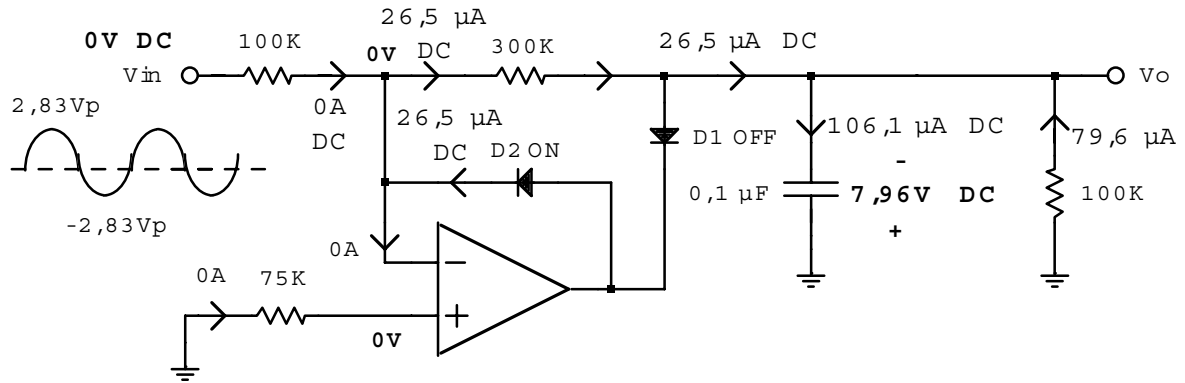

**NOTE:** The bottom of the O/P waveform will not be exactly -8,49V in practice.

first iteration

$$\text{Assume } |V_{o(ave)}| = 8,49V \Rightarrow I_{C(ave)} = \frac{8,49}{100K} + \frac{8,49}{300K} = 113,2 \mu A$$

$$\Delta V_{o(PP)} = \frac{\Delta Q}{C} = \frac{I_{C(ave)} \times \Delta t}{C} \approx \frac{I_{C(ave)} \times T}{C} = \frac{113,2 \mu \times 1m}{0,1\mu} = 1,132 V_{PP}$$

second iteration

$$|V_{o(ave)}| = |V_{o(peak)}| - \frac{\Delta V_{o(PP)}}{2} = 8,49 - \frac{1,132}{2} = 7,924$$

$$I_{C(ave)} = \frac{7,924}{100K} + \frac{7,924}{300K} = 105,65 \mu A$$

$$\Delta V_{o(PP)} = \frac{I_{C(ave)} \times T}{C} = \frac{105,65 \mu \times 1m}{0,1\mu} = 1,056 V_{PP}$$


third iteration (not necessary)

$$|V_{o(ave)}| = 8,49 - \frac{1,056}{2} = 7,96V$$

**EXERCISE**

**IDEAL OP AMP ANALYSIS**

No.7 **Phase Shifter**

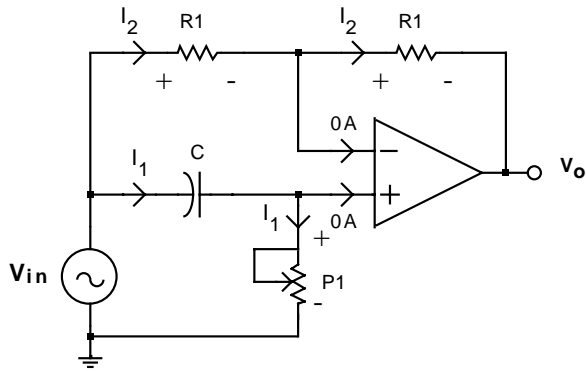

$$V^+ = V_{in} \times \frac{P_1}{P_1 - jX_C} = V^- \quad I_2 = \frac{V_{in} - V^-}{R_1}$$

$$V_o = V^- - I_2 R_1 = V^- - \left( \frac{V_{in} - V^-}{R_1} \right) R_1 = 2V^- - V_{in}$$

$$V_o = 2V_{in} \times \frac{P_1}{P_1 - jX_C} - V_{in} = V_{in} \times \left[ \frac{2P_1}{P_1 - jX_C} - 1 \right]$$

$$A_{VF} = \frac{V_o}{V_{in}} = \left[ \frac{2P_1}{P_1 - jX_C} - 1 \right] = \frac{2P_1 - (P_1 - jX_C)}{P_1 - jX_C}$$


$$A_{VF} = \frac{V_o}{V_{in}} = \frac{P_1 + jX_C}{P_1 - jX_C}$$

$$|A_{VF}| = \frac{\sqrt{P_1^2 + X_C^2}}{\sqrt{P_1^2 + (-X_C)^2}} = 1$$

$$\angle A_{VF} = ATAN\left(\frac{X_C}{P_1}\right) - ATAN\left(\frac{-X_C}{P_1}\right)$$

$$\angle A_{VF} = 2 \times ATAN\left(\frac{X_C}{P_1}\right)$$

No.8 **Phase Shifter**

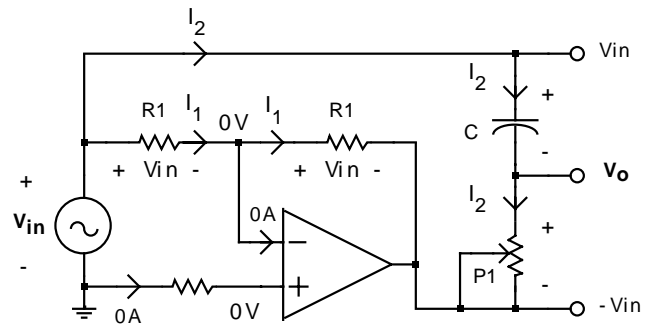

$$I_2 = \frac{V_{in} - (-V_{in})}{P_1 - jX_C} = \frac{2V_{in}}{P_1 - jX_C}$$

$$V_o = -V_{in} + I_2 P_1 = -V_{in} + \left( \frac{2V_{in}}{P_1 - jX_C} \right) P_1$$

$$V_o = V_{in} \times \left[ -1 + \frac{2P_1}{P_1 - jX_C} \right]$$

$$A_{VF} = \frac{V_o}{V_{in}} = \left[ \frac{2P_1}{P_1 - jX_C} - 1 \right] = \frac{2P_1 - (P_1 - jX_C)}{P_1 - jX_C}$$

$$A_{VF} = \frac{V_o}{V_{in}} = \frac{P_1 + jX_C}{P_1 - jX_C}$$

$$|A_{VF}| = \frac{\sqrt{P_1^2 + X_C^2}}{\sqrt{P_1^2 + (-X_C)^2}} = 1$$


$$\angle A_{VF} = ATAN\left(\frac{X_C}{P_1}\right) - ATAN\left(\frac{-X_C}{P_1}\right)$$

$$\angle A_{VF} = 2 \times ATAN\left(\frac{X_C}{P_1}\right)$$

EXERCISE

IDEAL OP AMP ANALYSIS

No.9 Howland current source

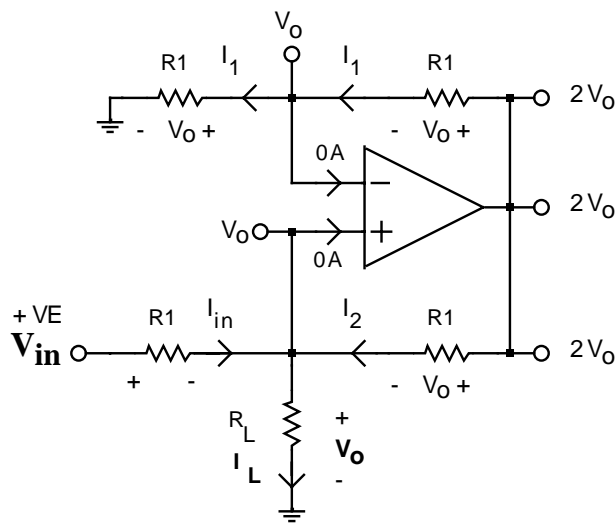


From the circuit diagram, we have:

$$I_L = I_{in} + I_2 = \frac{V_{in} - V_o}{R_1} + \frac{V_o}{R_1}$$

$$I_L = \frac{V_{in}}{R_1} - \frac{V_o}{R_1} + \frac{V_o}{R_1} = \frac{V_{in}}{R_1}$$

No.10 Bridge Amplifier

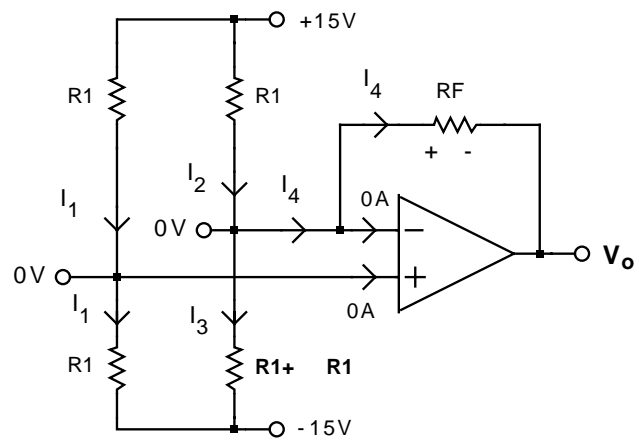

From the circuit diagram, we have:

$$I_4 = I_2 - I_3$$

$$I_4 = \frac{15}{R_1} - \frac{15}{R_1 + \Delta R_1}$$

$$I_4 = \frac{15R_1 + 15\Delta R_1 - 15R_1}{R_1 \times (R_1 + \Delta R_1)}$$

$$I_4 = \frac{15\Delta R_1}{R_1 \times (R_1 + \Delta R_1)}$$

$$V_o = 0 - I_4 R_F$$

$$V_o = - \left( \frac{15\Delta R_1}{R_1 \times (R_1 + \Delta R_1)} \right) R_F$$

Filename: OPA-ASS  
Directory: C:\CLAUDE\ELE-2  
Template: C:\WINDOWS\Application Data\Microsoft\Templates\Normal.dot  
Title: OPA-AN  
Subject: 99FALL  
Author: CLAUDE SAURIOL  
Keywords:  
Comments:  
Creation Date: 9/18/00 4:20 PM  
Change Number: 2  
Last Saved On: 9/18/00 4:20 PM  
Last Saved By: ALGONQUIN COLLEGE  
Total Editing Time: 1 Minute  
Last Printed On: 9/18/00 4:21 PM  
As of Last Complete Printing  
Number of Pages: 16  
Number of Words: 670 (approx.)  
Number of Characters: 3,821 (approx.)