

EXERCISE - OP AMP FREQUENCY RESPONSE


No.1 Look up data sheets for specifications.

A) The op amp shown beside operates from a single supply voltage, therefore determine R_4 and R_5 required to bias V_o to +7,5V DC.

B) Assuming that V_1 , V_2 and V_3 all range from 100 Hz to 10 kHz, calculate the standard values of C_1 , C_2 and C_3 required to obtain the same low cutoff frequency and no attenuation of the input signals at all.


C) Sketch the three gain responses V_o/V_1 , V_o/V_2 and V_o/V_3 on the same graph showing all relevant values.

D) Does the op amp have enough GBW for less than 1 dB attenuation of the HF signals? Explain.

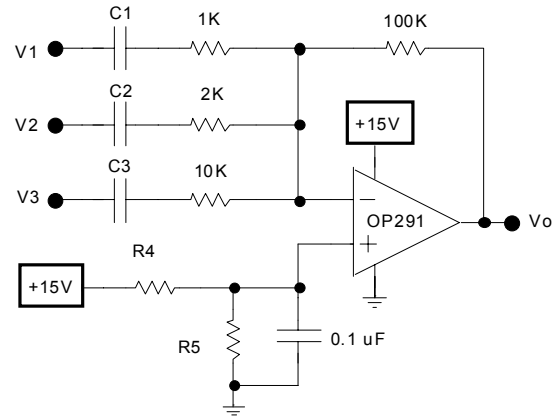

No.2

Sketch the gain response of this circuit assuming typical parameters - fully label with all relevant parameters.

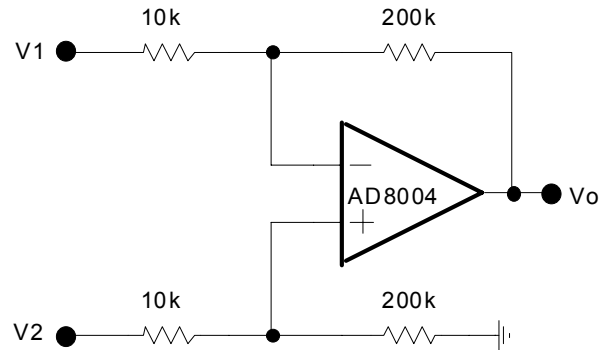


No.3

A) Prove that $A_{VF} = V_o/(V_2-V_1) = Z_F/Z_E$ assuming an ideal op amp.

B) Design the circuit for a gain of 26 dB and sufficient passband to accommodate the inputs whose frequency range is from 50 Hz to 50 kHz. Select the cutoff frequencies for 1 dB of attenuation at 50 Hz and 50 kHz.

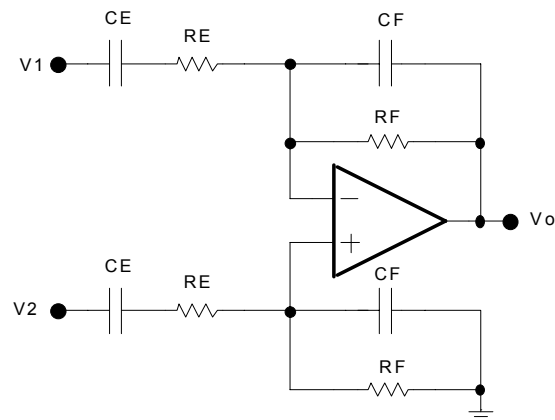C) What is the minimum GBW required for the op amp for less than 10% deviation caused by the GBW on the high cutoff frequency?




Exercise

Op Amp Frequency Response


No.4

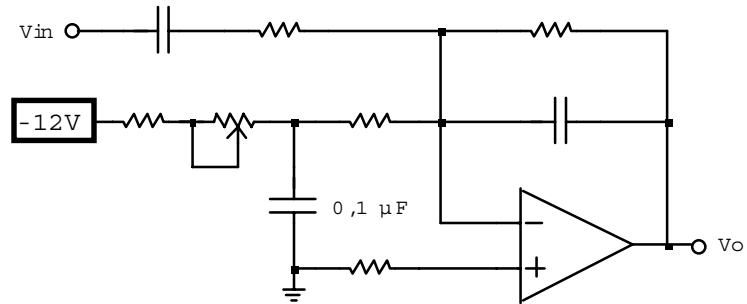Design the circuit for a gain of 30 dB and for $V_o(DC)$ trimmable for $+5V \pm 1V$. Determine the capacitor values for a passband of 1 Hz to 1 kHz.



What is the minimum GBW required of the op amp for less than 1% deviation of the high cutoff frequency caused by GBW?

No.5

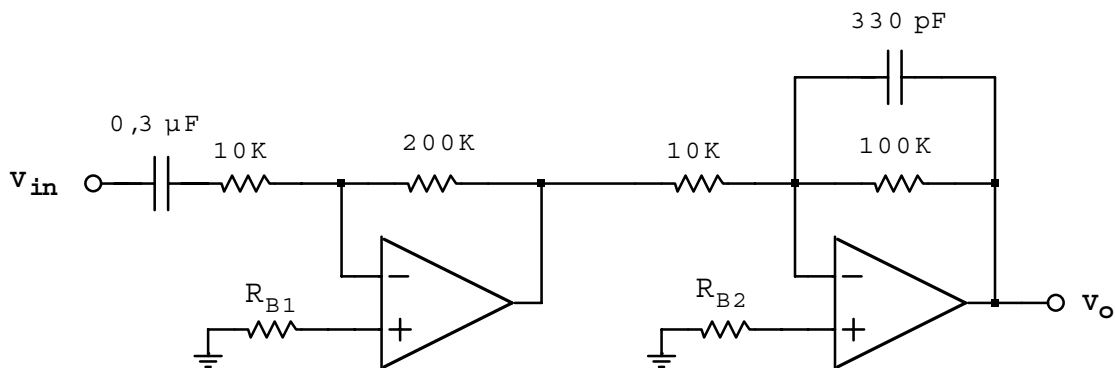

- A) Determine the transfer function of each stage and sketch the gain response of each stage. Also sketch the overall gain response and label with all relevant parameters.
- B) What GBW is sufficient for each stage for less than 10% error on F_{Hi} ? Explain.
- C) Determine the values of R_{B1} and R_{B2} ?

SOLUTIONS


No.1 A) R_4 and R_5 are connected in series, therefore $I_4 = I_5$ and the resistor ratio is given by:

$$\frac{I_4 R_4}{I_5 R_5} = \frac{I_4 R_4}{I_4 R_5} = \frac{R_4}{R_5} = \frac{V_4}{V_5}$$

Now $V_4 = V_5 = 7.5V$, therefore $R_4 = R_5$
In addition, we should balance the op amp inputs for DC resistance:

$$R_4 \parallel R_5 = R_4 \parallel R_4 = 0,5 R_4 = 100K$$

$$R_4 = R_5 = 200K$$

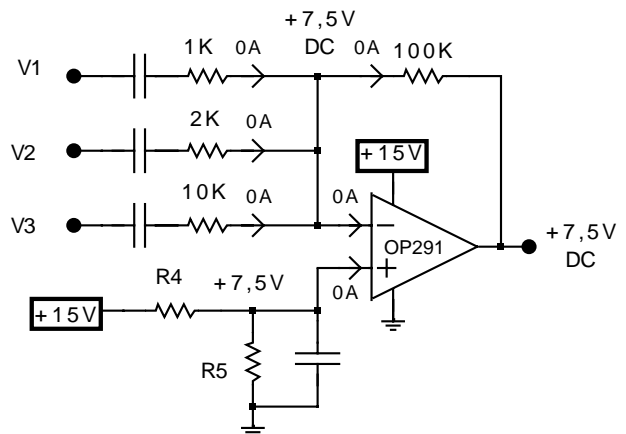

Exercise

B)

$$V_o = -(I_1 + I_2 + I_3)Z_F$$

$$V_o = -\left(\frac{V_1}{Z_1} + \frac{V_2}{Z_2} + \frac{V_3}{Z_3}\right)Z_F$$

$$V_o = -\left(\frac{Z_F V_1}{Z_1} + \frac{Z_F V_2}{Z_2} + \frac{Z_F V_3}{Z_3}\right)$$

$$V_o = -\left(\frac{R_F V_1}{R_1 + \frac{1}{j\omega C_1}} + \frac{R_F V_2}{R_2 + \frac{1}{j\omega C_2}} + \frac{R_F V_3}{R_3 + \frac{1}{j\omega C_3}}\right)$$

$$V_o = -\left(\frac{R_F}{R_1} \times \frac{V_1}{1 + \frac{1}{j\omega R_1 C_1}} + \frac{R_F}{R_2} \times \frac{V_2}{1 + \frac{1}{j\omega R_2 C_2}} + \frac{R_F}{R_3} \times \frac{V_3}{1 + \frac{1}{j\omega R_3 C_3}}\right)$$

Make $F_{C1} = F_{C2} = F_{C3} = 0,1 F_{\min} = 10 \text{ Hz}$ so that the minimum frequency signals are not attenuated.

$$C_1 = (2\pi F_C R_1)^{-1} = (2\pi \times 10 \times 1K)^{-1} = 15,9 \mu\text{F}, \text{ use } \mathbf{22 \mu\text{F std}}, F_{C1} = 7,2 \text{ Hz OK}$$

$$C_2 = (2\pi F_C R_2)^{-1} = (2\pi \times 7,2 \times 2K)^{-1} = 11 \mu\text{F}, \text{ use } \mathbf{10 \mu\text{F std}}, F_{C2} = 7,96 \text{ Hz OK}$$

$$C_3 = (2\pi F_C R_3)^{-1} = (2\pi \times 7,2 \times 10K)^{-1} = 2,21 \mu\text{F}, \text{ use } \mathbf{2,2 \mu\text{F std}}, F_{C3} = 7,2 \text{ Hz OK}$$

C) The high cutoff frequency will be determined by the GBW of the op amp and $\beta_V(\text{HF})$. Assume all X_C 's = 0 at HF.


$$R_{EQ} = 1K \parallel 2K \parallel 10K = 625$$

$$V_F = V_O \times \frac{R_{EQ}}{R_{EQ} + R_F} = V_O \times \frac{625}{625 + 100K}$$

$$V_F = V_O \times \frac{1}{161} \Rightarrow \beta_V = \frac{V_F}{V_O} = \frac{1}{161} = 6,211m$$


$$BW = \beta_V \times GBW = \frac{3M}{161} = 18,63 \text{ kHz}$$


Op Amp Frequency Response

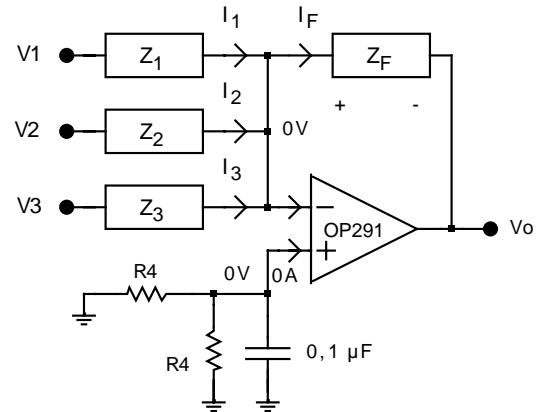

How to find $\beta_V(\text{HF})$

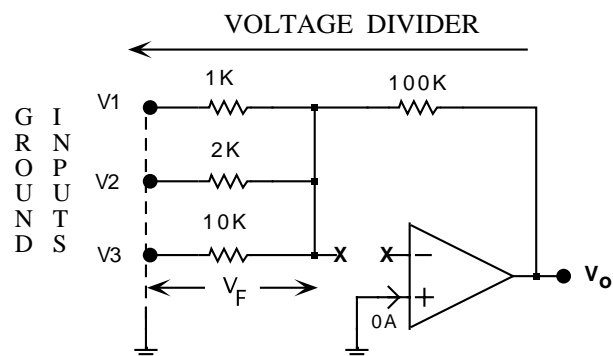All capacitors have close to zero reactance:



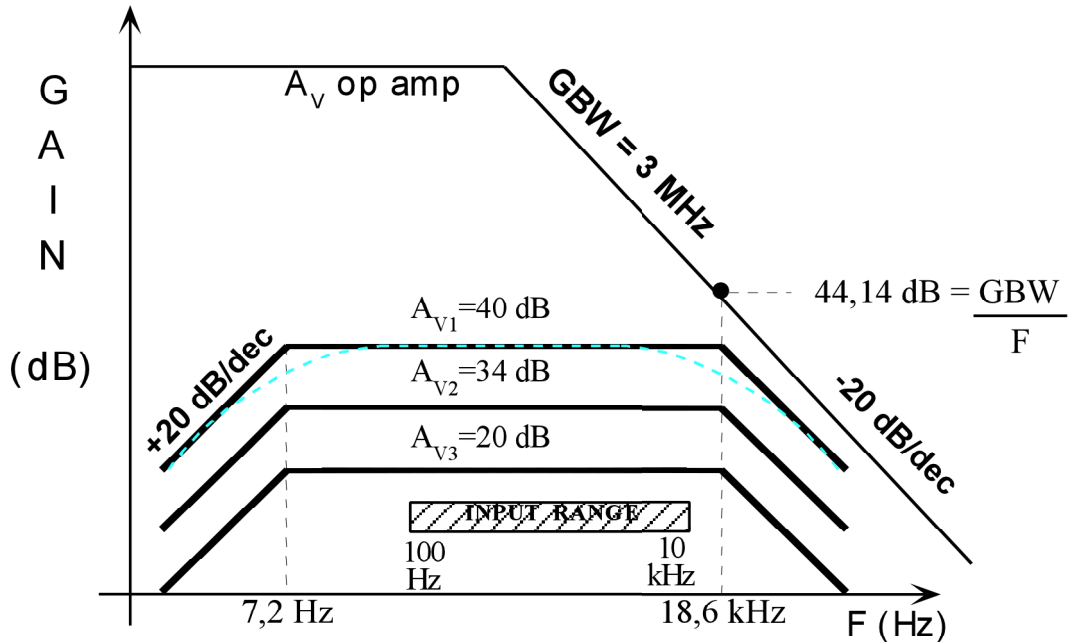

D) For 1 dB of attenuation at F_{max} , $F_{HI} = 2 F_{max}$ or $GBW = 2 F_{max} / \beta_V = 20k \times 161 = 3,22 \text{ MHz}$. So the OP291 would be fine with its typical GBW of 3 MHz but not for units having a worst case minimum GBW. Therefore the OP291 is not adequate, one should pick an op amp with a worst case minimum GBW of 3,22 MHz.



No.2

To find β_V , ground all inputs and open feedback loop, then find V_F in terms of V_o .

$$V_F = V_o \times 10K / (10K + 200K) = V_o / 21$$

$$\beta_V = V_F / V_o = 1/21$$
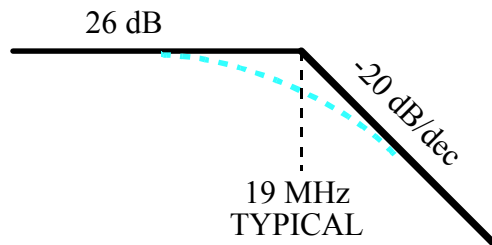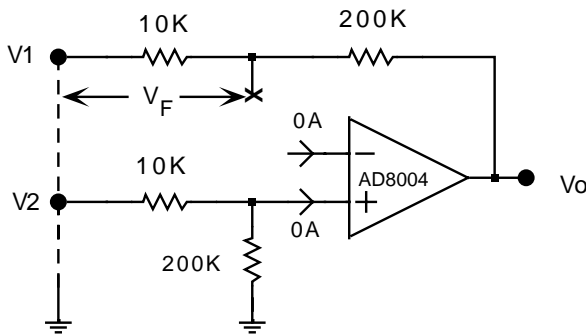
$$BW = \beta_V \times GBW = 400M / 21 = 19,05 \text{ MHz typ}$$



Typical Gain Response

Exercise

No.3 A)

$$V^+ = V^- = V_2 \times \frac{Z_F}{Z_E + Z_F}$$


$$V_o = V^- - I_1 Z_F = V^- - \left(\frac{V_1 - V^-}{Z_E} \right) Z_F$$

$$V_o = V^- + V^- \left(\frac{Z_F}{Z_E} \right) - V_1 \left(\frac{Z_F}{Z_E} \right)$$

$$V_o = V^- \left(1 + \frac{Z_F}{Z_E} \right) - V_1 \left(\frac{Z_F}{Z_E} \right)$$


$$V_o = V_2 \times \left(\frac{Z_F}{Z_E + Z_F} \right) \left(\frac{Z_E + Z_F}{Z_E} \right) - V_1 \left(\frac{Z_F}{Z_E} \right) = V_2 \left(\frac{Z_F}{Z_E} \right) - V_1 \left(\frac{Z_F}{Z_E} \right) = \left(\frac{Z_F}{Z_E} \right) \times (V_2 - V_1)$$

Op Amp Frequency Response

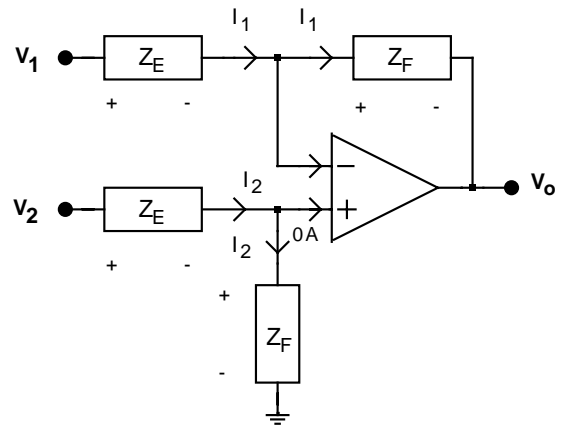


B)
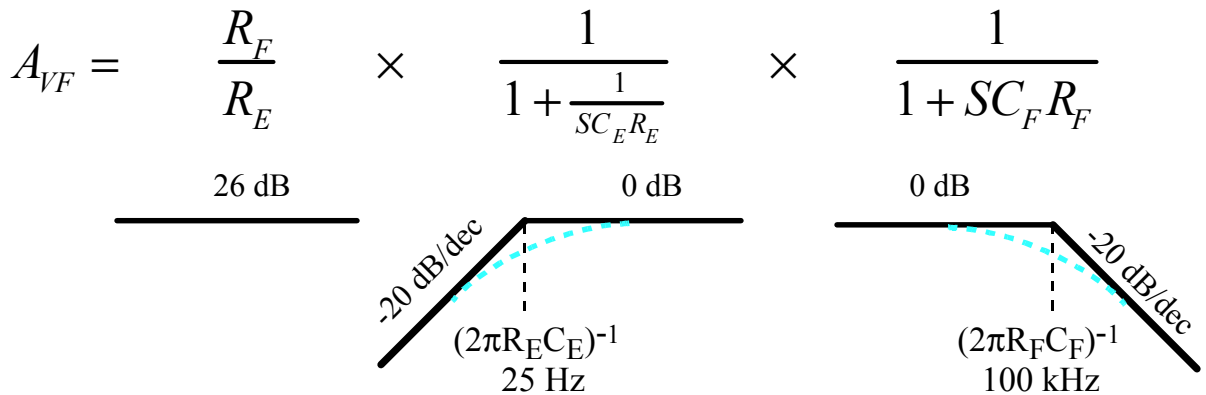
$$A_{VF} = \frac{Z_F}{Z_E} = \frac{R_F (1/SC_F)}{R_E + (1/SC_E)} = \frac{R_F}{R_E} \times \frac{1}{1 + \frac{1}{SC_E R_E}} \times \frac{1}{1 + SC_F R_F}$$



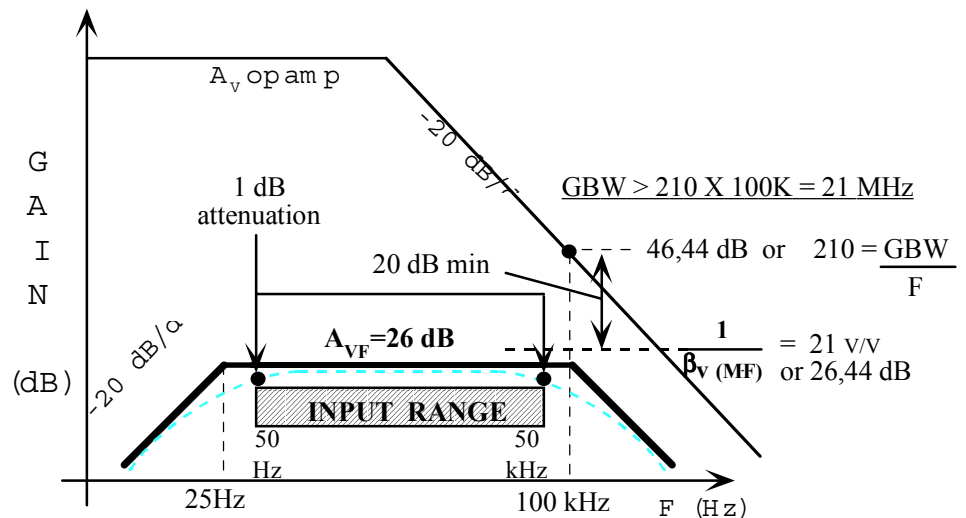For less than 10% error on $F_{HI} = 100$ kHz, A_v of op amp must be at least 20 dB above $(1/\beta_v)$ at $F = F_{HI}$. Tolerance of the components will introduce additional % error on F_{LO} and F_{HI} .



Exercise

Op Amp Frequency Response

Let $R_F = 20K$, $R_E = \frac{R_F}{|A_{VF}|} = \frac{20K}{20} = 1K$


$C_F = \frac{1}{2\pi R_F F_{Hi}} = \frac{1}{2\pi \times 20K \times 100K} = 79.6 \text{ pF}$, use 75 pF std $\Rightarrow F_{Hi} = \frac{1}{2\pi R_F C_F} = 106.1 \text{ kHz}$

$C_E = \frac{1}{2\pi R_E F_{Lo}} = \frac{1}{2\pi \times 1K \times 25} = 6.37 \text{ }\mu\text{F}$, use 6.8 }\mu\text{F std} $\Rightarrow F_{Lo} = \frac{1}{2\pi R_E C_E} = 23.4 \text{ Hz}$

Final Circuit

Stray capacitance will affect F_{Hi} because $C_F = 75 \text{ pF}$ is small and op amp GBW will lower F_{Hi} by about 8,4% if GBW = 21 MHz, that is

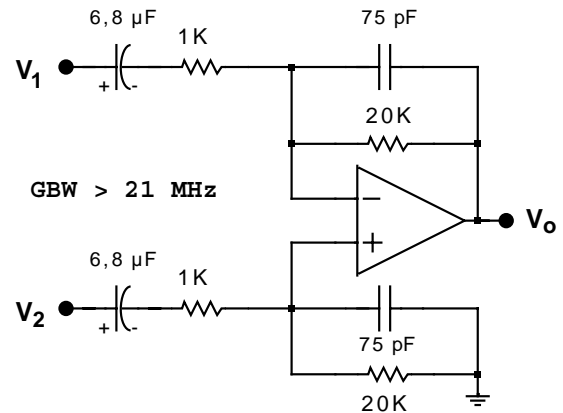$F_{Hi} = 106,1k \times \left(\frac{100 - 8,4}{100}\right) = 97,2 \text{ kHz}$



No.4 Let $R_E = 15K$, $R_F = |A_{VF}| \times R_E = 31.62 \times 15K = 474.3K$, use 470K std

$C_F = \frac{1}{2\pi R_F F_{Hi}} = \frac{1}{2\pi \times 470K \times 1K} = 338.6 \text{ pF}$, use 330 pF std $\Rightarrow F_{Hi} = \frac{1}{2\pi R_F C_F} = 1.026 \text{ kHz}$


$C_E = \frac{1}{2\pi R_E F_{Lo}} = \frac{1}{2\pi \times 15K \times 1} = 10.6 \text{ }\mu\text{F}$, use 10 }\mu\text{F std} $\Rightarrow F_{Lo} = \frac{1}{2\pi R_E C_E} = 1.06 \text{ Hz}$

$R_B = 470K \parallel \left(470K + \frac{500K}{2} + 430K\right)$

$R_B = 333.6K$ use 330K std

NOTE: the 0,1 }\mu\text{F cap is used to filter +12V supply rail noise. V_{in} must be positive all the time to ensure correct polarity of 10 }\mu\text{F polarised cap.

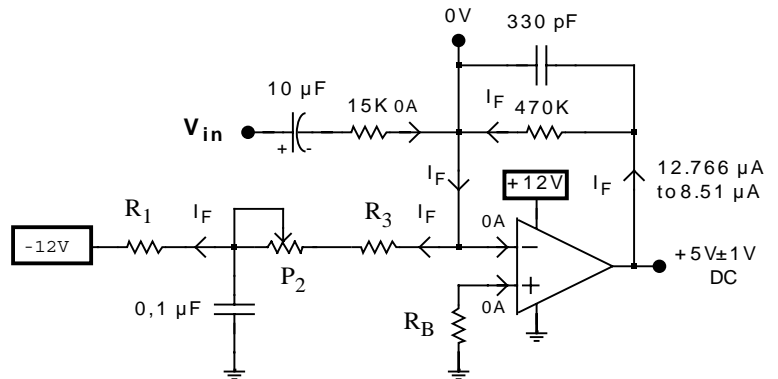$GBW > 100 F_{Hi} (1/\beta_V) = 100 \times 1K \times 32.33 = 3,23 \text{ MHz}$ for less than 1% error caused by GBW on $F_{Hi} = 1 \text{ kHz}$.



$R_{tot} = R_1 + P_2 + R_3 = 12V / 12.766 \text{ }\mu\text{A} \rightarrow 8.51 \text{ }\mu\text{A}$

$R_{tot} = 0.94M\Omega \rightarrow 1.41M\Omega$

$P_2 = \Delta R_{tot} = 0.94M - 1.41M = 470K$ use 500K pot std

$R_1 + R_3 = R_{tot(max)} - P_2 = 1.41M - 500K = 910K$,


let $R_1 = 470K$ std,

then $R_3 = 910K - 470K = 440K$ use 430K std

Exercise


No.5 A)

Op Amp Frequency Response

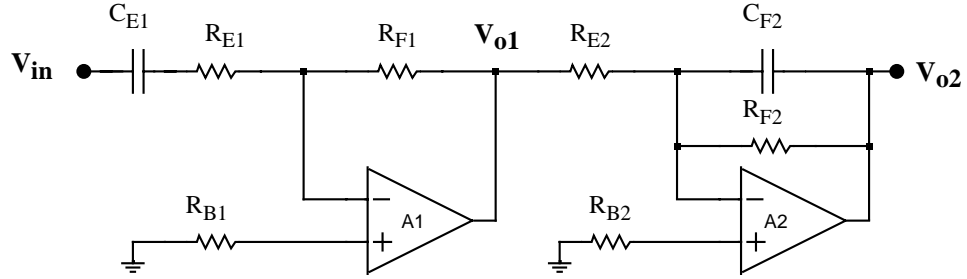

$$A_{V(tot)} = A_{V1} \times A_{V2} = \left(-\frac{Z_{F1}}{Z_{E1}} \right) \times \left(-\frac{Z_{F2}}{Z_{E2}} \right) = \left(\frac{R_{F1}}{R_{E1} + \frac{1}{sC_{E1}}} \right) \times \left(\frac{R_{F2} \parallel \frac{1}{sC_{E2}}}{R_{E2}} \right)$$
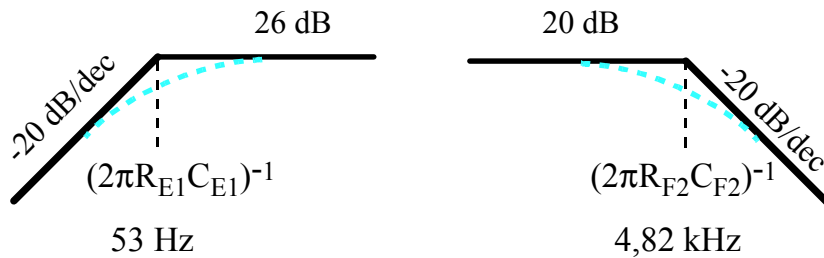
$$A_{V(tot)} = \left(\frac{R_{F1}}{R_{E1}} \times \frac{1}{1 + \frac{1}{sR_{E1}C_{E1}}} \right) \times \left(\frac{R_{F2}}{R_{E2}} \times \frac{1}{1 + sC_{E2}R_{E2}} \right)$$




No.5 C)

$$R_{B1} = 200k$$

$$R_{B2} = 10k \parallel 100k = 9,1k$$

Overall gain response

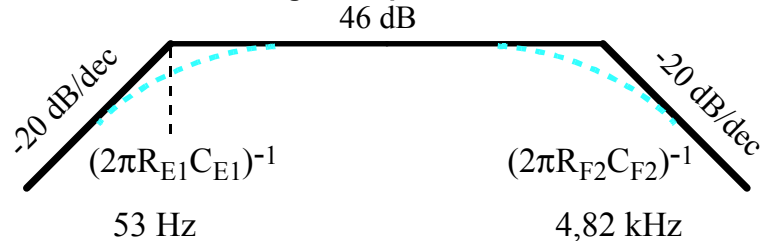

No.5 B)

To minimise the impact of the high cutoff frequency of the first stage on the 4,82 KHz cutoff of the second stage, it should be at least one decade above 4,82 kHz, which means its GBW > 1.01 MHz..

To obtain less than 10% error on the 4.82 kHz frequency, the op amp gain should be at least 20 dB above $1/\beta_{V2(res)}$. that is GBW > 530.2 kHz.

The worst case minimum GBW is therefore 1.01 MHz.

