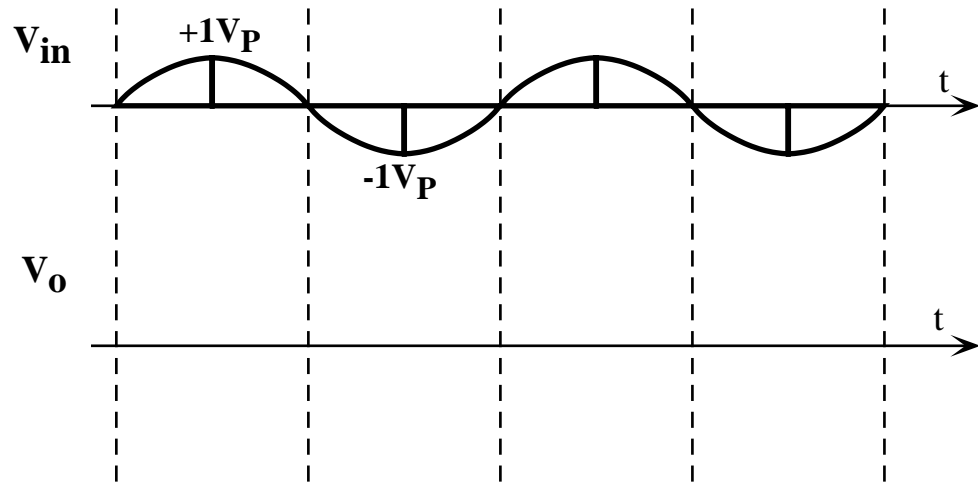




Show V_o waveform wrt V_{in} waveform.




No.2



Positive V_{in}

Negative V_{in}

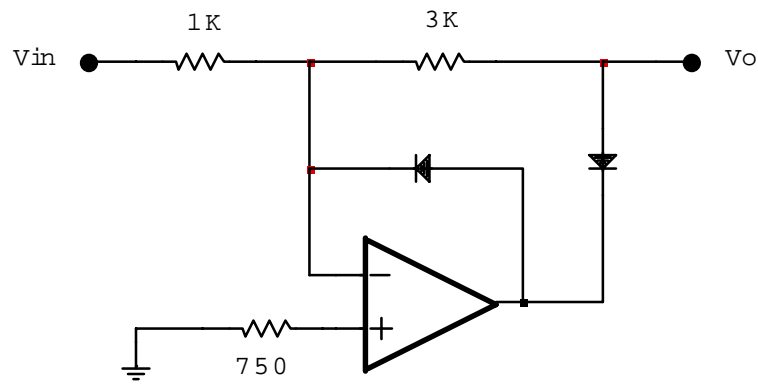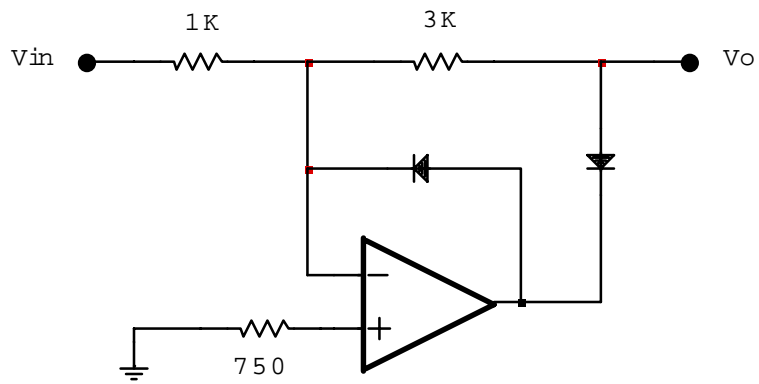



Show V_o waveform wrt V_{in} waveform.

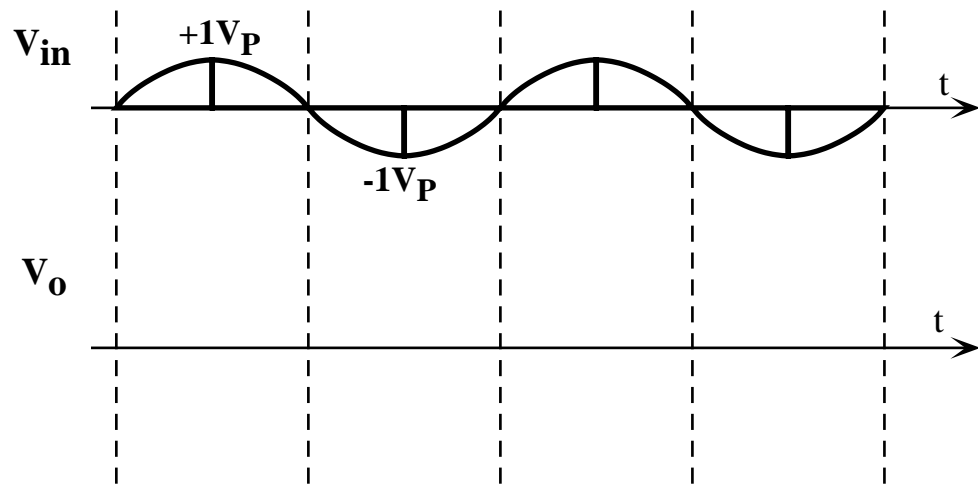

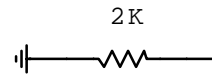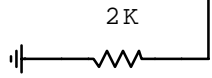



Show V_o waveform wrt V_{in} waveform.

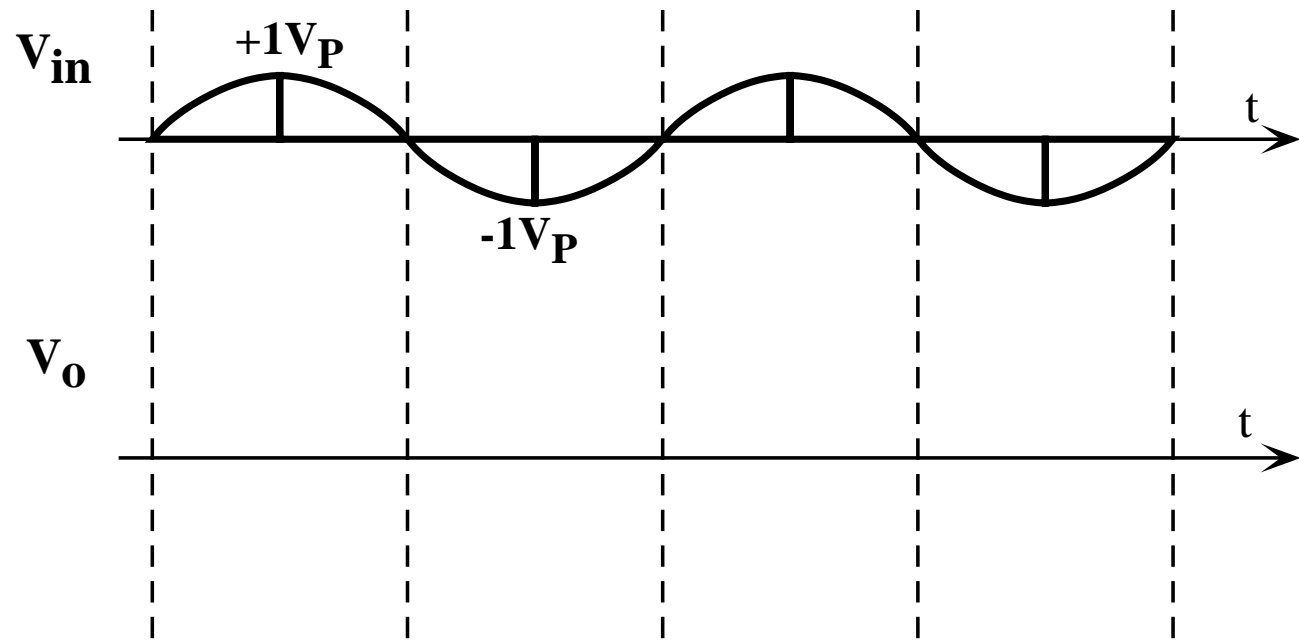

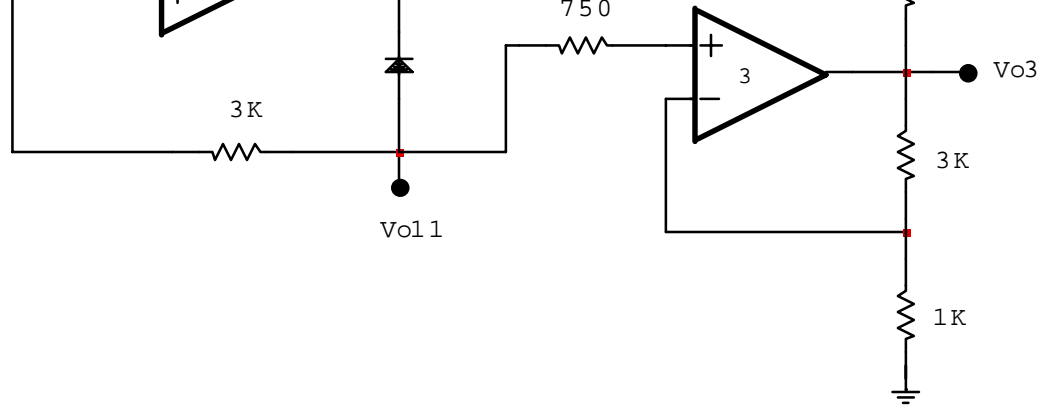




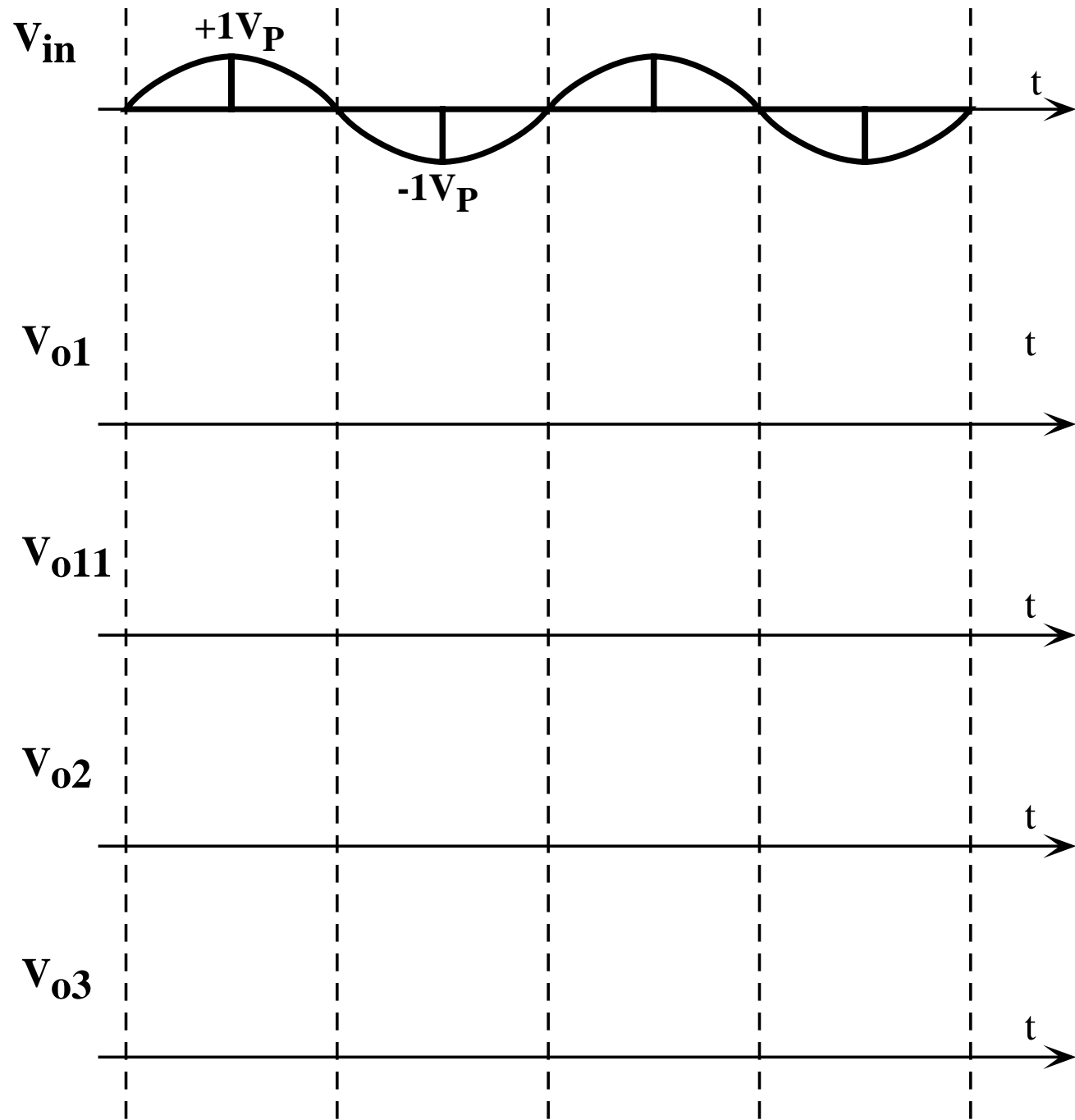
Show V_{o1} , V_{o11} , V_{o2} and V_{o3} waveforms wrt V_{in} waveform.



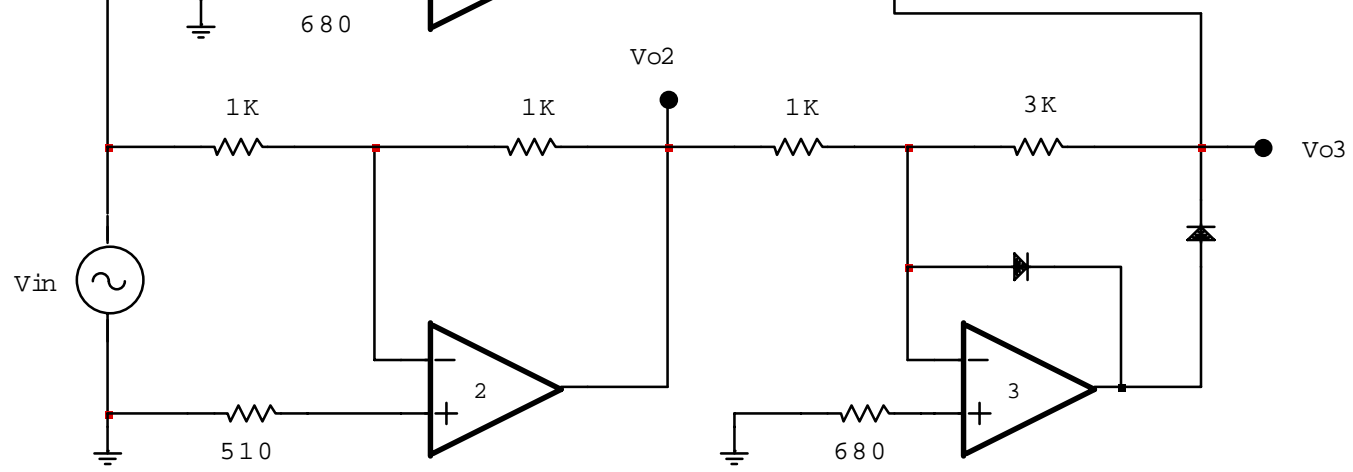

Show V_{o1} , V_{o2} , V_{o3} and V_{o4} waveforms wrt V_{in} waveform.



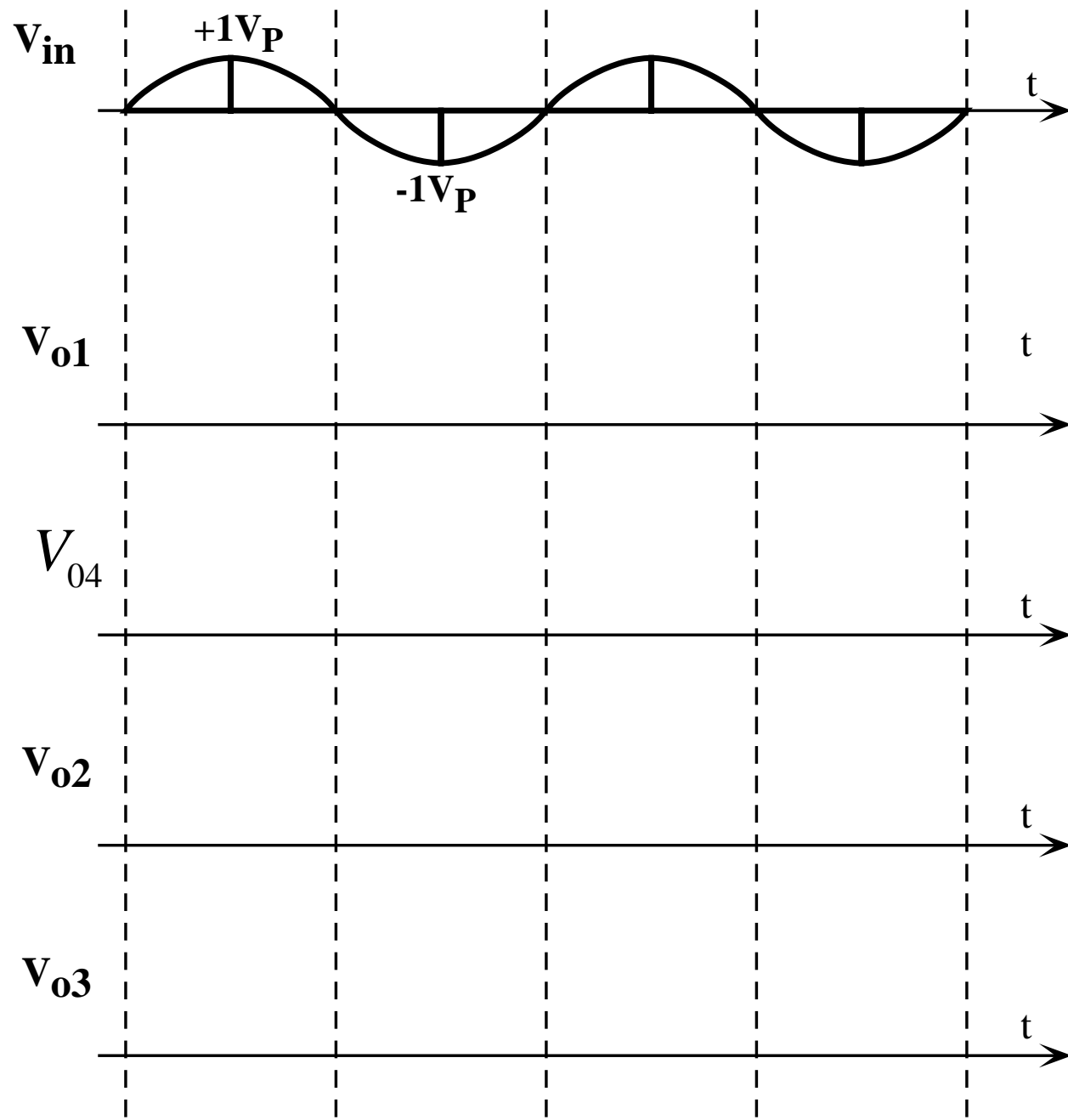


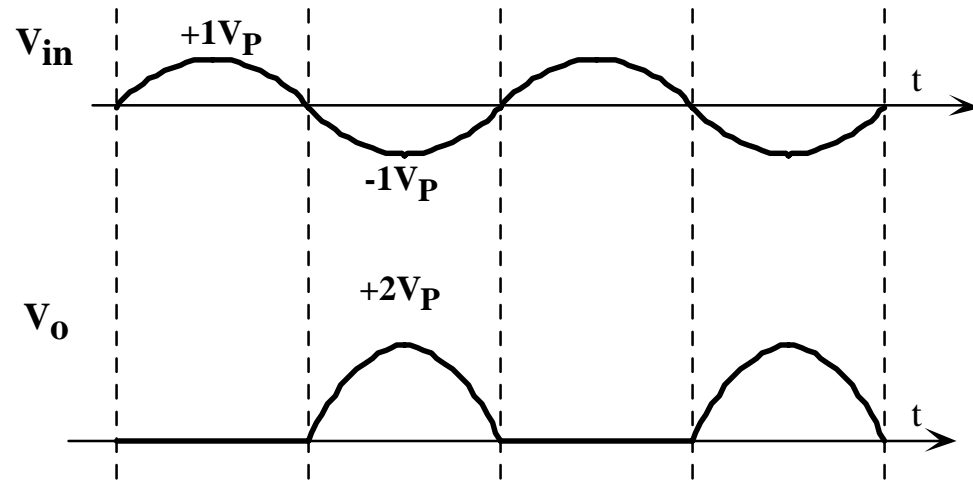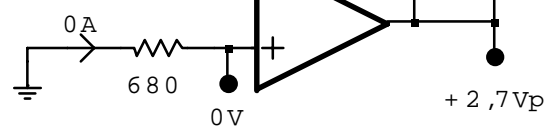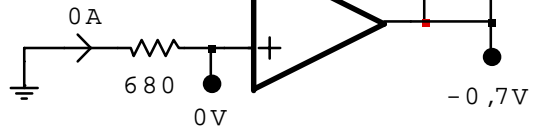


No.2

Positive Vin


Negative Vin

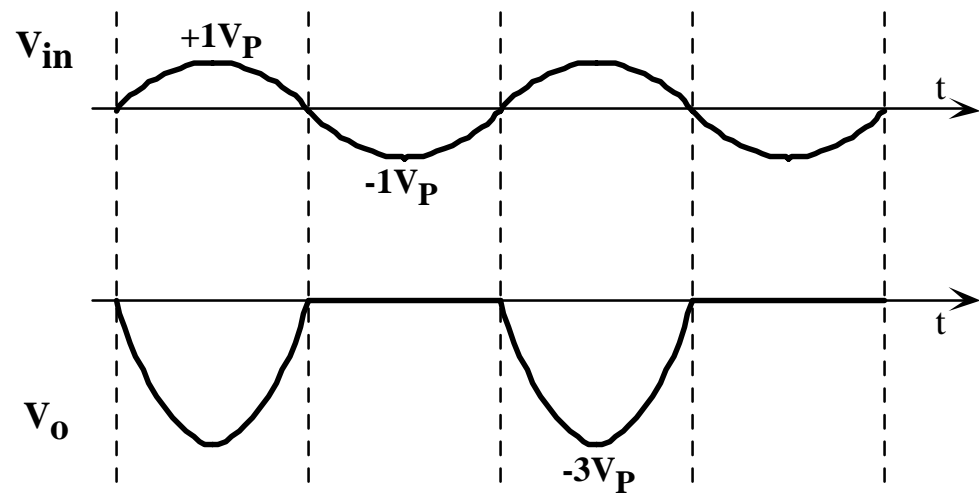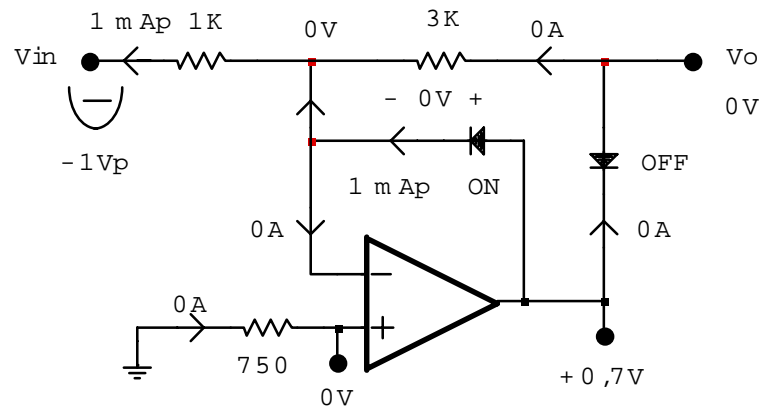
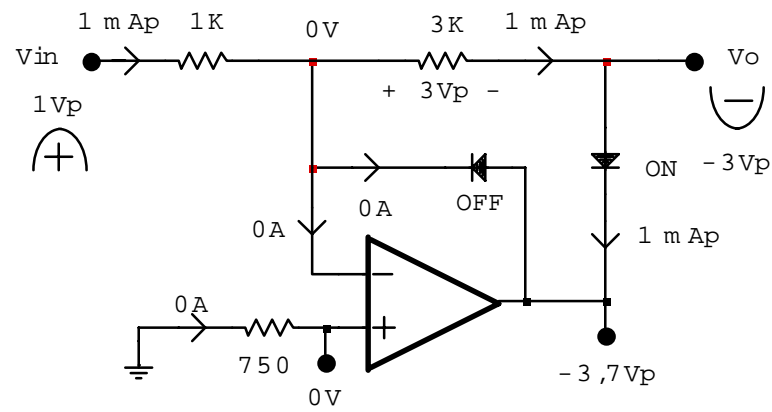


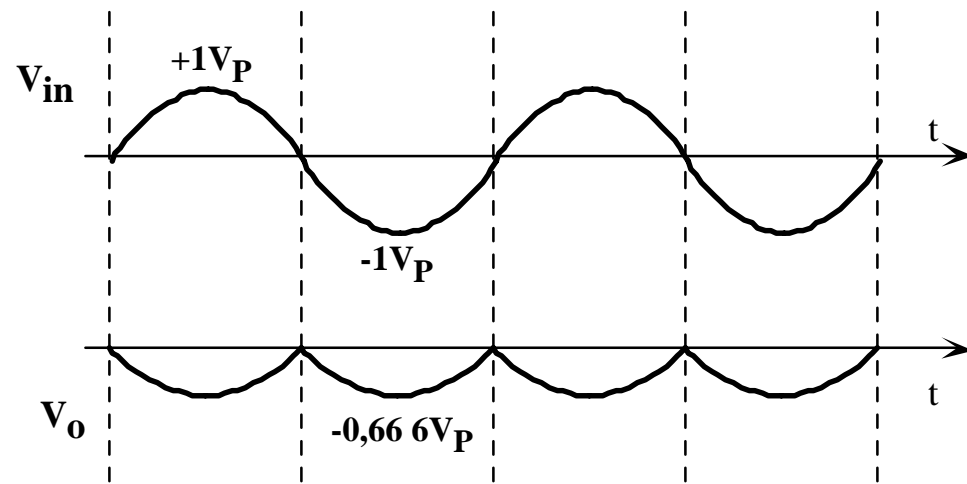


No.4

Positive Vin

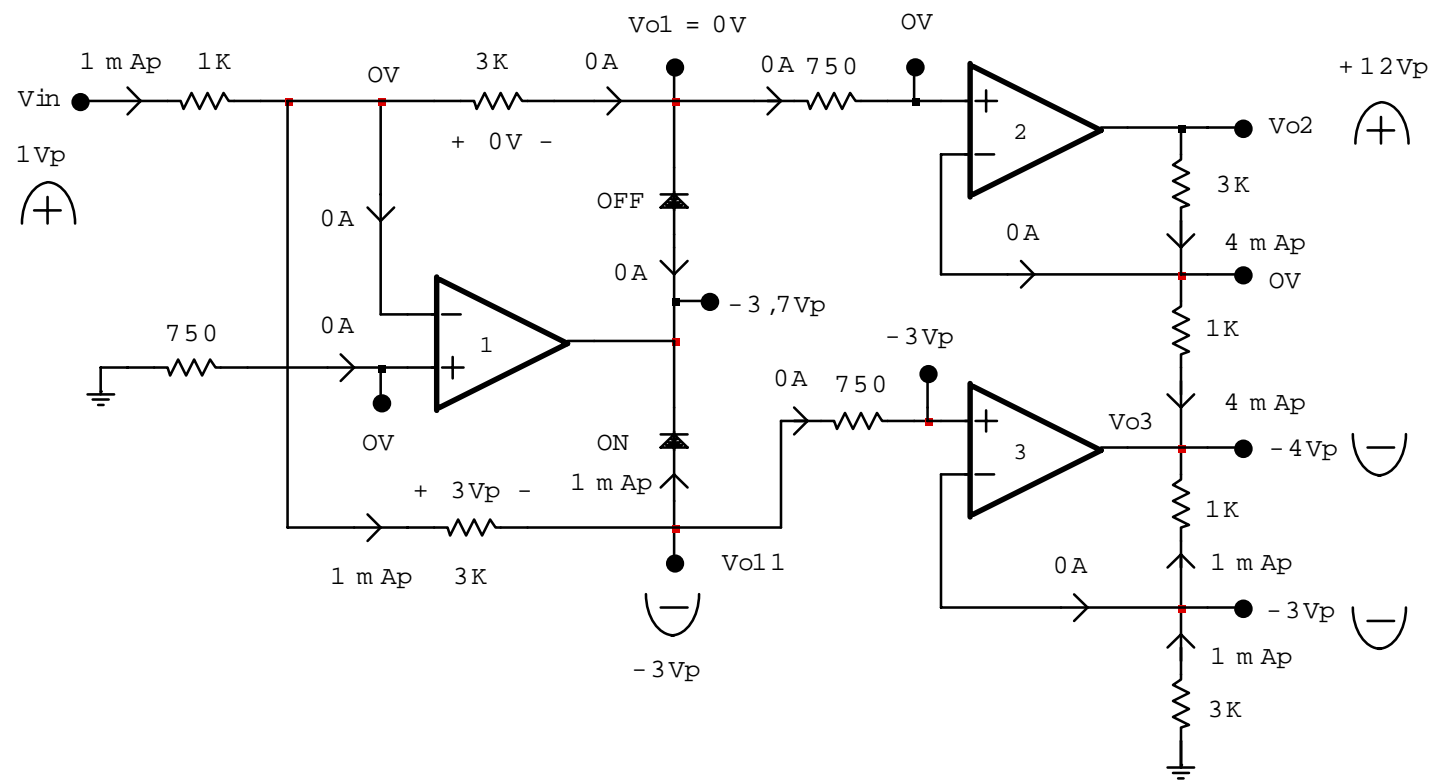

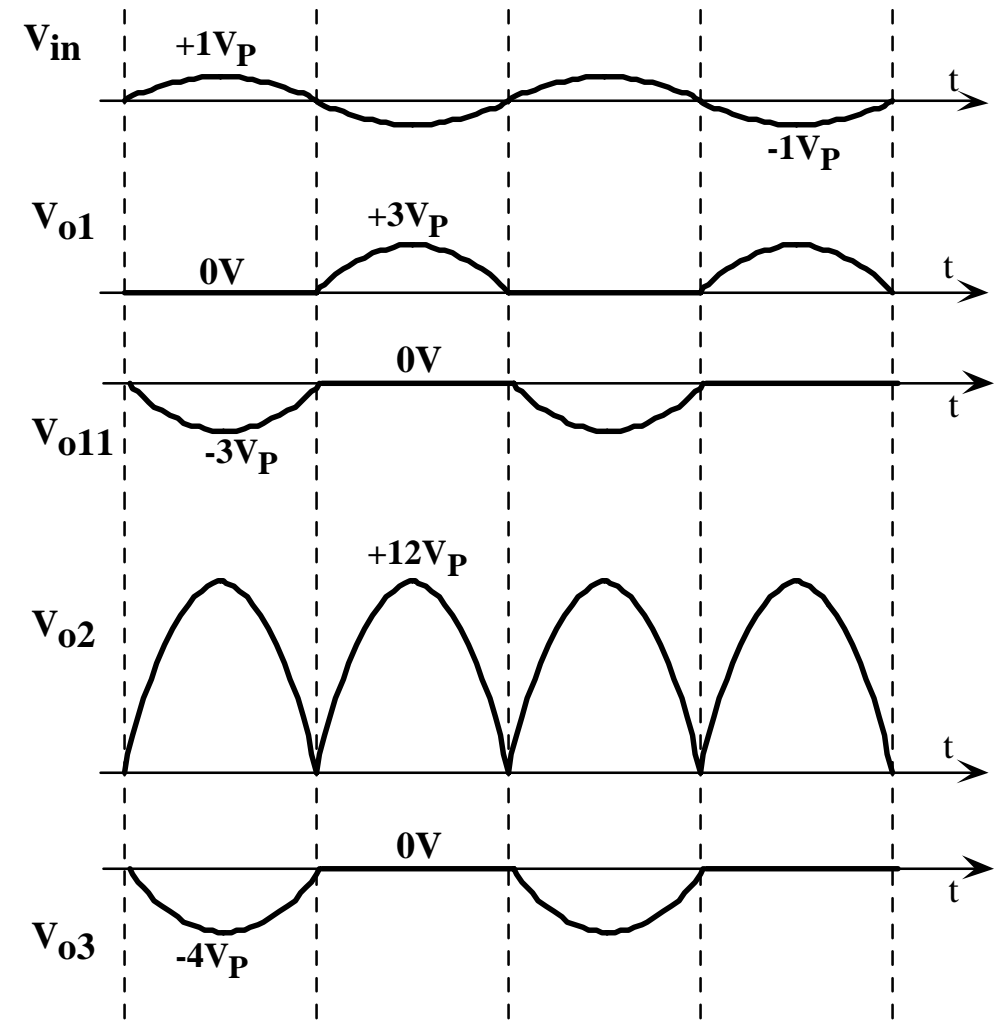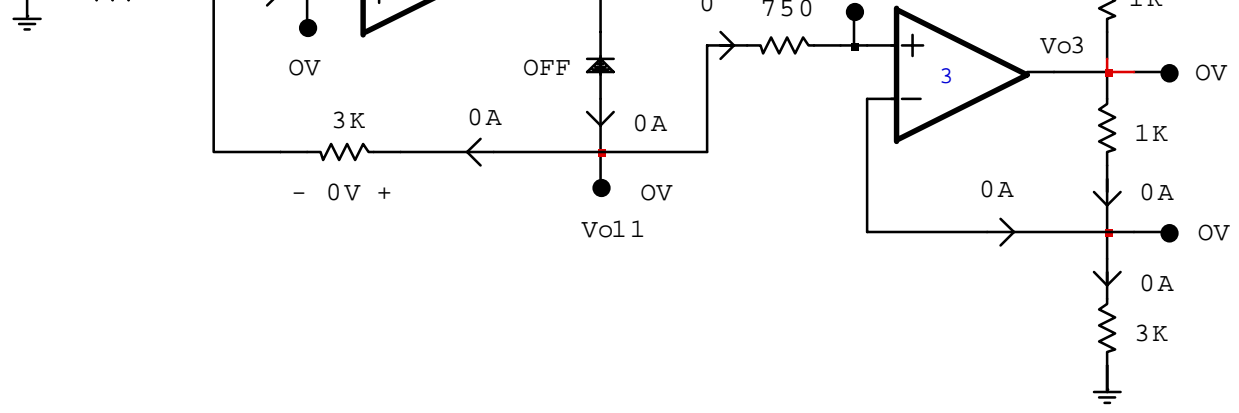

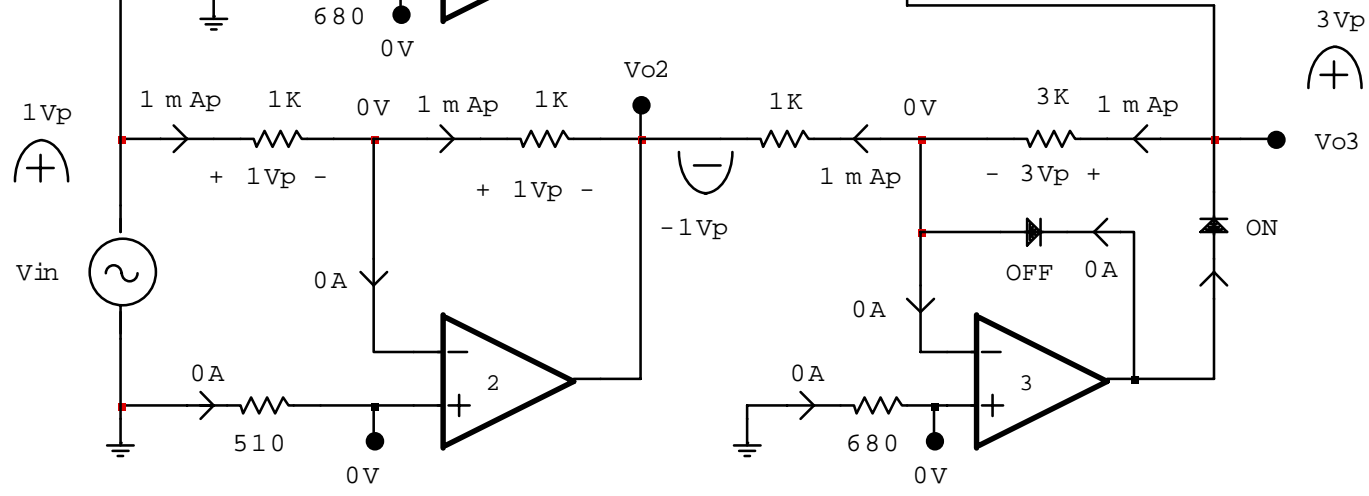

Negative Vin

