
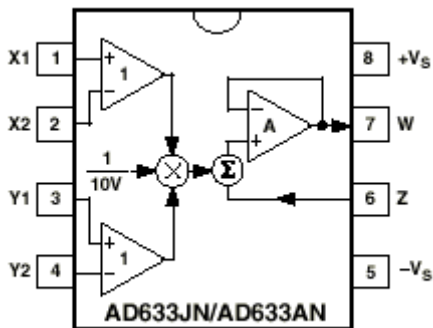



AUTOMATIC GAIN CONTROL

PART 1 AGC with passive peak detector

Circuit Diagram

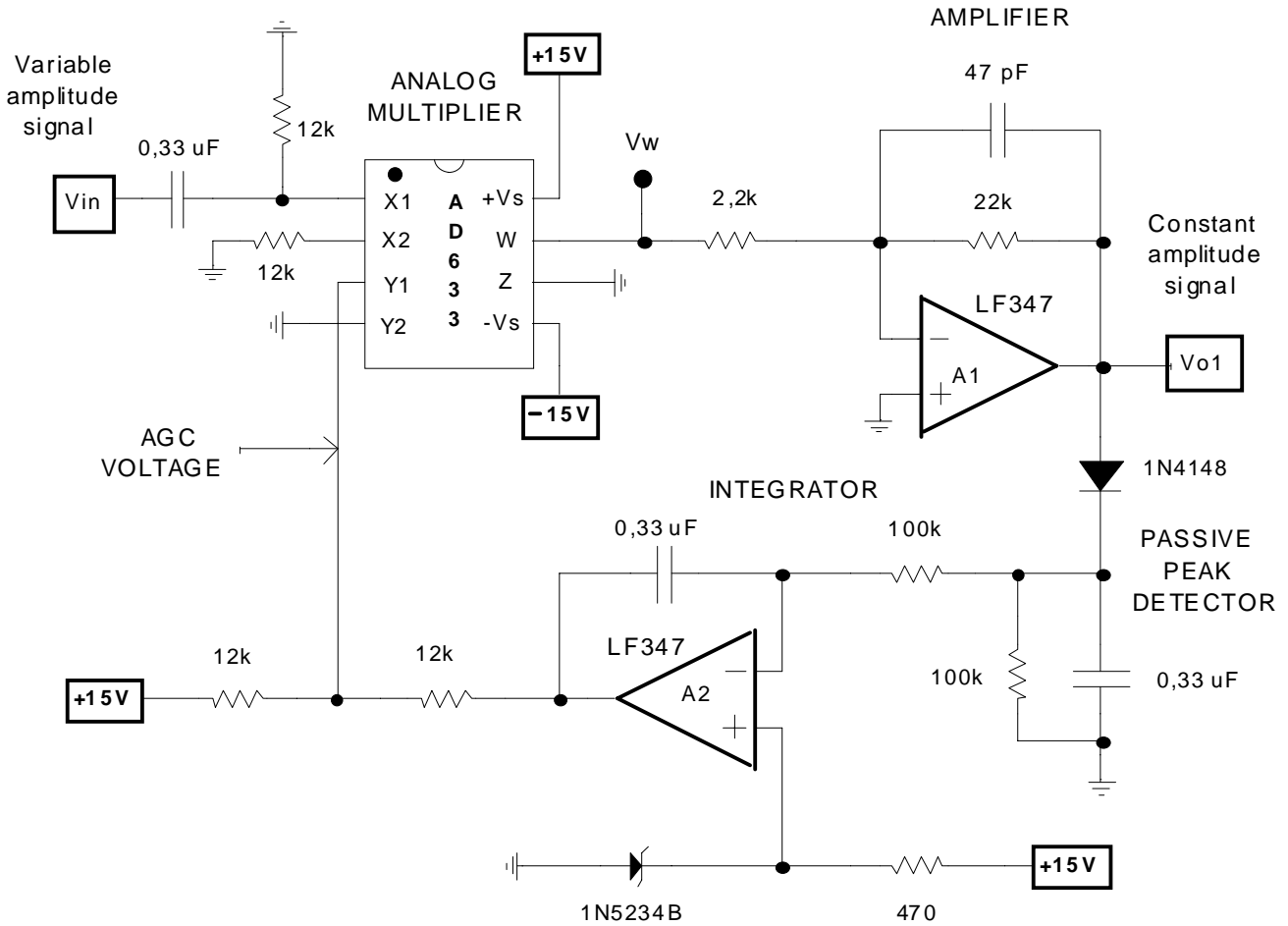

AD633 Analog Multiplier

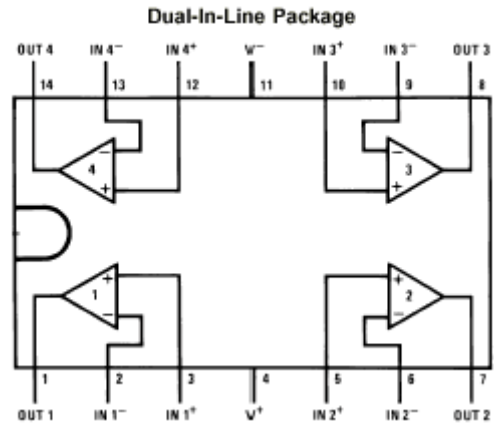

LF347 Quad Op Amp

Pre-lab

1. Determine the regulated amplitude of V_{o1} – look up Zener data at <http://www.fairchildsemi.com/>
2. Determine V_{Y1} min and max assuming typical saturation voltages for LF347 with $V_{sup} = \pm 15V$
3. Determine the range of input voltages (main input V_{in}) for which the AGC is operational. Why does not the AGC work outside this above-calculated range?
4. What is the peak AC voltage of V_w ?
5. Determine the peak to peak ripple at the peak detector output and at V_{Y1} for frequencies of 1 kHz and 10 kHz. Draw the expected ripple waveforms.

Lab Procedure

NOTE: The HP signal generator displays half the actual O/P amplitude if load $\gg 50\Omega$
 If load = 50Ω , it displays the correct amplitude.

1. Assemble circuit as per breadboard layout provided at the end.
2. Using a 1 kHz input sinewave, **adjust the amplitude of V_{in}** in order to obtain the DC voltages for V_{Y1} listed below. For each case measure the corresponding values of V_{o2} (DC), V_{o1} (rms), V_w (rms) and V_{in} (rms) with the DMM. Monitor V_{in} and V_{o1} on the oscilloscope throughout. Calculate A_{mult} from measurements.
3. Repeat the above for $V_{Y1(DC)}$ slightly above minimum and slightly below maximum when V_{o1} is still constant.

V_{Y1} (DC)	min	1	2	4	6	8	10	max
V_{o2} (DC)								
V_{o1} (rms)								
V_{in} (rms)								
V_w (rms)								
$A_{mult} = \frac{V_w}{V_{in}}$								

4. Measure the exact value of the Zener reference voltage – record value.
5. Measure the ripple voltage (with the scope) at the peak detector output and at V_{Y1} at frequencies of 100 Hz, 1 kHz and 10 kHz – ripple may be too small to be measured in some cases. Ensure that V_{in} is within operating range.

1. Determine the regulated amplitude of V_{o1} – look up Zener data at <http://www.fairchildsemi.com/>
2. Determine V_{Y1} min and max assuming typical saturation voltages for LF347 with $V_{sup} = \pm 15V$
3. Determine the range of input voltages (main input V_{in}) for which the AGC is operational. Why does not the AGC work outside this above-calculated range?
4. What is the peak AC voltage of V_w ?
5. Determine the peak to peak ripple at the peak detector output and at V_{Y1} for frequencies of 1 kHz and 10 kHz. Draw the expected ripple waveforms.

Lab Procedure

1. Assemble circuit as per breadboard layout provided at the end – don’t forget to remove the 47 pF capacitor in the inverting amplifier.
2. Using a 1 kHz input sinewave, **adjust the amplitude of V_{in}** in order to obtain the DC voltages for V_{Y1} listed below. For each case measure the corresponding values of V_{o2} (DC), V_{o1} (rms), V_w (rms) and V_{in} (rms) with the DMM. Monitor V_{in} and V_{o1} on the oscilloscope throughout. Calculate A_{mult} from measurements.
3. Repeat the above for $V_{Y1(DC)}$ slightly above minimum and slightly below maximum when V_{o1m} is still constant.

V_{Y1} (DC)	min	1	5	10	max
V_{o2} (DC)					
V_{o1} (rms)					
V_{in} (rms)					
V_w (rms)					
$A_{mult} = \frac{V_w}{V_{in}}$					

4. Measure the exact value of the Zener reference voltage – record value.
5. Measure the ripple voltage (with the scope) at the peak detector output and at V_{Y1} at frequencies of 100 Hz, 1 kHz and 10 kHz – ripple may be too small to be measured in some cases. Ensure that V_{in} is within operating range.
6. With V_{in} set such as to obtain V_{Y1} around 4V DC, measure V_{o1} (rms) at 1 kHz, 10 kHz, 100 kHz and measure the minimum and maximum frequencies at which V_{o1} is no longer regulated.

Post lab

1. Compare measured values to pre-lab values everywhere applicable.
2. Did V_{o1} vary at all? What was the % variation of V_{o1} ? Is it good? Explain.
3. Using the results of step 3 of the procedure, explain how the AGC circuit works.
4. Compare the performance of the two AGC circuits. Which one performed better? Explain.

Which circuit has a more predictable and accurate output? Explain.

Which one operated over a wider frequency range?

BREADBOARD LAYOUT

