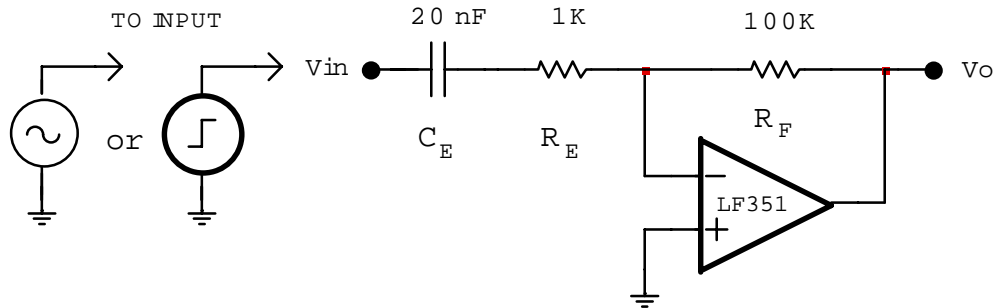


# DIFFERENTIATOR AND INTEGRATOR CIRCUITS

## PART 1      DIFERENTIATOR



**LF351 OP AMP DATA:**  $V_{sat} = \pm 13,5V$  typical at  $V_{sup} = \pm 15V$ ,  $I_{limit} = \pm 20$  mA typical


### PRE-LAB

1. If  $V_{in}$  is a  $0,3 V_{pp}$  triangular wave, determine the output waveform relative to  $V_{in}$ , at frequencies of 100, 200 and 300 Hz.
2. If  $V_{in}$  is a  $0,3 V_{pp}$  sine wave, determine the output waveform relative to  $V_{in}$ , at frequencies of 100, 200 and 300 Hz.
3. If  $V_{in}$  is a  $0,3 V_{pp}$  square wave, determine the output waveform relative to  $V_{in}$ , at frequencies of 100, 200 and 300 Hz – also calculate the time constant of the exponential edges of  $V_o$ .

### LAB


1. Set  $V_{off}$  and  $I_{off}$  to 0 in the op amp model - double click on op amp and edit model parameters.
2. Edit the pulse source or the sine source to obtain the proper input.- see page 3 to learn how to edit the pulse source to obtain a square wave or a triangular wave.
3. Verify all of your pre-lab predictions - label all Microcap waveforms with peak values and relevant times. Also write your name right on the graph and include in your lab report.  
For the squarewave input case, display  $V_{in}$ ,  $V_o$  and  $V_F$  and then measure the time constant of the exponential edges of  $V_o$  – to do so, measure two points  $(t_1, V_1)$  and  $(t_2, V_2)$  and  $V_F$  on the exponential edges of  $V_o$  then calculate 
$$\tau = (t_2 - t_1) / \ln \left( \frac{V_1 - V_F}{V_2 - V_F} \right)$$
4. Input a  $0,3 V_{pp}$  triangular wave with a frequency of 5 kHz and look at the output waveform. Explain what happens here. Include waveform in lab report.
5. Change the 1K resistor to 100 and input a  $0,3 V_{pp}$  triangular wave with a frequency of 200 Hz and look at the output waveform. Explain what happens here. Include waveform in lab report.
6. Repeat step 5 with a square wave input.

## PART 2      INTEGRATOR

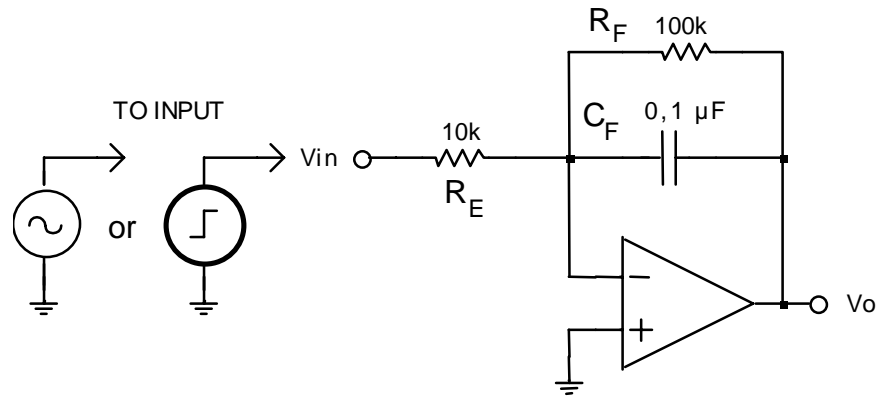

### PRE-LAB

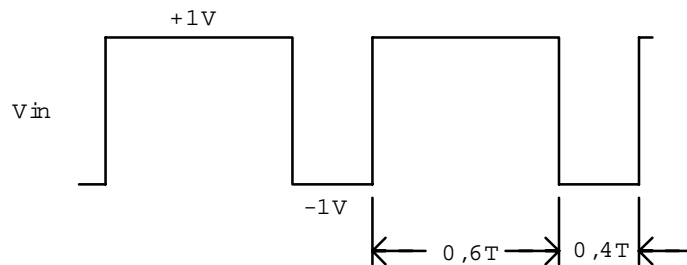1. Draw O/P waveform with respect to  $V_{in}$  shown for frequencies of 50 Hz, 100 Hz, 1 kHz and 10 kHz - label waveforms with AC and DC values as well as PW and SW.



- If  $V_{in}$  is a 4  $V_{pp}$  squarewave with a 75% duty cycle, calculate the frequency of  $V_{in}$  that will produce  $V_o = 1 V_{pp}$
- If  $V_{in}$  is a 10  $V_{pp}$  triangular wave with a frequency of 5 kHz, draw the expected O/P waveform with respect to  $V_{in}$ .

### LAB

Verify all waveforms predicted in the pre-lab with Microcap and explain any major discrepancies. For step 1 of pre-lab, ensure that you include 50 Hz and 100 Hz in the measurements to observe the behavior of the integrator when it does not integrate: draw the "unexpected" waveforms and explain them – measure the time constant of  $V_o$  for the 50 Hz and 100 Hz cases and verify that  $\tau = R_F C_F$ .  $V_{in}$  is not integrated when the period of  $V_{in}$  is not much smaller than  $\tau = R_F C_F$ .

Include all  $\mu$ Cap simulations in your lab report.

### LAB REPORT

Compare all pre-lab waveforms/values to the  $\mu$ Cap results, highlight discrepancies and explain. Include all  $\mu$ Cap simulations in report and answer all questions in lab procedure.


## EDITING THE PULSE SOURCE

### SQUARE WAVE

To edit the pulse source parameters, double-clicking the source symbol in the "select" mode and use the following values:

VONE=5V    VZERO=-5V    P1=0    P2=1n    P3=1m    P4=1m+1n    P5=2m

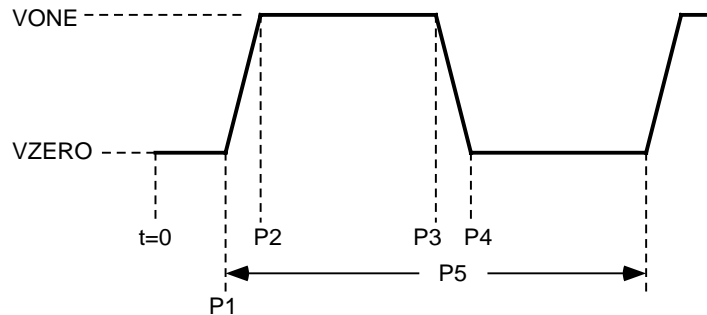The above parameters define a  $10V_{pp}$  500 Hz squarewave with 1ns rise and fall times and 50% duty cycle. The parameters of the pulse source are defined on the waveform shown below.



### TRIANGULAR WAVE

VONE=0.15V    VZERO=-0.15V    P1=0    P2=1m    P3=1m    P4=2m    P5=2m

The above parameters define a 500 Hz triangular wave with A 0,3  $V_{pp}$  amplitude.

