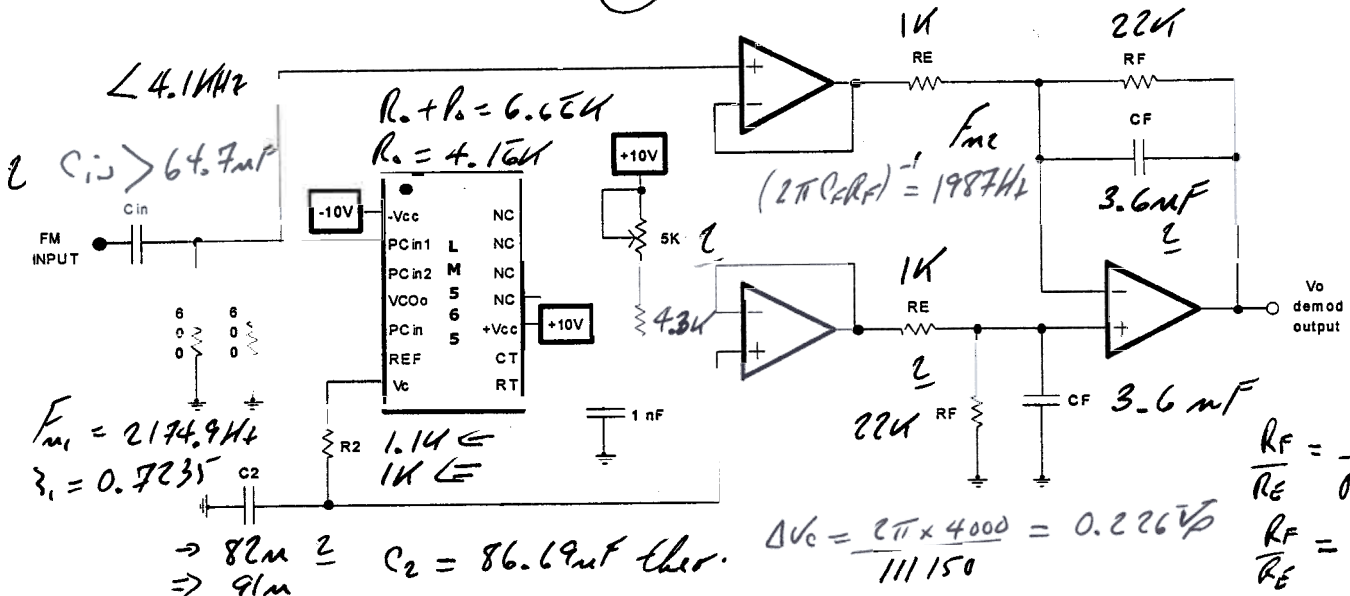


NAME: SOLUTIONS

25




A) Design a 3rd order FM demodulator with a BESSEL response that meets the following specs:

$F_{mod} = 0 \text{ to } 1000 \text{ Hz}$        $F_{car} = 45 \text{ kHz}$       FM frequency deviation = 0 to 4 kHz (peak)  
 Demodulator response: low-pass Bessel response with bandwidth of 1500 Hz  
 Normalised demodulator poles:  $1.32475 \angle 180^\circ$        $1.44993 \angle \pm 136.348^\circ$       } = 0.7235 } 4  
 Demod output: 0 to 5 V<sub>p</sub>       $12.485 \angle 180^\circ$        $13665 \angle \pm 136.348^\circ$   
 $F_{cen} \approx 0.3 / ((R_o + P_o)C_o)$        $K_d \approx 0.68 \frac{V}{rad}$        $K_o = \frac{\Delta \omega_{in}}{\Delta V_{C(Thev)}} \approx \frac{49.4 F_{cen}}{\Delta V_{CC}} = 111150 \frac{1/p}{V}$   
 $\tau_1 = R_1 C_2$        $\tau_2 = R_2 C_2$        $R_1 = 3.6K$        $\tau_1 + \tau_2 = \frac{K_o K_d}{\omega_n^2}$        $\tau_2 = \frac{2\zeta}{\omega_n} \cdot \frac{1}{K_o K_d} = 92.665 \mu s$   
 $312.08 \mu s$        $92.665 \mu s$       4       $404.75 \mu s$        $\zeta_1 = 312.08 \mu s$

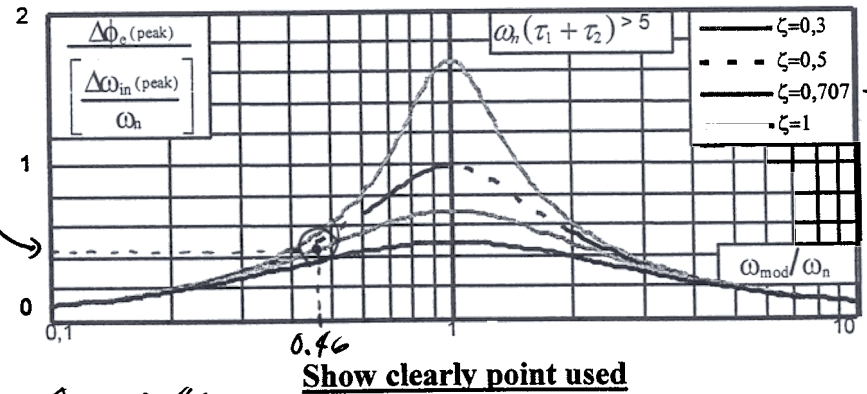B) Determine the maximum peak phase error if modulation is assumed to be sinusoidal.

Normalised phase error for FM sinusoidal modulation



$\approx 0.45$   
 $\omega_n(\tau_1 + \tau_2) = K_o K_d / \omega_n$   
 $= 5.53 > 5$   
 Curves valid  
 $F_{mod} = 0 \rightarrow 1000 = 0 \rightarrow 0.46$   
 $F_{m1} = 2174.9$

5% standard capacitors and resistors

1	1.1	1.2	1.3	1.5	1.6	1.8	2	2.2	2.4	2.7	3	x 10 <sup>N</sup> N = ... -3, -2, -1, 0, 1, 2, 3 ...
3.3	3.6	3.9	4.3	4.7	5.1	5.6	6.2	6.8	7.5	8.2	9.1	

$\Delta \phi_e (peak) \approx 0.45 \times 4000 / 2174.9 = 0.8276 \text{ } \mu s$